

# Homework 2 Solutions

---


---

---

---



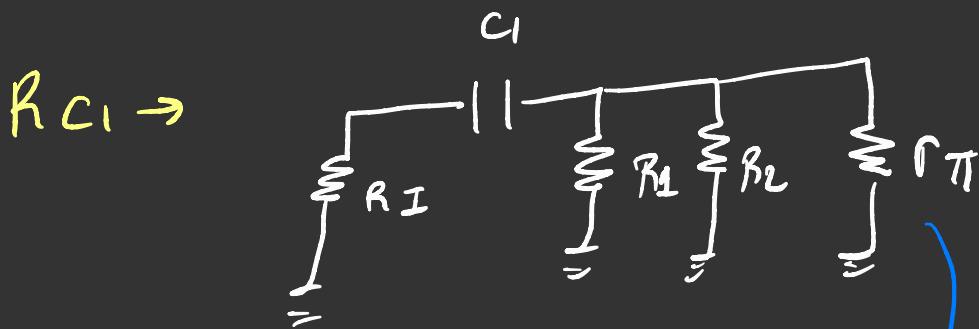
1-a) Let's calculate  
all the time constants  
due to each capacitor.



$$T_{C_1} = C_1 [R_I + (R_1 // R_2 // R_\pi)]$$


I did not neglect  
since  $V_A < \infty$

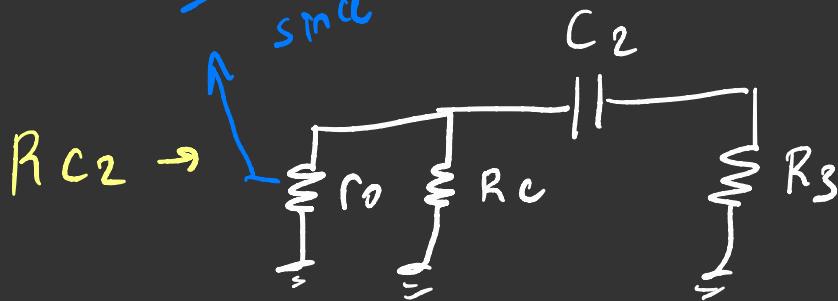$R_E$  is  
not effective  
since  $C_S$   
shorts.



$$T_{C_2} = C_2 \cdot [(R_c // R_o) + R_3]$$

$C_3$  is a little bit more tricky.

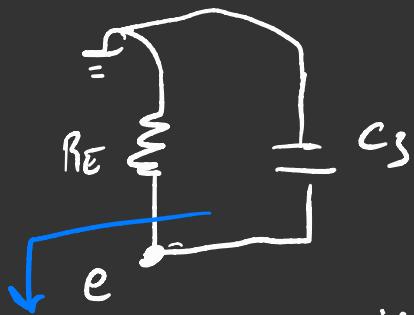


what is the resistance seen by the emitter side of the transistor. we have resistance at base. Thus, we need to transfer this resistance to the emitter side. we also have  $\frac{1}{g_m}$ . The resistance at base if you short

$$G. R_B = R_I \parallel R_1 \parallel R_2$$

we can transfer it to the emitter by dividing it to  $\beta$ .

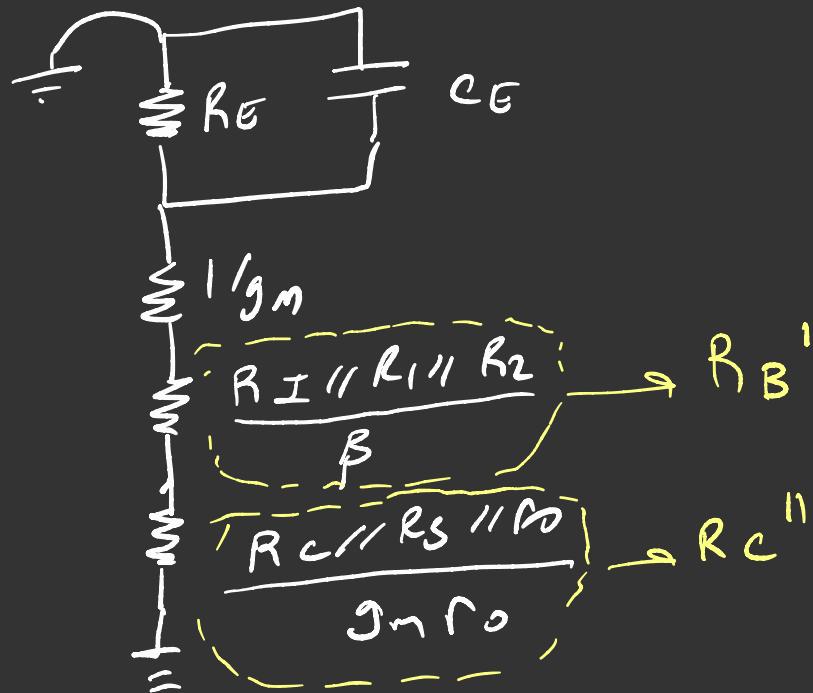♦ We also have  $V_A \approx \infty$  so  
 we can transfer collector resistance  
 to the base by dividing it  
 to  $\text{gm} R_o$ .  $R_{c'} = R_c // R_3 // R_o$   
 when we short  $R_3$ .  
 Regarding this we have,



$$\tau_{c_3} = C_3 \cdot [ R_E // (\frac{1}{g_m} + R_B' + R_C') ]$$

You can write

$$f_{3dB_L} = \frac{1}{2\pi} \left[ \frac{1}{\tau_{c1}} + \frac{1}{\tau_{c2}} + \frac{1}{\tau_{c3}} \right]$$

I did not write all the expression since it will be too long. The key is to find the time constants and equivalent resistances.

1-b) For the mid-band  $C_S$  shorts  $R_E$ .  $R_E$  is not effective. we have a voltage loss due to driver at the input.






$$R_1 \parallel R_2 \parallel \frac{\beta}{g_m} = R_{BB}$$

$$\frac{V_b}{V_I} = \frac{R_{BB}}{R_{BB} + R_I}, \quad V_b = V_{be}$$

A + the output

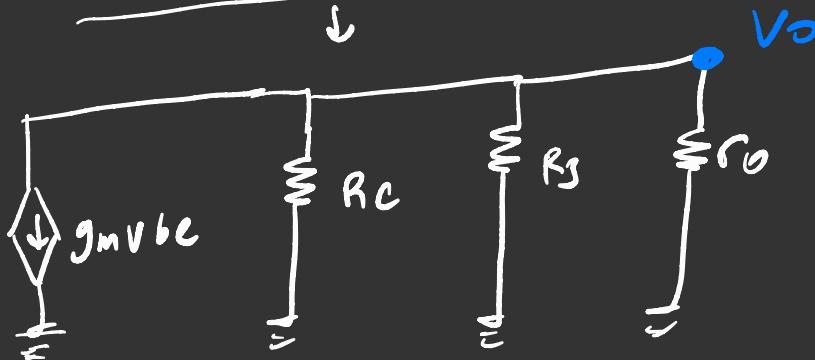


Loss factor  
 due to realistic  
 source resistance.

$$R_C \parallel R_B \parallel R_L = R_L'$$

$$\frac{V_O}{V_b} = g_m R_L'$$

$$\boxed{\frac{V_O}{V_I} = g_m R_L' \left( \frac{R_{BB}}{R_{BB} + R_I} \right)}$$

1-c) At the input  
we have

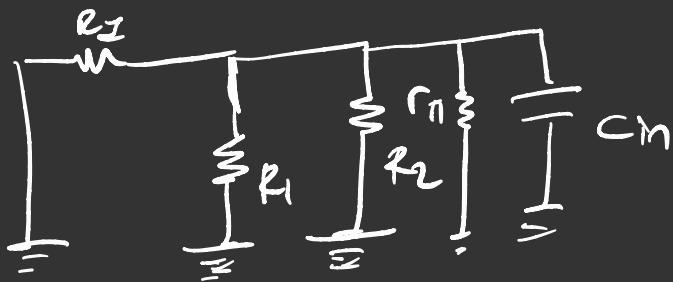

$$C_{in} = C_{\pi} + (g_m R_L^1) C_P$$

↳ recall  $R_L^1$  from  
2-b  
Miller effect


$C_{in}$  sees the equivalent resistance

$$R_{eq} = R_1 \parallel R_2 \parallel r_{\pi}$$

$$f_{p_1} = \frac{1}{2\pi(C_{in} R_{eq})}$$

Again, the important part is to find  
resistance and capacitance.

At the output

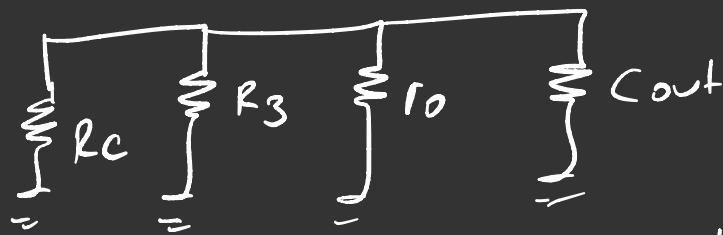

→ The Miller capacitance reflects to the output with its own value.


$$C_{out} = C_P$$

$$R_{Cout} = R_C \parallel R_3 \parallel R_O$$

$$f_{P2} = \frac{1}{2\pi (C_{out} R_{Cout})}$$

→ Note that we are shorting the bypass and coupling capacitors as their impedance goes to zero, while frequency is increased.  $\rightarrow T_C = \frac{1}{sC}$

2) At the input

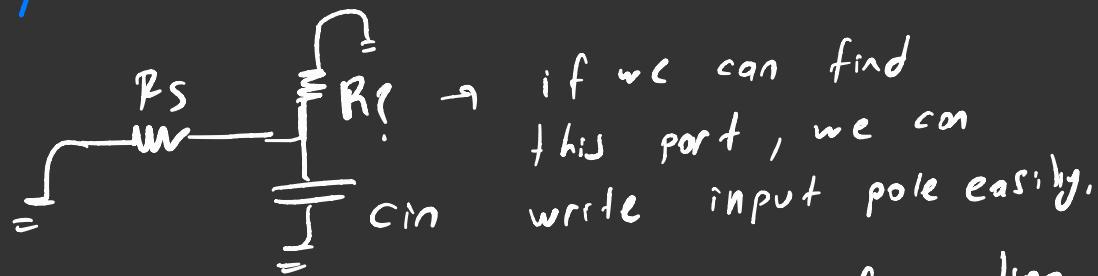

we have a common gate configuration.

The input resistance of it,

$$\left( \frac{1}{g_m} + \frac{R_D}{g_m r_0} \right), \text{ if } \lambda > 0$$


However, we also have  $R_P$ , thus

$$R_g = \frac{1}{g_m} + \frac{R_D}{g_m r_0} + R_P \rightarrow \text{the important part of the question}$$

$$f_{PIN} = \frac{1}{2\pi \underbrace{(R_S // R_g)}_{\text{we know these variables}} C_{in}}$$


we know these variables

At the output

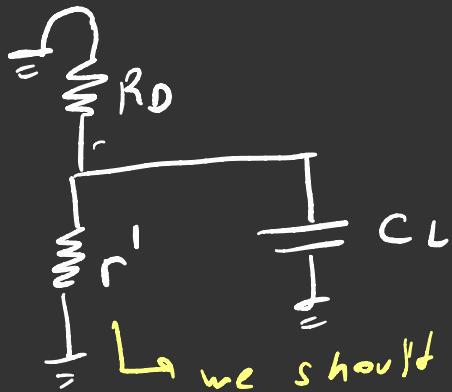

we should find this resistance

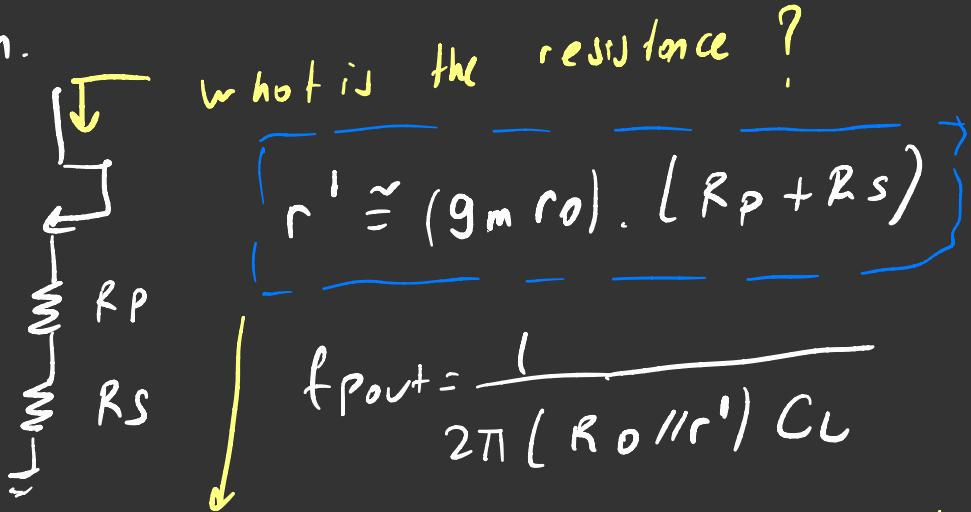
Essentially, when you look to the configuration from the drain, it's an amplifier with source degeneration.



the important part of the question

3) At the input we do not have any pole if we assume  $V_{in}$  is ideal, which means source resistance of the  $V_{in}$  source is equal to zero.

### At the output

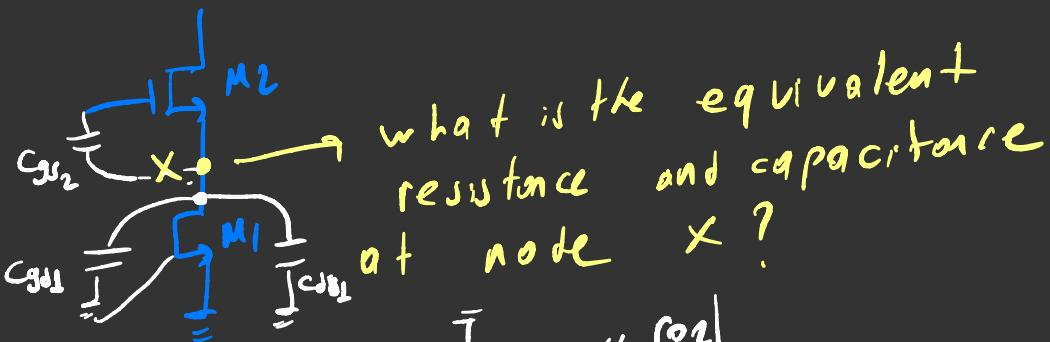


Gate is AC  
grounded as  $V_b$   
is a DC voltage.

$$\begin{aligned}
 & \text{Equivalent resistance at node } X: \\
 & R_{eq} = R_{01} \parallel R_{02} \parallel \frac{1}{g_{m2}} \\
 & \text{Equivalent capacitance at node } X: \\
 & C_{eq} = C_{gd1} + C_{db1} + C_{gs2}
 \end{aligned}$$


$$f_{3dB} = \frac{1}{2\pi(R_{eq})(C_{eq})}$$



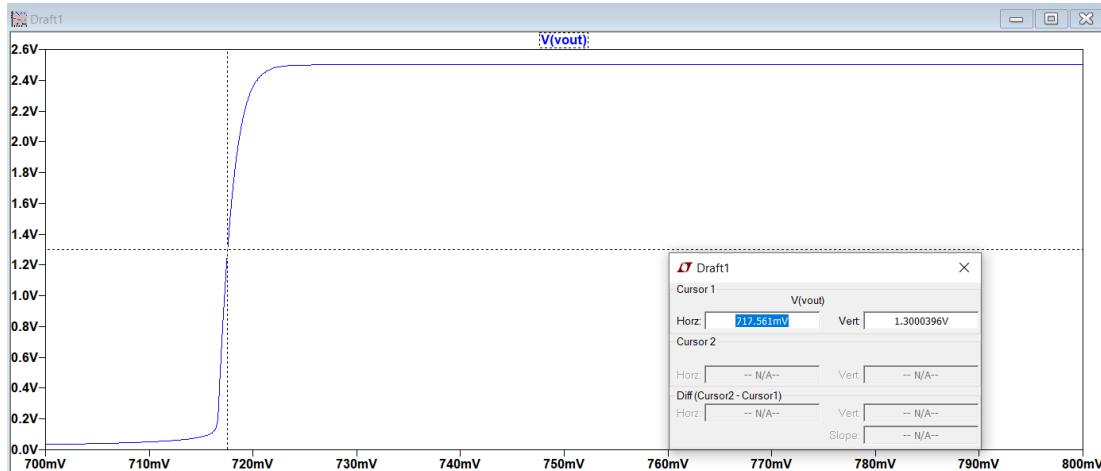4) a) To bring the output to the desire value 1.3V, the input source can be swept. You may need to increase the resolution of the sweep, since the circuit may have a large gain and the output would be very sensitive in this case. In figure below, you can see that, the required input DC level is 717.651 mV.



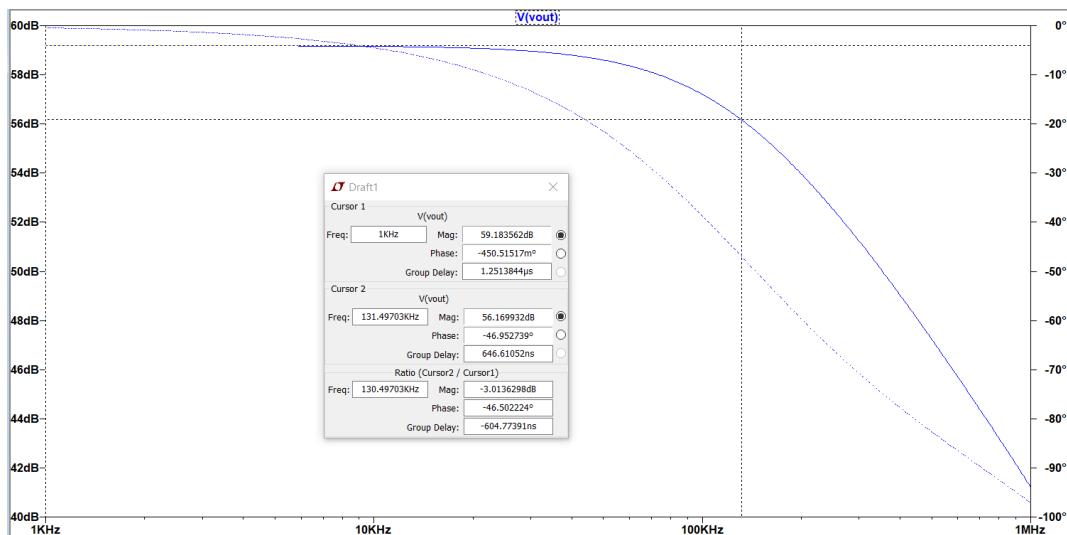b) In the figure below, you can see the bode plot of the  $V_{out}/V_{in}$ . The gain is around 59 dB and the bandwidth is around 130 kHz. Also look at carefully to the phase in the cursor. It is around 45 degree, which is expected. You may not observe the effect of 200fF load capacitance as discrete transistors such as 2N2222 has really large parasitic capacitance.



As you observed, the biasing is really challenging in this way ( $V_{DCin}=717.561\text{mV}$ , in real life supplies are not precise as much as in this question). The open loop amplifiers generally have this problem. In the negative feedback, we are going to see the feedback will also set the DC bias.