
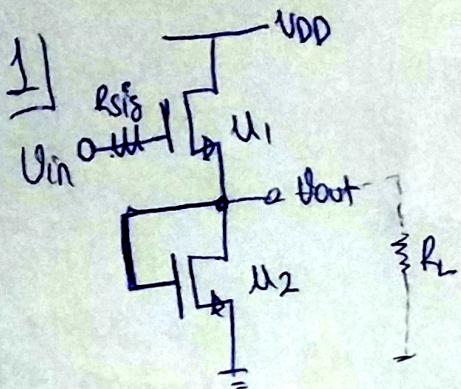


HW3 - 2020


Serdan Salt Frat
040170025

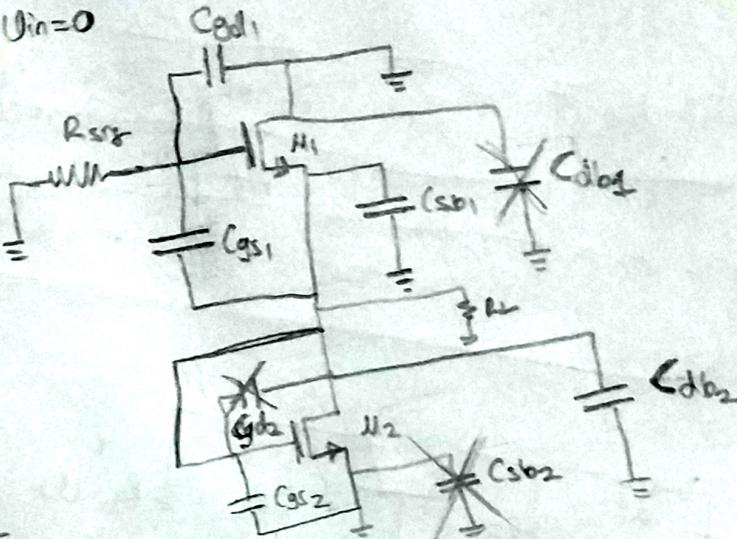

1) $U_{in} = 0$




2) Remove redundancies

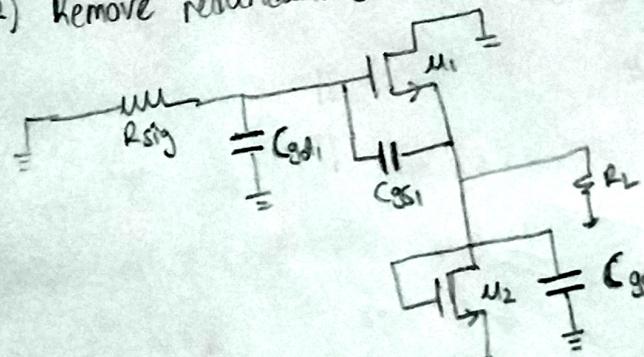


3) Consider one capacitor at time and replace others as open circuit.


For C_{gd1}

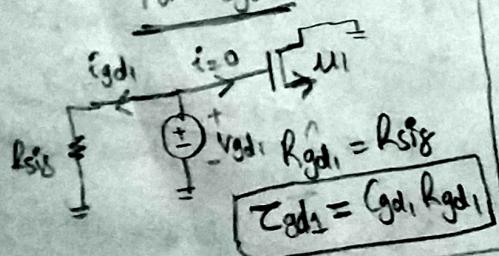

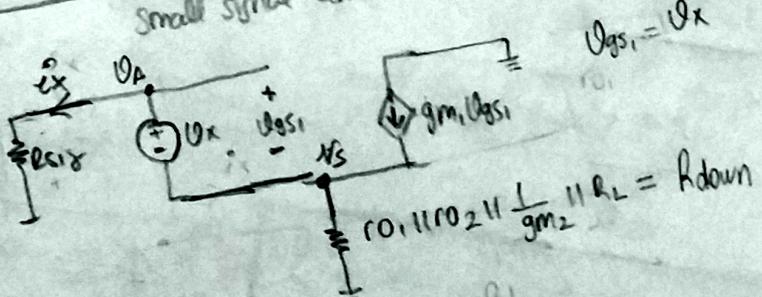For C_{gs1} (Since it is a floating capacitor we need to do small signal analysis)



For C_{out}

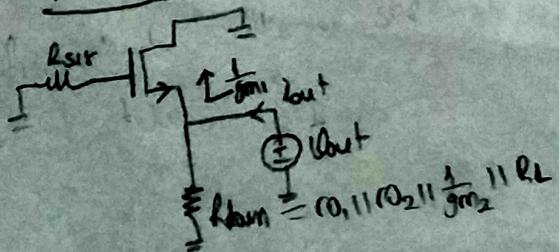

$$R_{out} = (ro_1 \parallel ro_2 \parallel \frac{1}{gm_1} \parallel \frac{1}{gm_2} \parallel RL)$$

$$Z_{out} = C_{out} R_{out}$$

$$ix R_{sig1} = U_x - U_{gs1} = gm_1 U_{gs1} R_{down}$$

$$\frac{U_x}{ix} = R_{gs1} = \frac{R_{sig1} + R_{down}}{1 + gm_1 R_{down}}$$

$$\Rightarrow R_{gs1} = \frac{R_{sig1} + (ro_1 \parallel ro_2 \parallel \frac{1}{gm_2} \parallel RL)}{1 + gm_1 (ro_1 \parallel ro_2 \parallel \frac{1}{gm_2} \parallel RL)}$$


$$- Z_{gs1} = C_{gs1} R_{gs1}$$

Then according to open-circuit time constant methodology.

$$f_{3-\text{dB}} = \frac{1}{\sum_{i=1}^3 Z_i} = \frac{1}{(Z_{\text{out}} + Z_{\text{gsi}} + Z_{\text{gd}})2\pi}$$


$$f_{3-\text{dB}} = \frac{1}{2\pi(C_{\text{out}}R_{\text{out}} + C_{\text{gsi}}R_{\text{gsi}} + C_{\text{gd}}R_{\text{gd}})}$$

2)

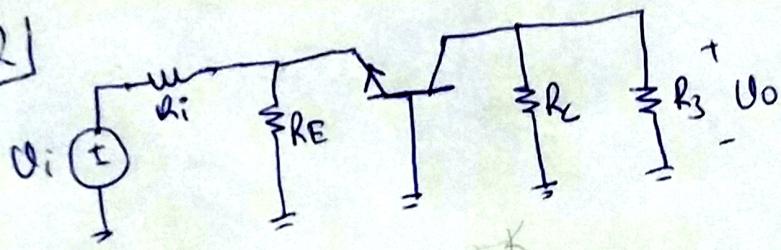


Since C_1 and C_2 are coupling capacitors, at high frequencies, they becomes short circuit.

1) $\text{O}_i = 0$

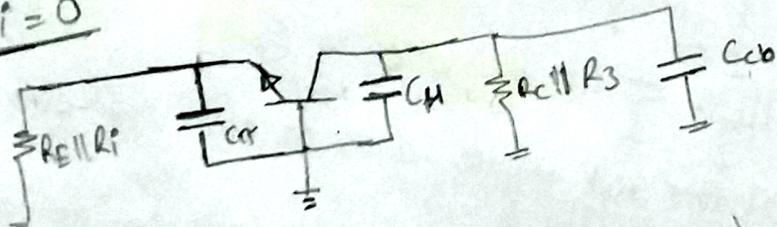

For $C\pi$

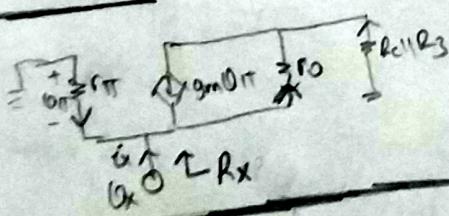

$$\text{O}_x - \left(i_x + \frac{\text{O}_i}{r_\pi} + g_m \text{O}_i \right) r_o - \left(i_x + \frac{\text{O}_i}{r_\pi} \right) (R_{cll} R_3) = 0$$

$$\text{O}_x - \left(i_x - \frac{\text{O}_x}{r_\pi} - g_m \text{O}_x \right) r_o - \left(i_x - \frac{\text{O}_x}{r_\pi} \right) (R_{cll} R_3) = 0$$

$$\text{O}_x - \left(i_x - \frac{\text{O}_x}{r_\pi} - g_m \text{O}_x \right) r_o - \left(i_x - \frac{\text{O}_x}{r_\pi} \right) (R_{cll} R_3) = 0$$


$$\text{O}_x \left(1 + \frac{r_o}{r_\pi} + g_m r_o + \frac{R_{cll} R_3}{r_\pi} \right) - i_x (r_o + R_{cll} R_3) = 0$$

$$R_{\text{X}} = \frac{r_o + (R_{cll} R_3)}{r_o + (R_{cll} R_3)} = \frac{r_{\text{mro}} + r_\pi (R_{cll} R_3)}{r_\pi + r_o + g_m r_o + r_o + (R_{cll} R_3)}$$

$$R_{\text{X}} = \frac{1 + \frac{r_o}{r_\pi} + g_m r_o + \frac{R_{cll} R_3}{r_\pi}}{\frac{r_\pi (r_o + R_{cll} R_3)}{r_\pi + (R_{cll} R_3)}} \Rightarrow R_{\text{pi}} = R_{\text{X}} \parallel R_E \parallel R_P$$

$$Z_{\pi} = C_{\pi} R_{\pi} = C_{\pi} (R_{\text{X}} \parallel R_{cll} R_3)$$

For $C_{\mu} + C_{cb}$

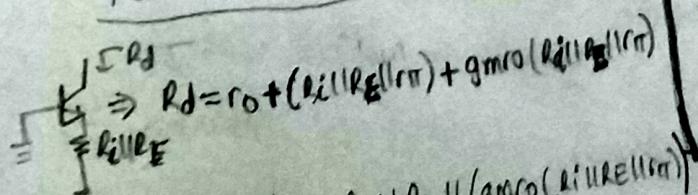


$$R_{\mu} = R_d \parallel R_{cll} R_3 \times R_{cll} R_3 \parallel (g_{mro}(R_{cll} R_{cll} R_3))$$


$$Z_{\mu} = (C_{\mu} + C_{cb}) [R_{cll} R_3 \parallel (g_{mro}(R_{cll} R_{cll} R_3))]$$

$$f_{3-\text{dB}} = \frac{1}{2\pi(Z_{\mu} + Z_{\pi})}$$

3

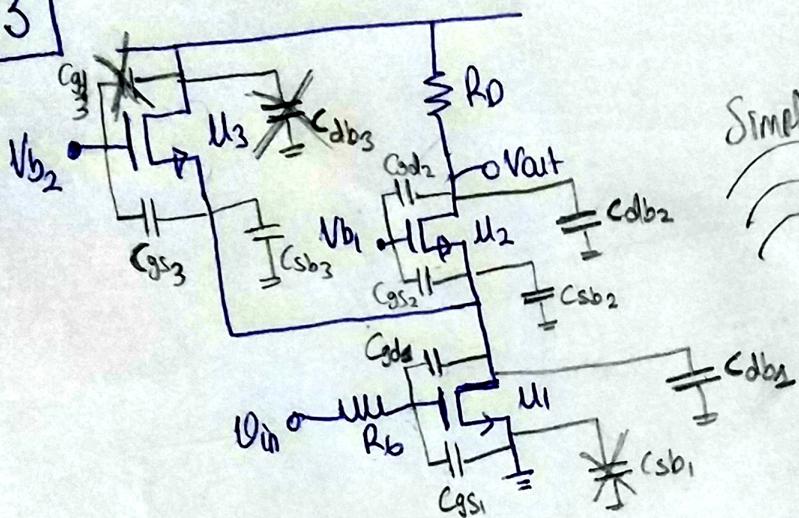

Simpliffr

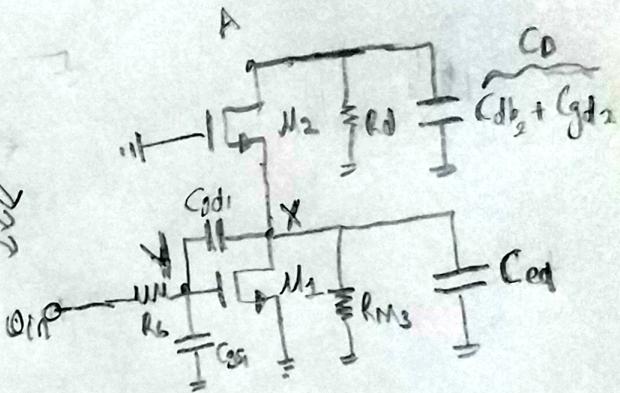



where

$$C_{eq} = C_{db1} + C_{gs2} + C_{sb2} + C_{gs3} + C_{sb3}$$

There is only one floating capacitor, C_{gd1} , and since we're asked to apply Miller's approximation, we need to calculate the DC gain between the terminals at C_{gd1} . (Between the terminals X-X')

In order to find DC gain we need to find R_{out} for which V_{out} is taken from the

drain of M_1 (Node X)

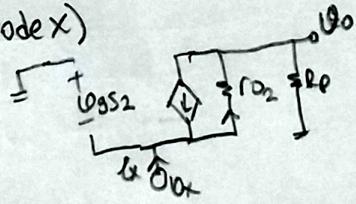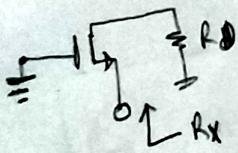


$$V_x - (ix + gm_2 C_{gs2}) R_02 - ix R_0 = 0$$

$$(V_x (1 + gm_2 R_02)) = ix (R_02 + R_0)$$

$$R_{X'} = \frac{V_x}{ix} = \frac{R_02 + R_0}{1 + gm_2 R_02} = \frac{(1/gm_2)(R_02 + R_0)}{\frac{1}{gm_2} + R_02}$$

$$R_X \approx \frac{R_02 + R_0}{gm_2 R_02} \quad (\text{since } R_02 \gg \frac{1}{gm_2})$$

Then,

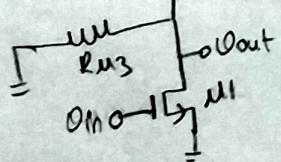

$$6m = gm_1$$


$$R_{out} = R_X \parallel R_{M3} \parallel R_01$$

$$R_{out} = \left(\frac{R_02 + R_0}{gm_2 R_02} \right) \parallel \left(\frac{1}{gm_3} \parallel R_03 \right) \parallel R_01$$

$$Av = gm_1 \left[\left(\frac{R_02 + R_0}{gm_2 R_02} \right) \parallel \left(\frac{1}{gm_3} \parallel R_03 \right) \parallel R_01 \right]$$

Now we separate C_{gd1} into two standard capacitors by using Miller's theorem.

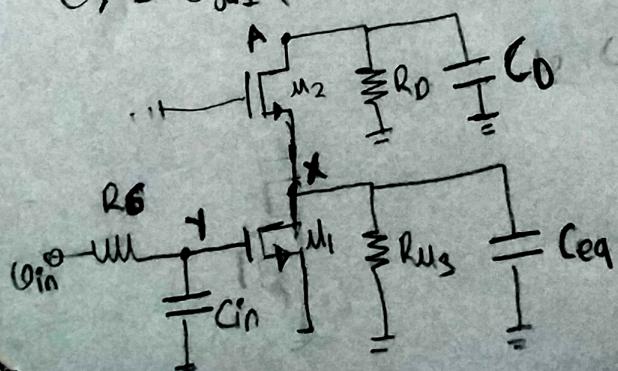$C_y = C_{gd1} (1 + Av)$; $C_x = C_{gd1} \left(1 + \frac{1}{Av} \right)$, and draw the new model




where

$$C_0 = C_{db2} + C_{gd2}$$

$$C_{in} = C_y + C_{gs1}$$

$$C_{eq} = C_x + C_{db1} + C_{gs2} + C_{sb2} + C_{gs3} + C_{sb3}$$

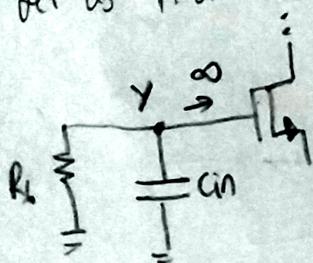Now, we obtained the model that we can apply the pole identification on
 let us first examine input pole which stems from the capacitor C_{in}




$$R_y = R_b$$

$$Z_y = C_{in} R_b$$

$$f_{in} = \frac{1}{2\pi C_{in} R_b}$$

Then, examine C_{eq}

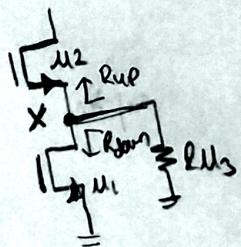we have found that $R_{up} \approx \frac{r_{O_2} + R_0}{g_{m_2} r_{O_2}}$




and we know $R_{down} = r_{O_1}$

Then $R_x = R_{M_3} \parallel R_{up} \parallel R_{down}$

$$\Rightarrow R_x = \left(\frac{1}{g_{m_3}} \parallel r_{O_3} \right) \parallel \left(\frac{r_{O_2} + R_0}{g_{m_2} r_{O_2}} \right) \parallel r_{O_1}$$

$$\Rightarrow Z_x = C_{eq} R_x \Rightarrow f_{eq} = \frac{1}{2\pi C_{eq} R_x}$$

Lastly, examine C_{up}

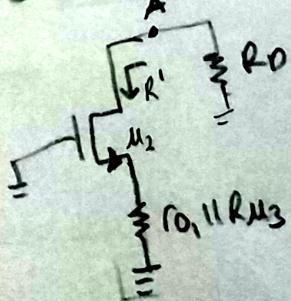

$$R' = r_{O_2} + (r_{O_1} \parallel R_{M_3}) + g_{m_2} r_{O_2} (r_{O_1} \parallel R_{M_3})$$

$$R_A = R_0 \parallel R' = R_0 \parallel [r_{O_2} + (1 + g_{m_2} r_{O_2})(r_{O_1} \parallel R_{M_3})]$$

$$Z_A = R_A C_0$$

$$f_A = \frac{1}{2\pi (R_A C_0)}$$

Node's names

X: Drain at M_1 and Source of M_2

Y: Gate of M_1

A: Drain at M_3

R_{M_3} : The resistance seen looking into the source of M_3