

# Homework-3 Solutions

---


---

---

---



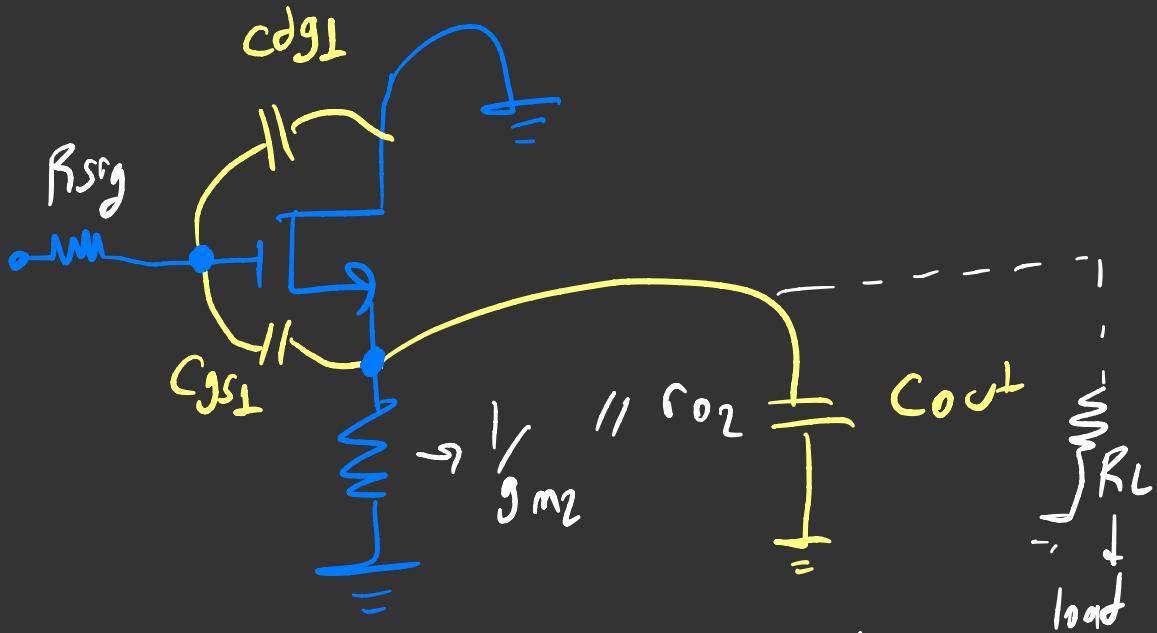1) Let's simplify the circuit and insert parasitic capacitances.



$$C_{out} = C_{sb1} + C_{gs2} + C_{db2}$$

\* The rest of the parasitics are short - Due to AC ground.  
 (For ex.  $C_{db1} \rightarrow$  drain bulk + ground)

- we need to calculate  
3 different time constant.


For Cd91

→ It is obvious. Cdg1 sees R<sub>SIG</sub> as the equivalent resistor


$$I_1 = R \sin \theta g d\perp$$

For Court

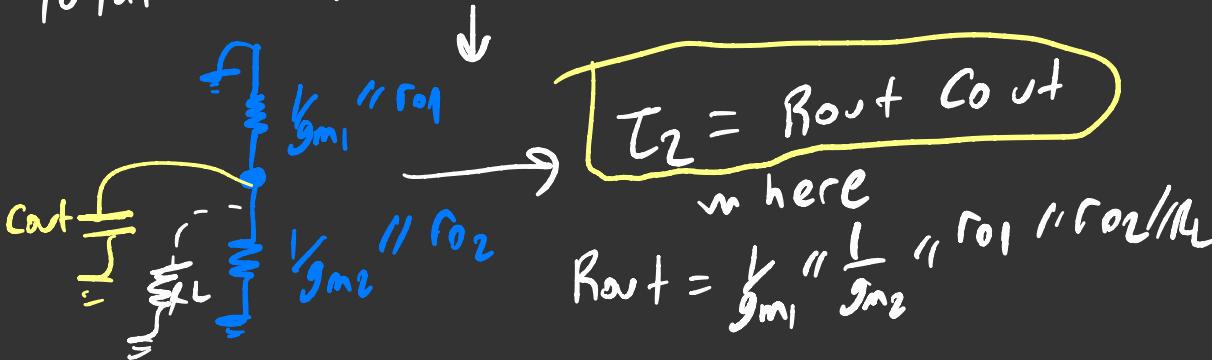→ It is also easy.  $C_{out \ see}$   
total output resistance



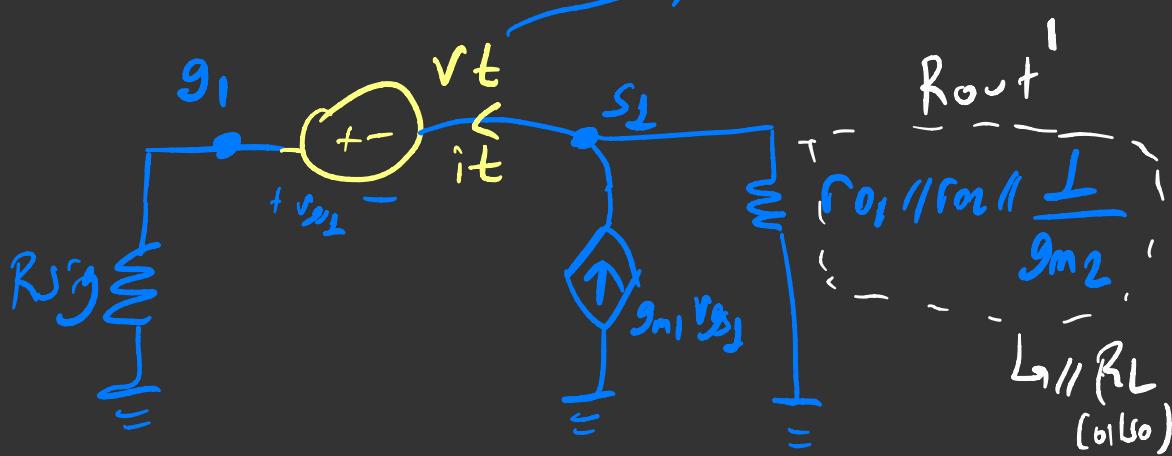☞  $C_{gs1}$  is the tricky part.  
 Remember in Hw-2 we neglected it as we assumed  $R_{sig} = 0$ , but in this case we have  $R_{sig}$ . test voltage.



☞ Be careful while you are modelling. The transistor always converts  $v_{gs}$  to  $g_m v_{gs}$  (voltage-current conversion).

we need FUL in here,  
but we are gonna discuss  
the results.

$$V_t = i_t R_{sig} + (i_t - g_m V_{gs1}) R_{out}^{-1}$$
$$V_{gs1} = V_t \nearrow$$

we have

$$R_{gs} = \frac{V_t}{i_t} = \frac{R_{sig} + R_{out}^{-1}}{1 + g_m R_{out}^{-1}}$$

$$T_3 = C_{gs1} \frac{R_{sig} + R_{out}^{-1}}{1 + g_m R_{out}^{-1}}$$



$$f_{3dB} = \frac{1}{2\pi (C_1 + C_2 + C_3)}$$


A discussion on the  
effect of  $C_{GS}$   
to  $3dB$  frequency

(you can skip this part)


To understand the effect of  $C_{GS}$  in the source follower, we also need to understand the effect of Miller capacitance  $C_{GD}$  in common-source amplifiers.

(P.S. → you can jump to page 16, this is extra)

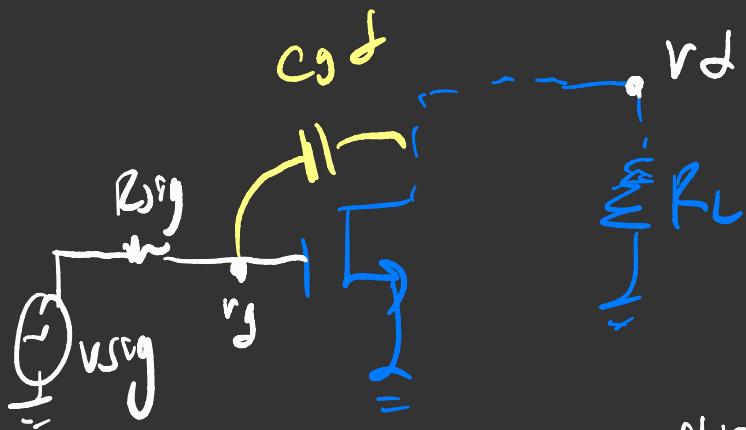So first of all think about Miller Effect. If will be an intuitive analysis that you cannot find in the textbooks.



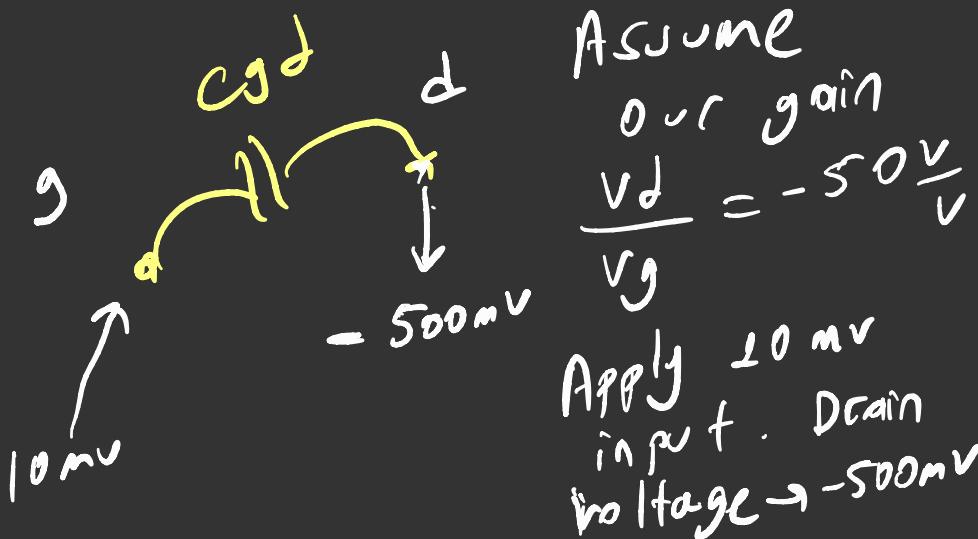
- why we are multiplying with the gain  $\frac{Vd}{Vg}$  ?
- what are we changing at the input? (beside  $Cgs$ )



The results

- we need to charge  $C_{gd}$  with  $10 \text{ mV} - (-500 \text{ mV})$   
 $= 510 \text{ mV}$
- so we need more time  
 because instead of just  $10 \text{ mV}$   
 we are charging  $C_{gd}$  with  $510 \text{ mV}$ !

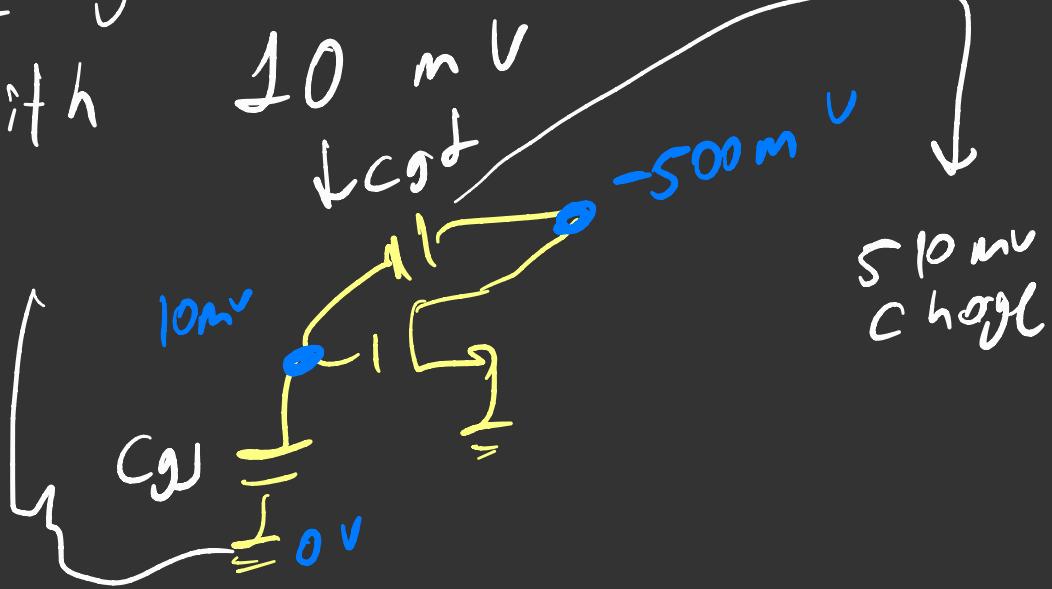• On the other hand, for CGJ we just have to charge with




$10 \text{ mV}$  charge

• This is why we multiply the  $C_{GJ}$  with the gain. It is basically a capacitive voltage multiplier.

So what about  $C_{GS}$  for source followers?

10mV

Apply small signal.

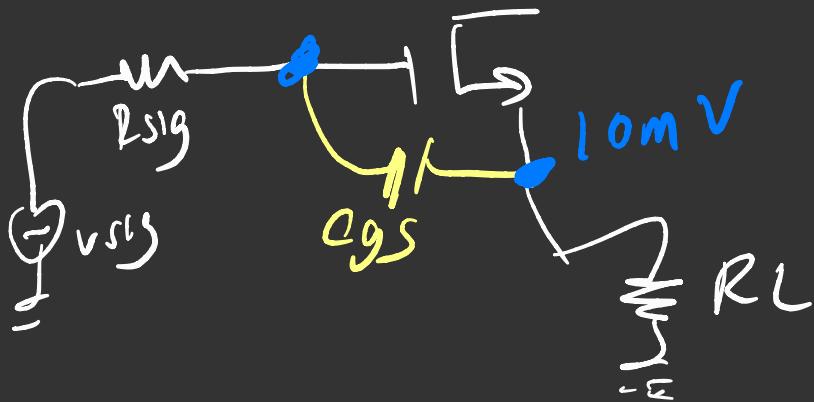


• What is the gain of source followers?  $IV/V$

a So if we are talking

about charging, we are

not even charging  $C_{GS}$  in this case. ↓

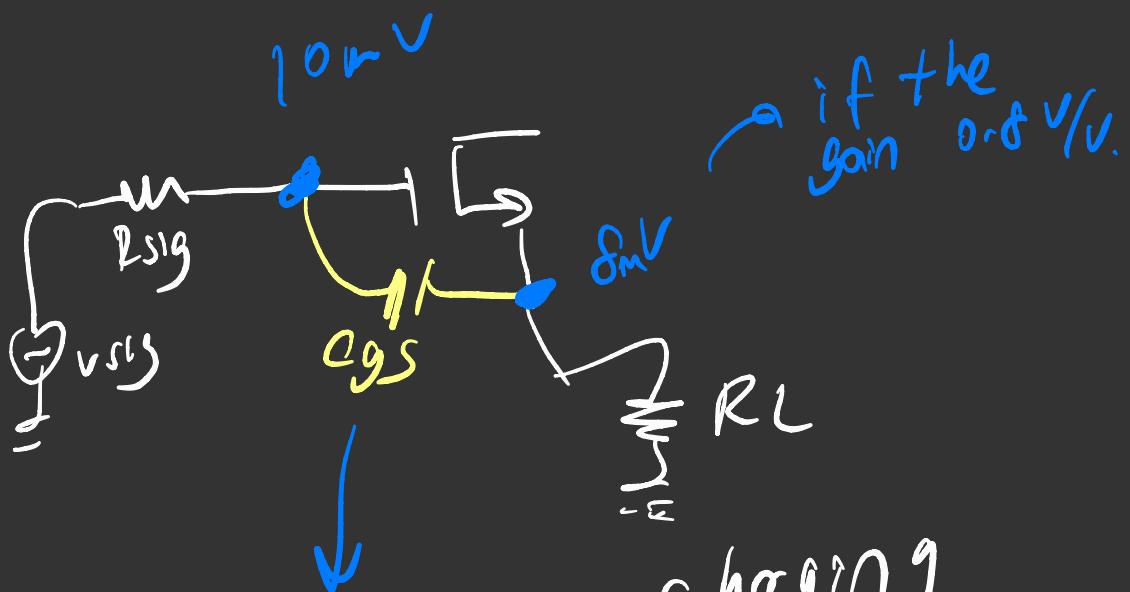- But, we know that, generally gain is  $0.7, 0.8 V/V$  instead of  $1 V/V$  due to non-idealities.



Still we are charging  
 $C_{GS}$  with  $2mV$  instead of  
 $10mV \rightarrow$  Effective  $C_{GS}$ ,  
 $= C_{GS}/5$

# It is like reverse Miller effect!

Now, let's think about  
 $T_3$  in the question -

$$T_3 = C_{GS1} \frac{R^{\text{sig}} + R^{\text{out}}}{1 + g_m R^{\text{out}}}$$

where  $R^{\text{out}} = \frac{1}{g_m (R_1 || R_2 || RL)}$

Assume  $R_1, R_2 \gg g_m$  and  $RL$   
 (It should be in a good design)


$$T_3 \approx C_{GS1} \frac{R^{\text{sig}} + \left( \frac{1}{g_m} || RL \right)}{g_m \left( \frac{1}{g_m} || RL \right)}$$



→ Why do we use source follower?

- Voltage Buffer

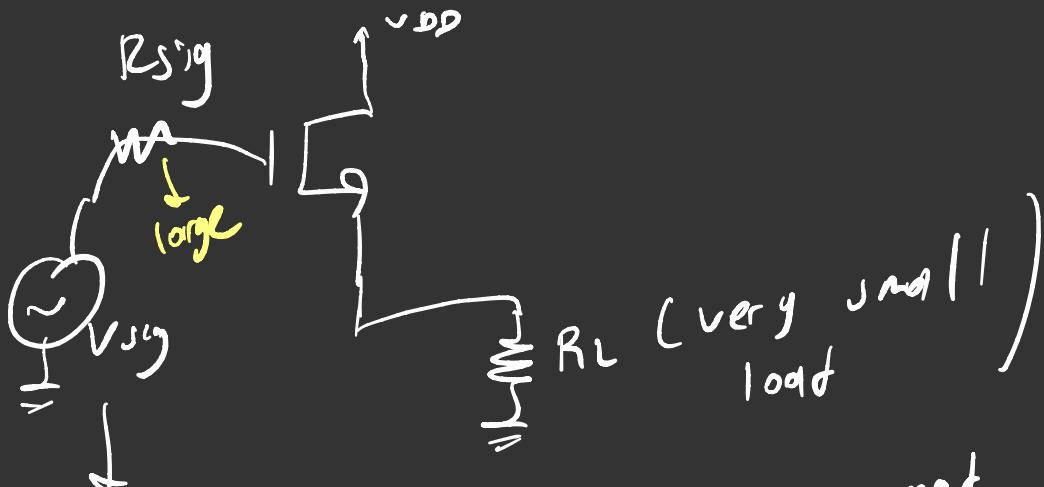↳ we need to drive  
very small resistance  
such as speaker (coil)  
in audio amplifiers.



Normally  
it comes  
from another  
stage.

In or out  
buffer  
 $R_L \ll \frac{1}{gm}$

So let's recall  $T_3$   
again.

$$T_3 \approx C_{S\perp} R_{sig} + \frac{\left( \frac{1}{g_m 2} // R_L \right)}{g_m 1 \left( \frac{1}{g_m 2} // R_L \right)}$$

rearrange

$$R_{sig} \Rightarrow \frac{1}{g_m 2} \rightarrow R_L$$

obvious part

$$T_3 \approx \frac{C_{S\perp} R_{sig}}{\left( \frac{1}{g_m 1} \widehat{R_L} \right)}$$

division factor

↳ should be large  
in a good buffer!


## Conclusion

- For  $T_3$  and  $C_{GST}$  we have a reverse Miller effect, effective  $C_S$

$$C_{S,eff} = \frac{C_{GST}}{g_m R_L}$$

- In a good buffer design effect of  $C_{GST}$  on  $SAB$  bandwidth would be negligible!

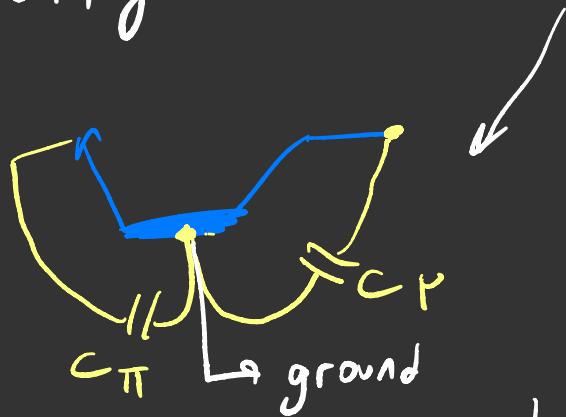
2) for this common-base configuration, we have parasitics



So, we have 2 time constant

$$\tau_1 = \left( R_{in} \parallel R_E \parallel L_I \right) C_\pi$$

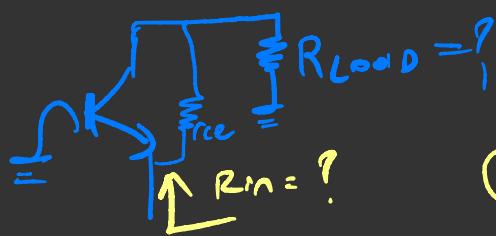what is  $R_{in}$  for common-base configuration



$$R_{LOAD} = R_C \parallel R_S$$


so

$$R_{in} \approx \frac{1}{g_m} + \frac{R_C \parallel R_S}{g_m R_o}$$

I assumed  $\frac{r_L}{\beta} \ll r_o$  ( $r_o = r_{ce}$ )

$$I_2 = R_{out} C_P$$


what is  $R_{out}$ ?

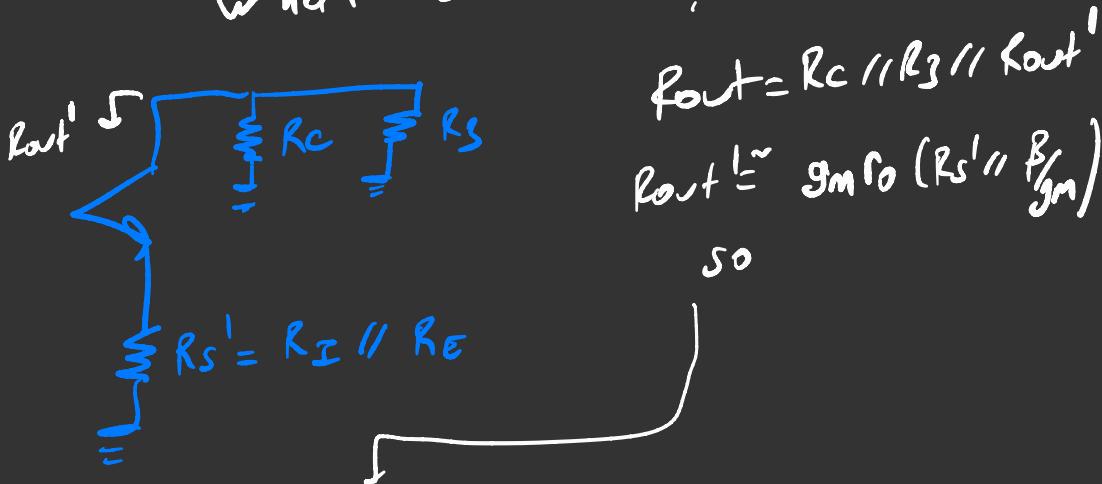

$$f_{3dB} = \frac{1}{2\pi(R_i + I_2)}$$

\* The important point is to find  $R_{in}$  and  $R_{out}$  in this question - In general you will see that  $R_{in} \approx 1/g_m$   $R_{out} \approx R_C \parallel R_S$  since other terms are negligible

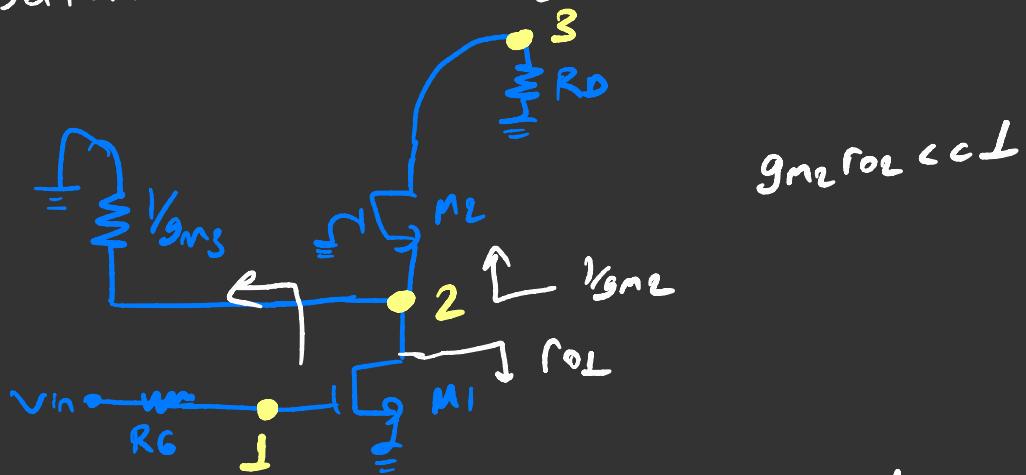3) We have 3 nodes in the signal path. Let's simplify the circuit.



The parasitic capacitances at node-1

$$C_1 = C_{gs1} + C_{gd1} \frac{V_2}{V_1}, \quad R_1 = R_G$$

$$\frac{V_2}{V_1} = g_{m1} \left( \frac{1/g_{m2} \parallel r_{01}}{g_{m3}} \right) \approx \frac{g_{m1}}{g_{m2} + g_{m3}}$$

So

$$T_1 = R_G \left( C_{gs1} + C_{gd} \frac{g_{m1}}{g_{m2} + g_{m3}} \right)$$

$\Rightarrow I$  also assumed  $\frac{1}{g_{m3}} \ll r_{03}$

The parasitic capacitances at node-2

$$C_2 = C_{gd1} + C_{db1} + C_{gs3} + C_{sb2} + C_{gs2}$$
$$+ C_{sb2}$$

$$R_2 = \frac{1}{g_{m2}} \parallel r_{o1} \parallel \frac{1}{g_{m3}} = \frac{1}{g_{m2}} \parallel \frac{1}{g_{m3}}$$

$$I_2 = \frac{1}{g_{m2} + g_{m3}} C_2$$

The parasitic capacitances  
at node-3

$$C_3 = C_{gd2} + C_{db2}$$

$$R_3 = g_{m2} r_{o2} \left( \frac{1}{g_{m3}} \parallel r_{o3} \parallel r_{o1} \right)$$

↳ dominant

$$\parallel R_D$$

$$R_3 \approx g_{m2} r_{o2} \text{ for } \frac{1}{g_{m3}} \ll R_D$$

$$T_3 = \left( \frac{g_{m2}}{g_{m3}} r_{o2} \parallel R_D \right) (C_{gd2} + C_{db2})$$

Discussion about the circuit

(You can skip this part)

→ what is the gain of this circuit?

Let's assume  $g_{m2} \gg g_{m3}$

Gain will be  $g_{m1} R_D$

• Some as common source.

Why do we use cascode?

Recall  $\tau_1$

$$\tau_1 = R_C \left( C_{GS} + C_{GD} \frac{g_m}{g_m + g_{m2}} \right)$$

$$\tau_1 \approx R_C \left( C_{GS} + C_{GD} \frac{g_m}{g_m} \right)$$

Assume  $g_m \approx g_m$

$$\tau_1 \approx R_C (C_{GS} + C_{GD})$$

No Miller Effect

$\tau_1$  decreases

↳ better frequency response !!

④ we use cascode structure  
for high frequency design,  
or it eliminates Miller  
Effect for RF Amps.


⑤ what are we trading  
off for this?

→ Extra transistor mean)  
that output voltage swing  
decreases. we can lower


$V_{out}$  to  $V_{DS1} + V_{DS2}$   
In common source it would  
be  $V_{DS1} \rightarrow (V_{GS1} - V_{T1})$



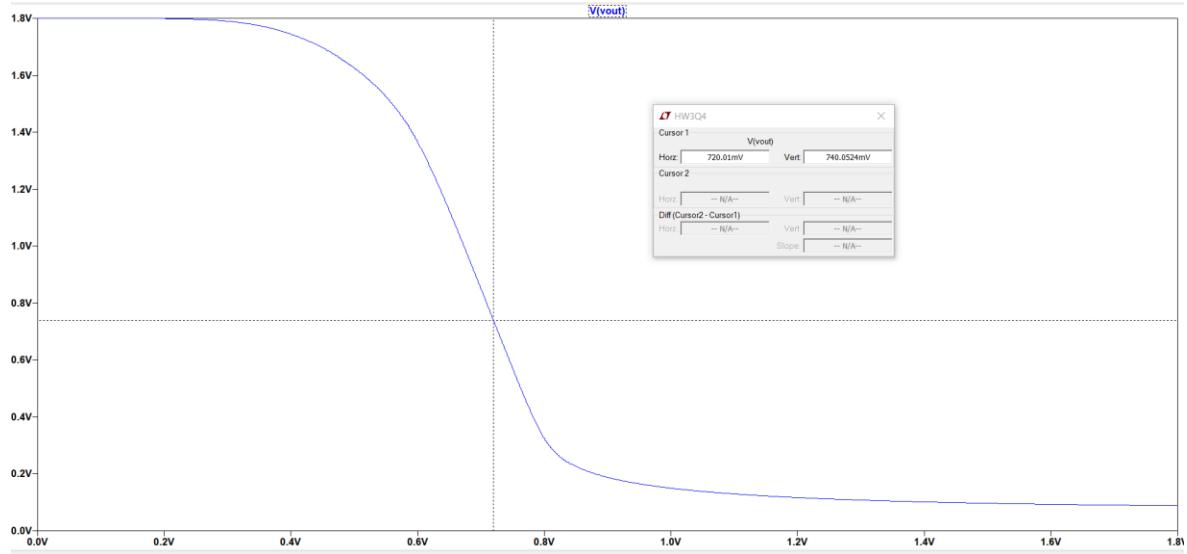
4) In the first part, we need to bias the circuit such that  $V_{OUT}=0.74V$  @ DC. Thus, we sweep the gate of  $M_{13}$ , with a DC voltage source to obtain this value.



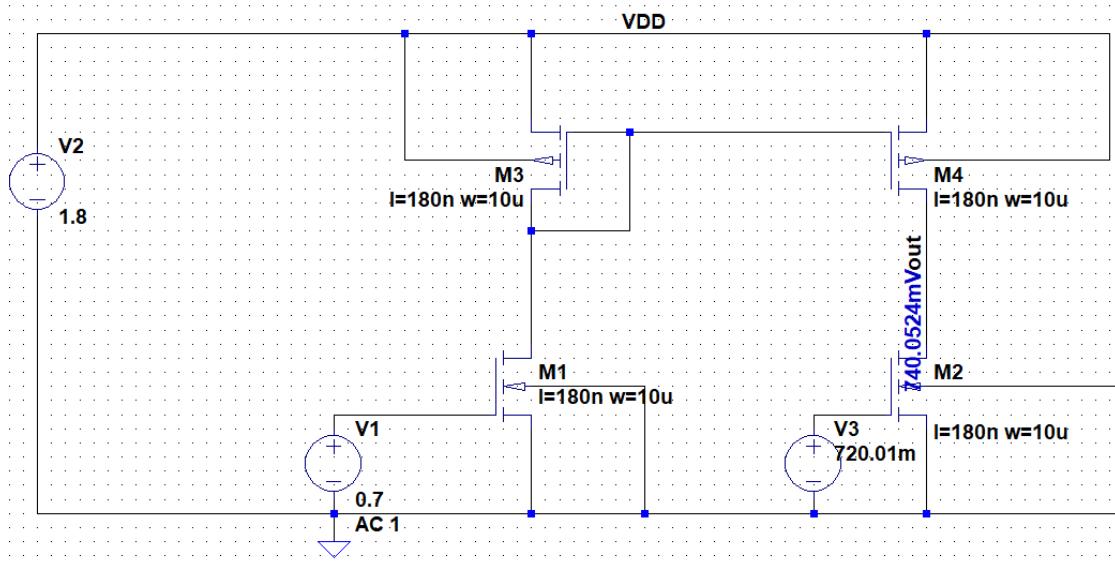The DC bias voltage value of  $V_{G13}=720.01$  mV. After applying this bias voltage the DC operating point of the output can be seen below.



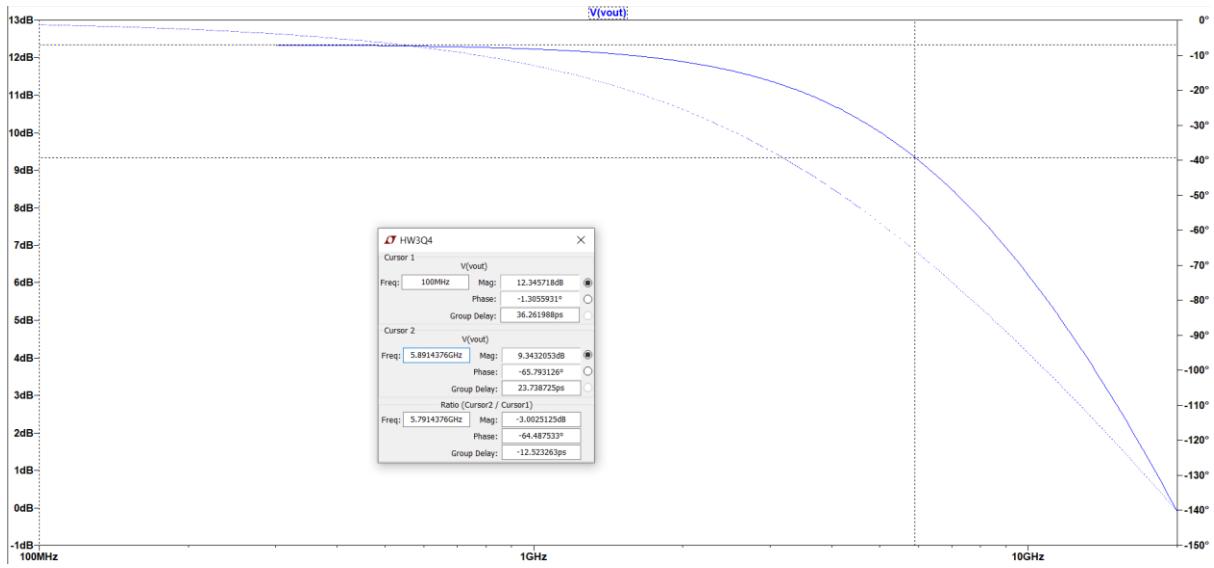You can see the frequency response of the amplifier on the next page. The low frequency gain is equal to 12.34 dB and the 3 dB frequency is equal to 5.9 GHz. You can observe that the phase shift is equal to 65 degree. Normally, we would expect 45 degree for a single dominant pole but it is not the case for this amplifier.



## Possible Mistakes

- Importing wrong models.
- Forgetting to enter the transistor geometry.
- Wrong DC biasing.
- Connecting bulk connections to the wrong nodes (It should be VDD for PMOS, ground for NMOS).
- Forgetting to apply AC signal from the input.
- Forgetting to apply power supply.

## Notes

- For MOS the terminals drain and source do not matter. Remember that MOSFET is a symmetrical device.
- Transistor width and length are the design parameters for MOSFET. You should not include it to the model. It should be the designer's choice.
- The biasing method in the question is not a good choice. Biasing with the voltage sources are called as bad design. You are going to learn biasing with current sources in more advanced classes. It is always problem to bias single ended input circuits without using coupling capacitors.