

Y.E.

$$P1) \beta_{F_1} = g_{m1} \cdot r_{ac1} = 10mS \cdot 10k = \underline{\underline{100}}$$

$$r_{ai_1} = 100 \cdot \left(\frac{1}{g_{m1}} + r_{ce} \right) = 20k$$

$$V_{a1} = V_u \frac{20k//10k}{20k//10k + 5k} = 0,57V_k$$

$$\frac{V_{b1}}{V_{a1}} = - \frac{g_{m1} \cdot (100k//2k//r_{ai2})}{1 + g_{m1} \cdot (0,1k)} \quad r_{ai2} = \beta_{F_2} \cdot \frac{1}{g_{m2}} = \underline{\underline{2k}}$$

$$g_{m2} = \frac{20}{5k} = 4mS \quad \beta_{F_2} = \underline{\underline{8}}$$

$$\frac{V_{b1}}{V_{a1}} = - \frac{10m \cdot 0,99k}{1 + 10m \cdot 0,1k} = - \underline{\underline{4,95}}$$

$$V_{b1} = -2,92 V_k = V_{a2}$$

$$i_o = \frac{2,92 \cdot V_k \cdot 20}{10k} \rightarrow \frac{i_o}{V_k} = - \underline{\underline{564mS}}$$

M. E.

2) $\beta_N = \beta_P = 100 \mu \cdot 20 = 2 \text{ mA}/\sqrt{2}$

$$I_{DN} = \frac{\beta_N}{2} \cdot (V_{GS} - V_{Th})^2 \cdot \left(1 + \frac{V_{DS}}{V_A}\right)^0$$

$$1 \text{ mA} = 1 \text{ mA} \cdot (V_{GS} - (-1,5) - 0,5)^2 \cdot \left(1 + \frac{V_{DS} + 1,5}{V_A}\right)$$

$$1 = V_{GS} + 1 \rightarrow \underline{V_{GS} = 0 \text{ V}} = V_{GGN}$$

$$I_{DP} = \frac{\beta_P}{2} (V_{GS} - V_{Th})^2 \cdot \left(1 + \frac{V_{DS}}{V_A}\right)^0$$

$$1 \text{ mA} = 1 \text{ mA} \cdot (V_{GGP} - 5 - (-0,5))^2$$

$$1 = V_{GGP} - 4,5 \rightarrow \underline{V_{GGP} = 5,5 \text{ V}}$$

b) $V_{i2} = 0$

$$\frac{V_o}{V_{i1}} = \frac{V_{dN}}{V_{SN}} = \left(g_{mN} + \frac{1}{r_{dsN}} \right) \cdot (r_{dsN} \parallel r_{dsp})$$

$$g_{mN} = g_{mp} = \sqrt{2 \cdot \beta_N \cdot I_o} = 2 \text{ mS}$$

$$r_{dsN} = r_{dsp} = \frac{40 \text{ V}}{I_o} = 40 \text{ k}\Omega$$

$$\frac{V_o}{V_{i1}} = (2 \text{ m} + 0,025 \text{ m}) \cdot (20 \text{ k}\Omega) \cong 40$$

$V_{i1} = 0$

$$\frac{V_o}{V_{i2}} = \frac{V_{dp}}{V_{gp}} = - g_{mp} \cdot (r_{dsN} \parallel r_{dsp})$$


J. E.

$$\frac{V_o}{V_{in}} = -2 \cdot 20k = -40$$

Superposition $\rightarrow V_o = 40 \cdot V_{ic} - 40 \cdot v_{in}$

$$A_d = \frac{V_o}{V_{ic} - V_{in}} = 40$$

c)

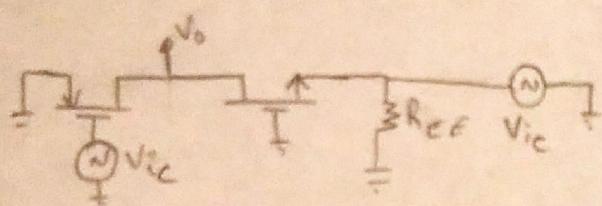

$$R_{EE} = \frac{-1,5 + 5}{1mA} = 3,5 k\Omega$$


$$V_o = 40 \cdot V_{ic} - 40 \cdot v_{in} = 0 \rightarrow A_c = 0$$

$$CMRR = \left| \frac{A_d}{A_c} \right| = \infty$$

M.C.

P3) $V_o = V_i$:

a)

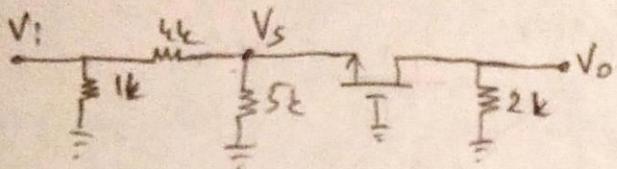

$$V_s = 5 \cdot \frac{5}{9} - 5 = -2,22 \quad I_0 = \frac{-2,22 + 5}{5\text{k}} = 0,56 \text{ mA}$$

$$g_m = \sqrt{2 \cdot \beta \cdot I_0} = \sqrt{2 \cdot 4 \cdot 10^{-2} \cdot 10^{-3}} = 2,11 \text{ mS}$$

$$\frac{V_o}{V_i} = \frac{5}{9} \cdot g_m \cdot 2\text{k} = \underline{\underline{2,34}}$$

b) $V_o < 5\text{V} \rightarrow \text{Max } V_i \approx 2,13\text{V}$

c)

My C

$$p6) V_{o1} = 10V = V_{ee} \rightarrow V_p = 10 \cdot \frac{1}{5} = 2V$$

$$V_{o1} = -10V = V_{ee} \rightarrow V_p = -2V$$

$$\underline{V_m > 2V \rightarrow V_{o1} = -10V}$$


$$V_p = -10 \cdot \frac{1}{5} = -2V \rightarrow \frac{V_m + 2}{1k} = \frac{-2 - V_{out}}{2k}$$

$$2V_m + 4 = -2 - V_{out} \rightarrow \boxed{V_{out} = -2V_m - 6}$$

$$\underline{V_m < -2V \rightarrow V_{o1} = 10V}$$

$$V_p = 2V \rightarrow \frac{V_m - 2}{1k} = \frac{2 - V_{out}}{2k}$$
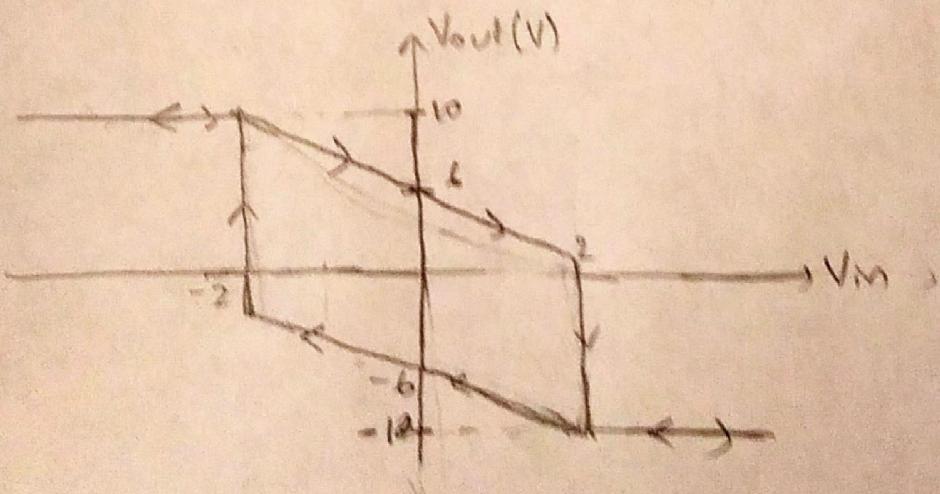
$$2V_m - 4 = 2 - V_{out} \rightarrow \boxed{V_{out} = 2V_m + 6}$$



$\gamma \in .$

p5) $V_{D1} = 10V \quad V_H^+ = 2V \quad V_H^- = -2V$

$V_{out} > V_H^+ \rightarrow V_{D1} = -10V$

$$V_P = -10 \cdot \frac{1}{5} = -2V = V_N$$

$$\frac{V_M + 2}{1k} = \frac{-2 - V_{out}}{2k} \quad V_{out} = -2V_m - 6$$

$V_{out} < V_H^- \rightarrow V_{D1} = 10V$

$$V_P = 2V = V_N$$

$$\frac{V_M - 2}{1k} = \frac{2 - V_{out}}{2k} \quad V_{out} = -2V_m + 6$$