
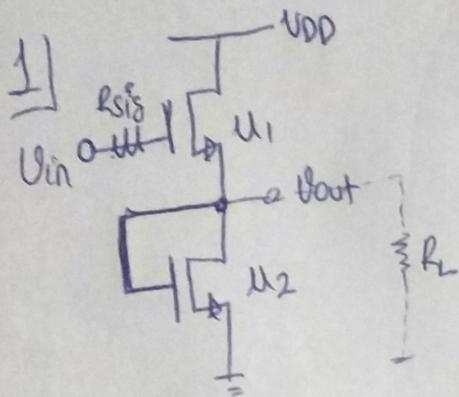


HW3 - 2020


Serden Saif Eranit
040170025

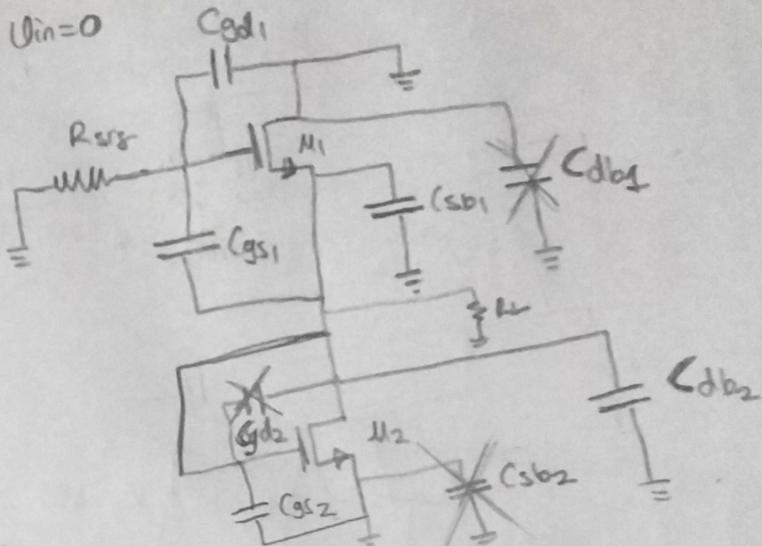

$$1) \text{ } U_{in} = 0$$




2) Remove redundancies

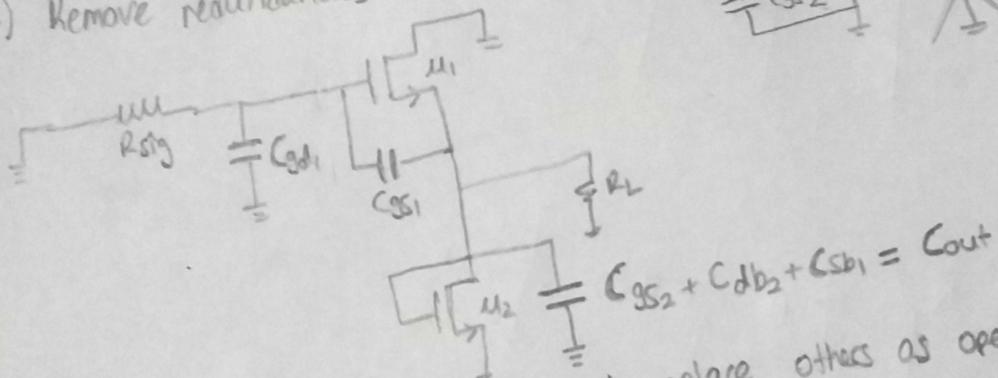


3) Consider one capacitor at time and replace others as open circuit.

For C_{gd1}

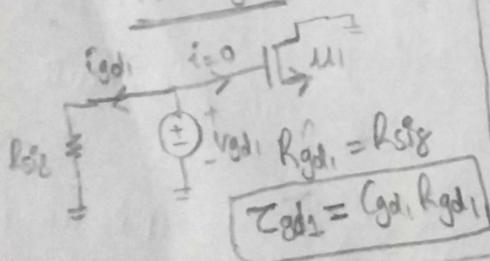

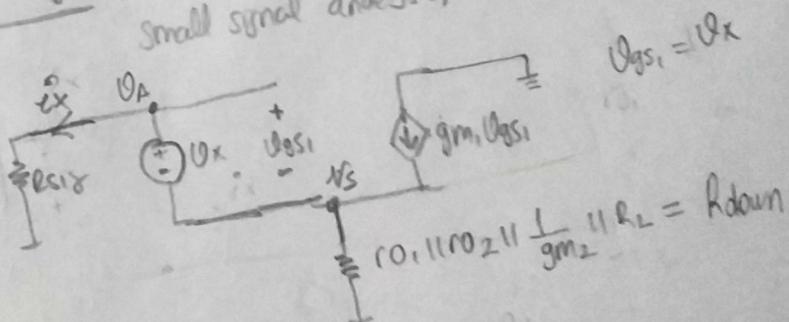For C_{gs1} (Since it is a floating capacitor we need to do small signal analysis)



$$U_s = (gm_1 U_x - ix) R_{down}$$

$$ix R_{sig} - U_x = gm_1 U_x R_{down} - ix R_{down}$$


$$U_x (1 + gm_1 R_{down}) = ix (R_{sig} + R_{down})$$

$$\frac{U_x}{ix} = R_{gs1} = \frac{R_{sig} + R_{down}}{1 + gm_1 R_{down}}$$

$$\Rightarrow R_{gs1} = \frac{R_{sig} + (r_o1 || r_o2 || \frac{1}{gm_2} || R_L)}{1 + gm_1 (r_o1 || r_o2 || \frac{1}{gm_2} || R_L)}$$

$$- Z_{gs1} = C_{gs1} R_{gs1}$$

For C_{out}

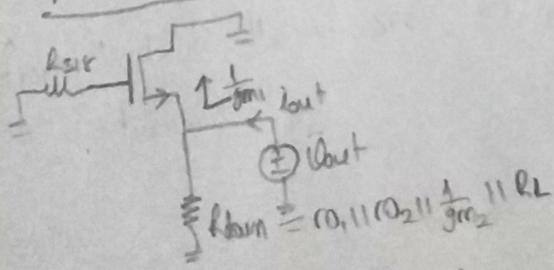


$$R_{out} = r_o1 || r_o2 || \frac{1}{gm_1} || \frac{1}{gm_2} || R_L$$

$$Z_{out} = C_{out} R_{out}$$


Then according to open-circuit time constant methodology.

$$f_{3-\text{dB}} = \frac{1}{\sum_{i=1}^3 Z_i} = \frac{1}{(Z_{\text{out}} + Z_{gss} + Z_{gdd})2\pi}$$

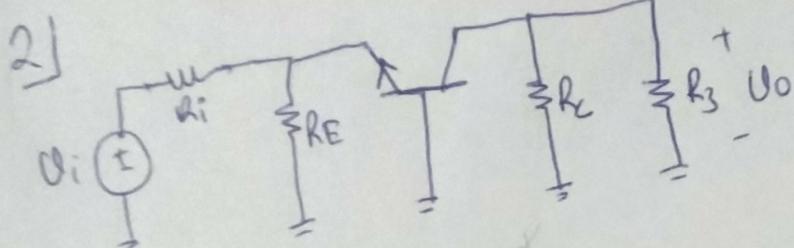
$$f_{3-\text{dB}} = \frac{1}{2\pi(C_{\text{out}}R_{\text{out}} + C_{gss}R_{gss} + C_{gdd}R_{gdd})}$$



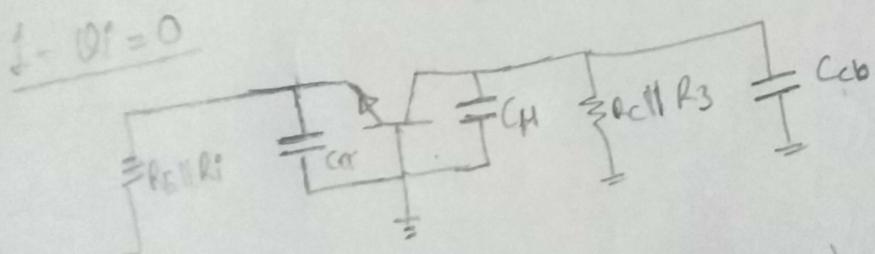Since C_1 and C_2 are coupling capacitors, at high frequencies, they becomes short circuit.



For C_{π}

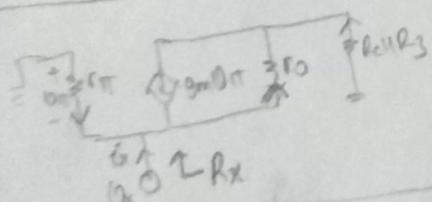

$$\theta_x - \left(ix + \frac{\theta_I}{r_{\pi}} + g_m \theta_I \right) r_o - \left(ix + \frac{\theta_I}{r_{\pi}} \right) (R_c || R_3) = 0$$

$$\theta_x - \left(ix - \frac{\theta_I}{r_{\pi}} - g_m \theta_I \right) r_o - \left(ix - \frac{\theta_I}{r_{\pi}} \right) (R_c || R_3) = 0$$

$$\theta_x - \frac{r_o + (R_c || R_3)}{r_o + (R_c || R_3)} - ix(r_o + R_c || R_3) = 0$$

$$r_o + (R_c || R_3) = \frac{r_o + (R_c || R_3)r_{\pi}}{r_o + g_m r_{\pi} r_o + (R_c || R_3)r_{\pi}}$$

For $C_{\mu} + C_{cb}$

$$\Rightarrow R_d = r_o + (R_c || R_E || r_{\pi}) + g_m r_o (R_c || R_E || r_{\pi})$$

$$R_{\mu} = R_d || R_c || R_3 \times R_c || R_3 || (g_m r_o (R_c || R_E || r_{\pi}))$$


$$Z_{\mu} = (C_{\mu} + C_{cb}) [R_c || R_3 || (g_m r_o (R_c || R_E || r_{\pi}))]$$

$$R_x = \frac{r_o + g_m r_o + R_c || R_3}{(B+1)r_o + (R_c || R_3)}$$


$$R_{\pi} = R_x || R_E || R_i \Rightarrow R_{\pi} = R_x || R_E || R_i$$

$$Z_{\pi} = C_{\pi} R_{\pi} = C_{\pi} (R_x || R_E || R_i)$$
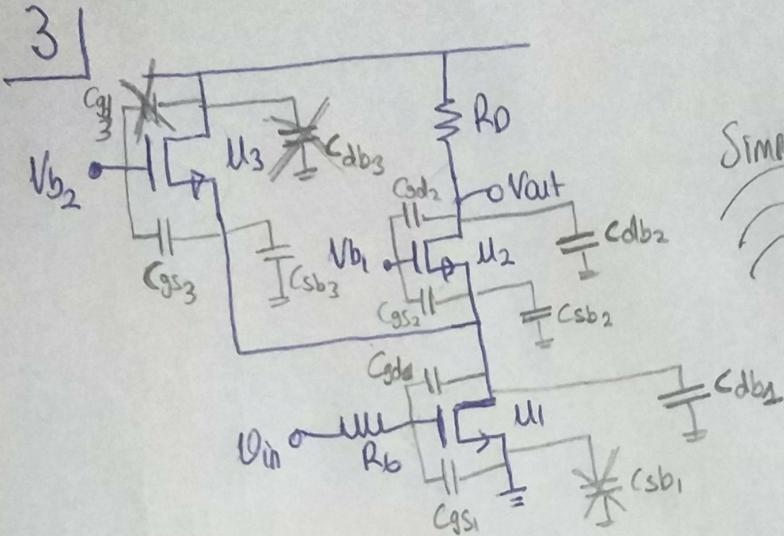
$$f_{3-\text{dB}} = \frac{1}{2\pi(C_{\mu} + C_{\pi})}$$





Simplify

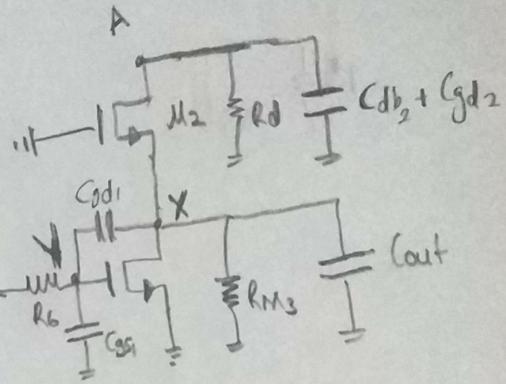

Where

$$C_{out} = C_{db1} + C_{gs2} + C_{sb2} + C_{gs3} + C_{sb3}$$

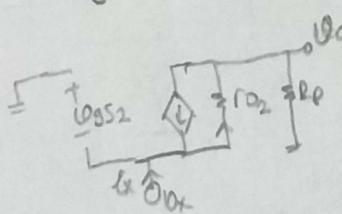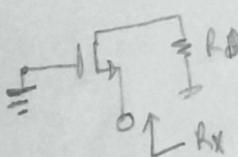There is only one floating capacitor, C_{d1} , and since we're asked to apply Miller's approximation, we need to calculate the DC gain between the terminals at C_{d1} . In order to find DC gain we need to find R_{out} for which V_{out} is taken from the source of M_1 .




$$V_x - (i_x + g_m 2 V_{gs2}) R_o - i_x R_o = 0$$

$$(V_x (1 + g_m 2 R_o)) = i_x (R_o + R_o) \quad \leftarrow 10x$$

$$R_x = \frac{V_x}{i_x} = \frac{R_o + R_o}{1 + g_m 2 R_o} = \frac{(1/g_m 2)(R_o + R_o)}{\frac{1}{g_m 2} + R_o}$$
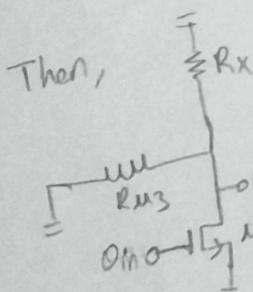
$$R_x \approx \frac{R_o + R_o}{g_m 2 R_o} \quad (\text{since } R_o \gg \frac{1}{g_m 2})$$



$$6m = g_m 2$$

$$R_{out} = R_x \parallel R_{ds3} \parallel R_o$$


$$R_{out} = \left(\frac{R_o + R_o}{g_m 2 R_o} \right) \parallel \left(\frac{1}{g_m 3} \parallel R_o \right) \parallel R_o$$

$$A_v = g_m 1 \left[\left(\frac{R_o + R_o}{g_m 2 R_o} \right) \parallel \left(\frac{1}{g_m 3} \parallel R_o \right) \parallel R_o \right]$$

DC gain between the terminals at the floating capacitor is $A_v = 6m R_{out}$

Now we separate C_{d1} into two standard capacitors by using Miller's theorem.

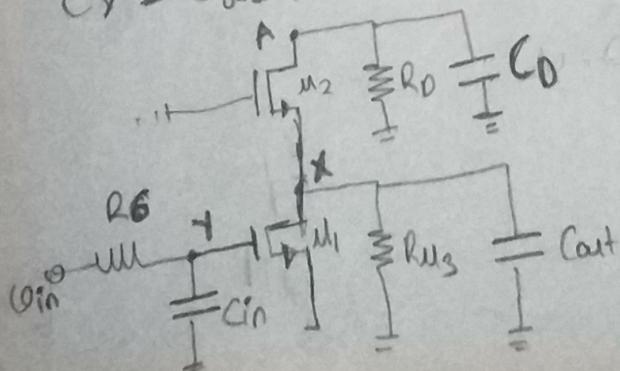$C_y = C_{d1} (1 + A_v)$; $C_x = C_{d1} \left(1 + \frac{1}{A_v} \right)$, and draw the new model




where

$$C_0 = C_{db2} + C_{db3}$$

$$C_{in} = C_y + C_{gs1}$$

$$C_{out} = C_x + C_{db1} + C_{gs2} + C_{sb2} + C_{gs3} + C_{sb3}$$

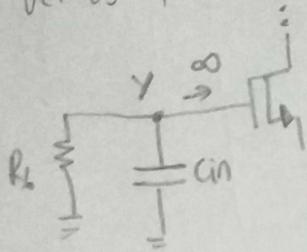Now, we obtained the model that we can apply the pole identification on let us first examine input pole which stems from the capacitor C_{in}




$$R_y = R_6$$

$$Z_y = C_{in} R_6$$

$$f_{in} = \frac{1}{2\pi C_{in} R_6}$$

Then, examine C_{out}
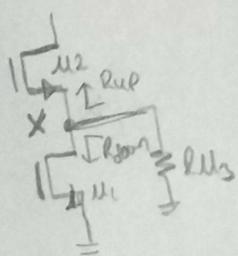
$$\text{we have found that } R_{up} \approx \frac{r_{O2} + R_0}{g_{m2} r_{O2}}$$




$$\text{and we know } R_{down} = r_{O1}$$

$$\text{Then } R_x = R_{M3} \parallel R_{up} \parallel R_{down}$$

$$\Rightarrow R_x = \left(\frac{1}{g_{m3}} \parallel r_{O3} \right) \parallel \left(\frac{r_{O2} + R_0}{g_{m2} r_{O2}} \right) \parallel r_{O1}$$

$$\Rightarrow Z_x = C_{out} R_x \Rightarrow f_{out} = \frac{1}{2\pi (C_{out} R_x)}$$

Lastly, examine C_{up}

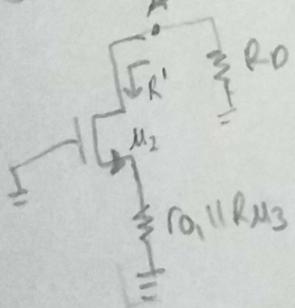

$$R' = r_{O2} + (r_{O1} \parallel R_{M3}) + g_{m2} r_{O2} (r_{O1} \parallel R_{M3})$$

$$R_A = R_0 \parallel R' = R_0 \parallel [r_{O2} + (1 + g_{m2} r_{O2})(r_{O1} \parallel R_{M3})]$$

$$Z_A = R_A C_D$$

$$f_A = \frac{1}{2\pi (R_A C_D)}$$

Node's names

X: Drain at M_1 and Source of M_2

Y: Gate of M_1

A: Drain at M_3

R_{M3} : The resistance seen looking into the source of M_3