

Homework-6 Solutions

Note: I used $k_n = \rho n \cos \frac{\omega}{C}$

$k'_n = \rho n \cos \alpha$, $I_D = \frac{1}{2} k_n (V_{GS} - V_{TH})^2$

notation. Even you use a different notation, I won't downgrade your solution. Do not worry about it.

However, some metrics such as efficiency should be same.



1-a) M₁ behaves as a current source. It operates in saturation region and $V_{DS2} = 0$.

$$I_{D1} = \frac{1}{2} k_n (V_{GS} - V_{TH})^2$$

$$= \frac{1}{2} 1.2mA/V^2 (1.8)^2 V^2$$

$$= 19.44 mA$$

→ For $R_L = \infty$, the max. output voltage depends on θ_1 . θ_1 should not leave the forward operating region.

$$V_{OMAX} = 5V - V_{CESAT\theta_1} = 4.8V$$

V_{Omin} is about M₁. There are two scenarios - 1) M₁ should not leave saturation region.

2) M₁ should sink all the current on R_L.

One of these two factors limits the minimum voltage.

Since R_L = ∞ , it does not have any current. We should check the first scenario.

$$V_{Dm1\ min} = V_{O2} - V_{THM1}$$

$$= 5V - (-1.8V) = 3.2V$$

$$\text{So } \boxed{V_{out\ min} = -3.2V}$$

→ For R_L = 500 Ω

V_{max} is the same as if only depends on O₂.

$$\boxed{V_{max} = 4.8V}$$

Let's check the scenario - 2 for

$$R_L = 0.5 \text{ k}\Omega$$

Question \rightarrow Can M_1 sink all the current which flows through R_L ? $I_{M1} = ?$

$$I_{M1} = 19.44 \text{ mA}$$

\hookrightarrow If all of this current flows through R_L ,

$$V_{R_L} = 0 - 19.44 \text{ mA} \times 0.5 \text{ k}$$

$$= -9.72 \text{ V}$$

\downarrow
we cannot go beyond this voltage, however our limiting factor in scenario - 1 was worse. Thus,

$$\boxed{V_{out \min} = -3.2 \text{ V again!}}$$

1-5) we know that for the positive output voltage we can go up to 4.8V. Thus, the positive peak won't be problematic.

* For the negative side M₁ should sink the current. (should provide the necessary current)

$$V_{out} = -2V = 0 - R_{Lmin} \times \underbrace{19.44 \text{ mA}}_{\text{our constant current on } M_1}$$

$$R_{Lmin} = \frac{2V}{19.44 \text{ mA}} \approx 103 \text{ ohm}$$

→ we cannot use a load resistor smaller than 103 ohm, if we want to -2V output signal at the output!

1-c) For the efficiency,

$$\text{Load Power, } P_L = \frac{\left(\left(V_{\text{out max}}\right)/\sqrt{2}\right)^2}{R_L}$$

$$V_{\text{out max}} = 2 \text{ V}$$

$$P_L = \frac{\left(2/\sqrt{2}\right)^2}{R_L} \approx 19.4 \text{ mW}$$


⇒ The rms voltage is $V_{\text{peak}}/\sqrt{2}$
what is supply power?

From negative supply, we are consuming
constant M_s current 19.66 mA.

$$P_S (\text{from } -5V) = 19.66 \text{ mA} \times 5V = 97.2 \text{ mW}$$

↓
the current consumption for
positive supply

Let's plot the graph

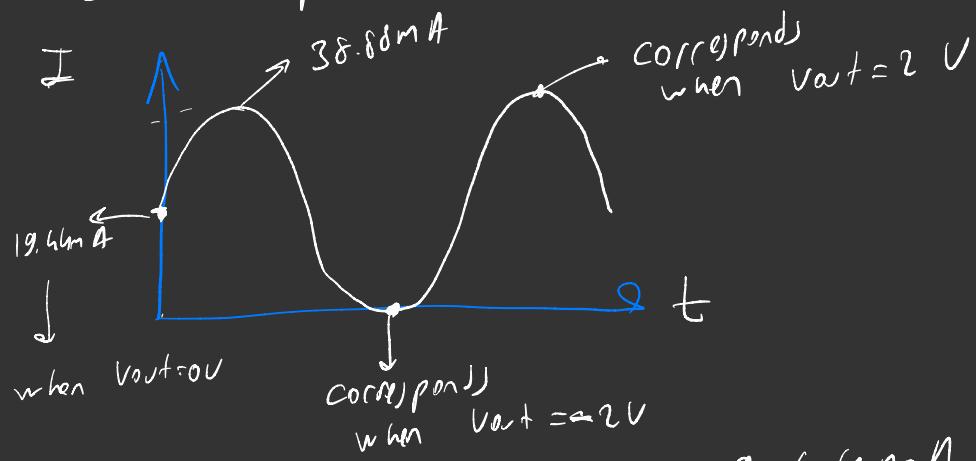

$$\text{Average current} = 19.6 \text{ mA}$$

thus,

$$P_S (\text{from } 5V) = 97.2 \text{ mW} \text{ (also)}$$

Total power consumption from supply

$$P_{S \text{ TOTAL}} = 194.4 \text{ mW}$$

$$\eta = \frac{\text{Load Power}}{\text{Supply power}} = \frac{19.6 \text{ mW}}{194.4 \text{ mW}} \approx 0.10$$

2) The question is a little bit tricky.

a) For $V_i = 0$, $V_{E\theta_1} = 0.7V$,

$$V_{E\theta_1} = V_{B\theta_3}$$

$$V_o = V_{B\theta_3} - V_{B\theta_2} = 0V$$

$$I_R = 0A$$

so $I_{E\theta_3} = I_{E\theta_4}$

The transistors are matched and if they have the same V_{BE} , they also should have the same current, in quiescent conditions.

Then, $I_{E\theta_3} = I_{E\theta_2}$

$$I_{E\theta_1} = I_{E\theta_2}$$

Since $I_{E\theta_3} = I_{E\theta_4}$

$$\rightarrow I_{E\theta_1} = I_{E\theta_2} = I_{E\theta_3} = I_{E\theta_4}$$

$$I_{R1} = \frac{V^+ - V_{BE3}}{R_1} = \frac{12 - 0.7}{250} = 45.2 \text{ mA}$$

$$I_{B3} + I_{E1} = 45.2 \text{ mA}$$

$$\beta = 50 \quad (I_B = I_B1 = I_B2 = I_B3 - I_E1)$$

$$\frac{I_{E1}}{41} + I_{E1} = 45.2 \text{ mA}$$

$$I_{E1} = 44.1 \text{ mA}$$

$$I_{B3} = 1.1 \text{ mA}$$

$$I_{E1} = I_{E2} = 44.1 \text{ mA} = 2E3 = I_{E4}$$

$$I_{B1} = I_{B2} = 1.1 \text{ mA} = I_{B3} = I_B$$

Observe that for class AB operation, output stage quiescent currents are not zero as opposite of class B!

2-b) For $V_i = 5V$, we can neglect the current of O_4 since it will be much smaller than O_3 .


V_o will track V_i due to O_1, O_3 configuration, thus

$$V_i = 5V = V_o, i_o = \frac{5V}{8\Omega} = 0.625A$$

All of this current through R_L , will be provided by O_3 , thus

$$I_{E3} = 0.625A, I_{B3} = 25.25mA$$



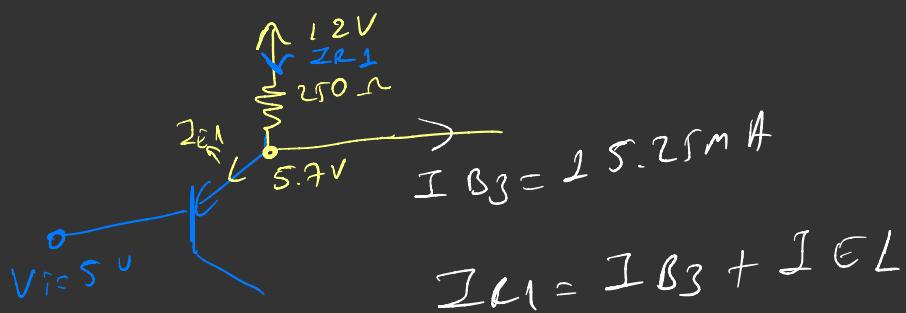

$$I_{R1} = \frac{12V - 5.7V}{250} = 15.2 \text{ mA} + I_{E1}$$

$$I_{E1} \approx 10 \text{ mA}, \quad I_{B1} \approx 24.4 \mu\text{A}$$

Since $I_{Q4} \approx 0$, $I_{B24} \approx 0$


All of the current through R_2

flows from I_{E2} ,

$$I_{E2} = I_{R2} = \frac{(4.3V) - (-12V)}{250 \Omega} = 65.2 \text{ mA}$$

$$I_{B2} = \frac{65.2 \text{ mA}}{n_L} \approx 1.59 \text{ mA}$$

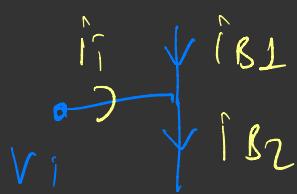So what is the current drawn from the V_i ?



$$\begin{aligned}i_O &= i_{B2} - i_{B1} \\&= 1.59mA - 0.24mA \\&= \underline{\underline{1.346mA}}\end{aligned}$$

Notes for 2-b

- The exact solution should be employed using exponential equation, however it is so complicated, this solution is not exact but gives what we need.

2-c) Current gain = $\left[\frac{i_O}{i_I} = \frac{625mA}{1.346mA} \approx 464 \frac{A}{A} \right]$

$$3) \text{ a) } V_i = V_{62} = -1.5 \text{ V}$$

$$V_0 = V_{52} = 0 \text{ V}$$

$$\text{so } V_{652} = -1.5 \text{ V}$$

$$I_{D2} = \frac{1}{2} k' \rho \frac{W}{L_2} \left(|V_{62}| - |V_{TH2}| \right)^2$$

$$0.5 \text{ mA} = \frac{1}{2} 40 \frac{\mu A}{V^2} \cdot \left(\frac{W}{L_2} \right) (0.7)^2 \cancel{V^2}$$

$$\boxed{\frac{W}{L_2} = \frac{500 \times 2}{40 \times 0.49} \approx 51}$$

$$V_{651} = |V_{652}| = 1.5 \text{ V}, \text{ thus}$$

$$V_{61} = V_{63} = 1.5 \text{ V}, V_{653} = |V_{654}|$$

$$V_{63} - V_{653} - |V_{654}| = V_I = -1.5 \text{ V}$$

$$\text{so } V_{653} = |V_{654}| = 1.5 \text{ V}$$

$$\frac{\frac{w}{L} (1)}{\frac{w}{L} (2)} = \frac{k' p}{k' n}$$

(since I_D and V_{GS} are the same)

$$\boxed{\frac{w}{L} 1 = 20.4}$$

$$\Rightarrow \text{Since } V_{GS1} = V_{GS2} (= V_{GS3} = V_{GS4})$$

we easily can find $\frac{w}{L} (3)$ and $\frac{w}{L} (4)$

$$\frac{\frac{w}{L} (3)}{\frac{w}{L} (2)} = \frac{I_{D(A)}}{I_{D(L)}} = \frac{0.2 \text{ mA}}{0.5 \text{ mA}} = \frac{2}{5}$$

$$\boxed{\frac{w}{L} 3 = 8.16}$$

$$\frac{\frac{w}{L} (4)}{\frac{w}{L} (2)} = \frac{I_{D(A)}}{I_{D2}} = \frac{2}{5}, \quad \boxed{\frac{w}{L} 4 = 20.4}$$

$$3-5) V_{OMAX} = \min \left[(V^+ - V_{OUI}), V_{GS1} \right]$$

since $V_{GS} < V^+$ and $V_{OUI} < V_{GS1}$


The worst case scenario

$$V_{OMAX} = V_{GS} - V_{GS1}$$

$$= 10V - \underbrace{0.2V}_{\substack{\text{voltage} \\ \text{drop on} \\ Z_{EIA}}} - V_{GS1} = 8.3V$$

- ⊕ It is not the exact result, as
- ⊕ while V_O increases I_{L1} will increase and V_{GS1} will decrease and I_{D1} will increase.
- ⊕ However, we can assume V_{GS} is constant for a quick observation.

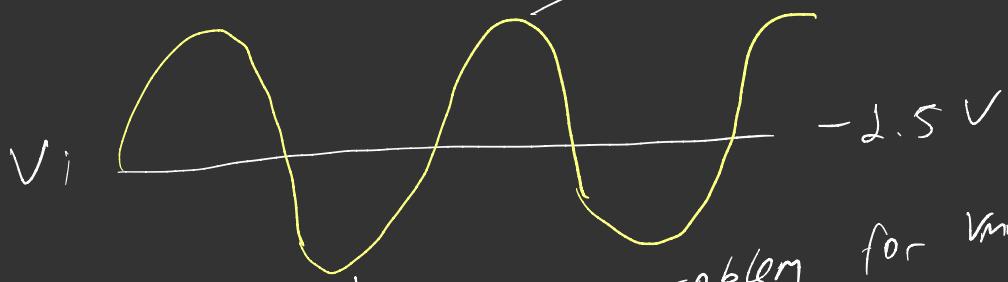For minimum V_i as given V_{out} let's be low, for assume this is problem for V_{min}



\rightarrow this is problem for V_{min}

when we decrease V_i , there is no problem for M_1 as it always operates at saturation region. However, M_2 may leave the saturation region.

$$V_{G2} - V_{THP} \geq -10V$$

$$V_{G2} > -10.8V$$

$$V_{G2} > -9.3V$$

$$\boxed{V_{G2mn} = -9.3V}$$

Important Note


For the positive side $I_{B(A)}$ limits our operation. It is a current source and should not leave saturation. This is why we cannot go beyond 9.8V at V_{BE} . However, for the negative side, there is nothing which limits us except M_2 transistor.

Good luck for the


exam

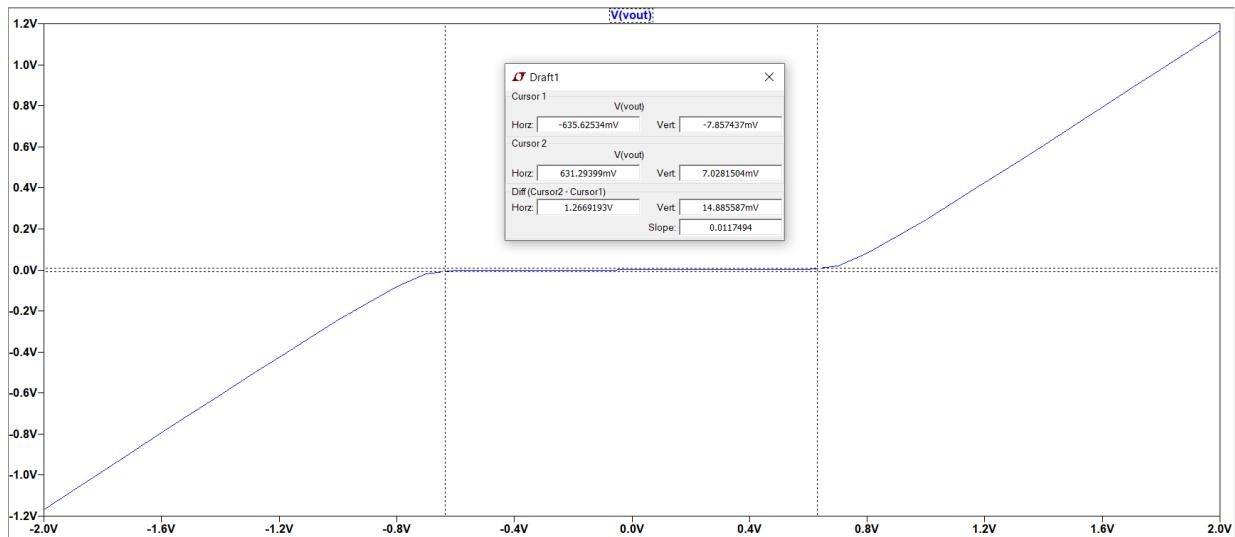QUESTION 4 (LT-SPICE)


For the transfer characteristic, you need to complete DC sweep simulation between -2V and 2V. You can see it below. The dead-zone is between -630 mV and 630 mV, which is an expected result. Please zoom to the plots.



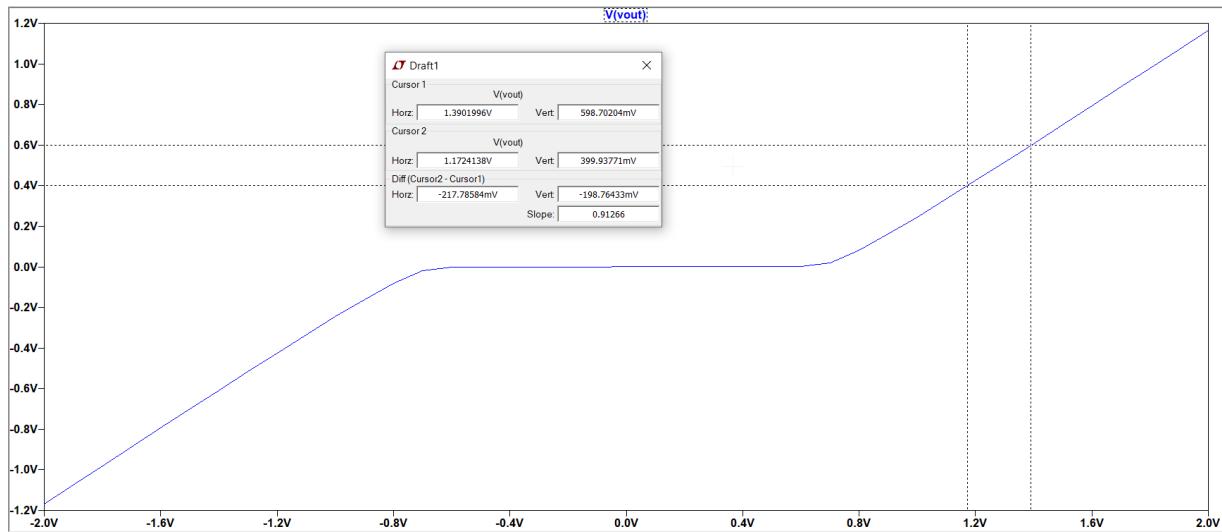
You can observe the slope for the gain, which is equal to 0.91 V/V as given below.




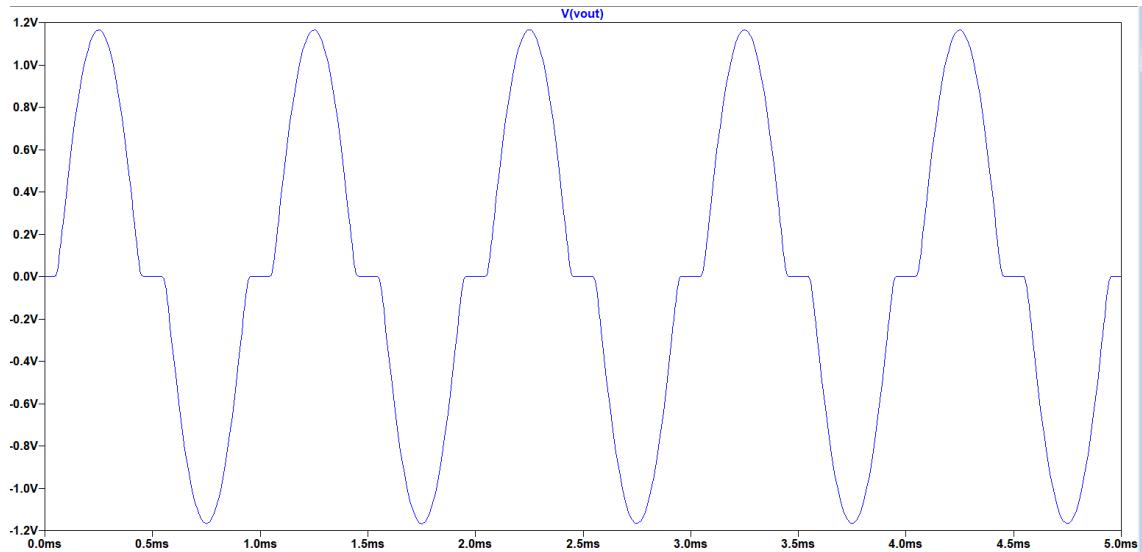When you apply a sinusoidal signal with 2V peak voltage (you should choose a frequency) with 1 kHz (you can choose another appropriate frequency) you can observe the output and cross-over distortion, which is expected from a class B output stage.



For 16 ohm load resistance, you won't see any reasonable change in DC transfer characteristics and transient analysis. However, if you zoom to the maximum output levels, for 8 ohm it is around 1.16V whereas for 16 ohm it is around 1.2V. Let's plot the output current waveforms for 2 different load resistance value. The peak current for 8 ohm load is equal to 145 mA whereas it is equal to 75 mA for 16 ohm load. This is why the output voltage levels are different from each other. V_{BE} value of the transistors is depend on the current value!. You would observe more dramatic change if you increase the difference of the load resistors.

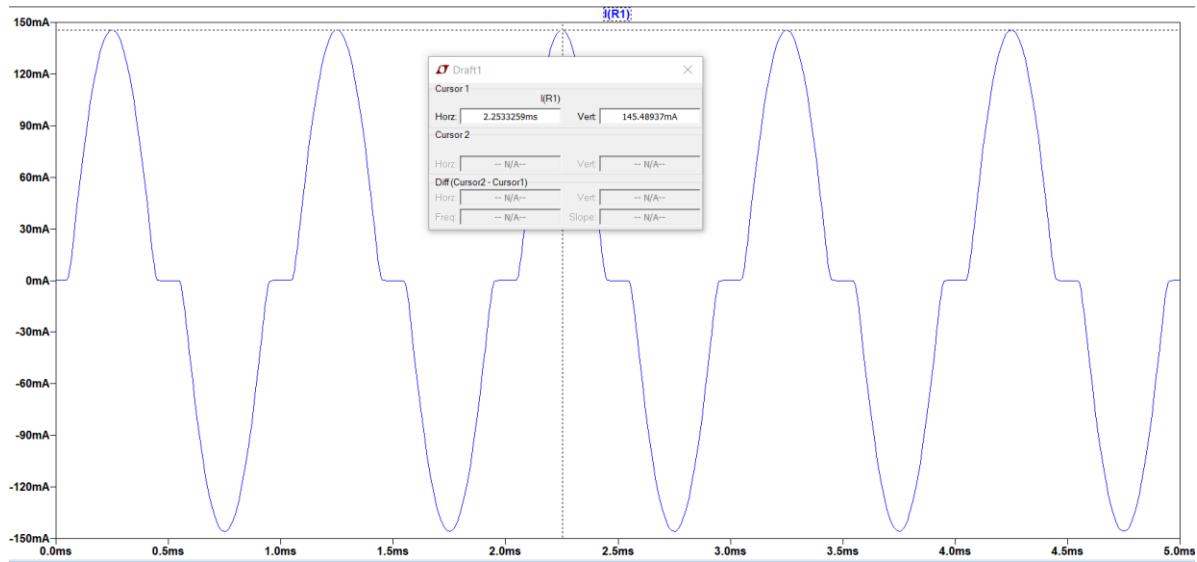

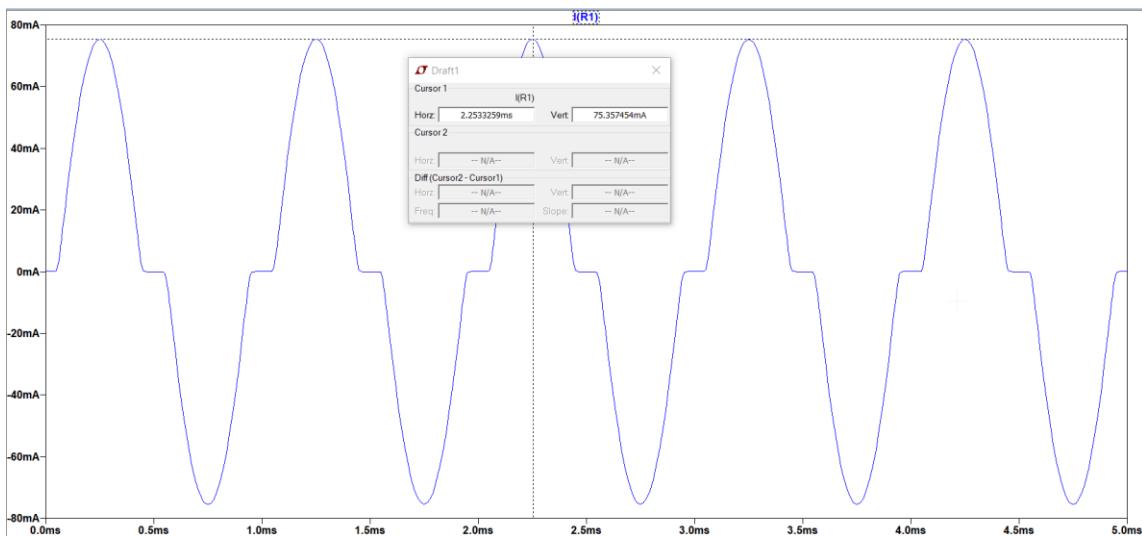

Important note: Observe the maximum output voltages. They are equal to $(2V - V_{B_{enpn}})$ or $(-2V + |V_{B_{epnp}}|)$ instead of 2V and -2V.