



– EHB 335E – ANALOG ELECTRONICS – 11219 –




SERDEN SAIT ERANIL
040170025

HW3 - 2020

Serdan Salt Frat
040170025

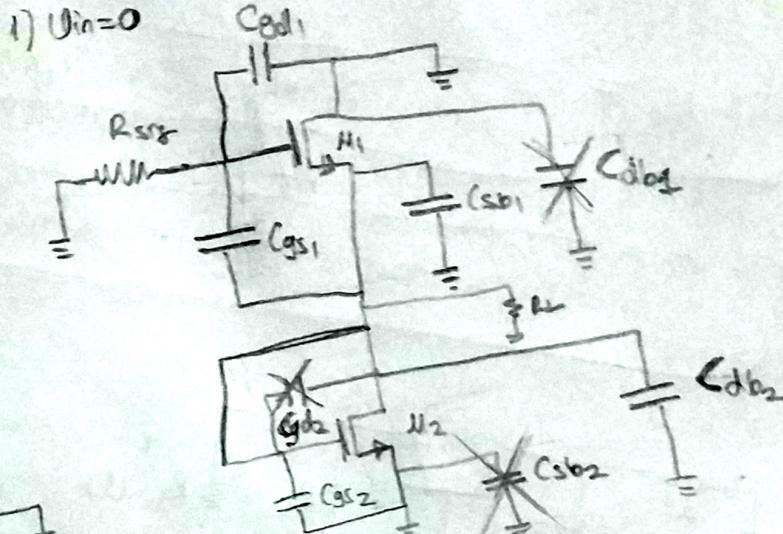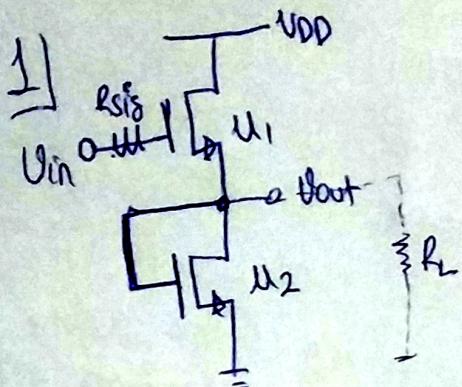

2) Remove redundancies

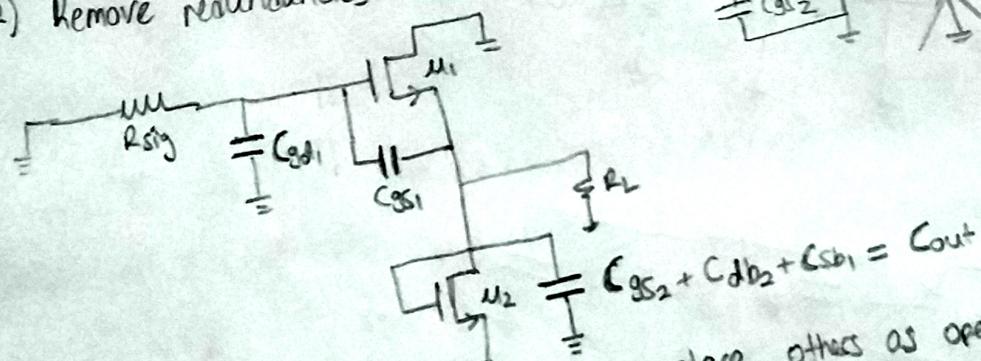

3) Consider one capacitor at time and replace others as open circuit.

For C_{gd1}

$$R_{gd1} = R_{sig}$$

$$Z_{gd1} = C_{gd1} R_{gd1}$$

For C_{gs1} (Since it is a floating capacitor we need to do small signal analysis)

$$V_{gs1} = V_x$$

$$i_S = (g_m V_x - i_x) R_{down}$$

$$i_x R_{sig} - V_x = g_m V_x R_{down} - i_x R_{down}$$

$$V_x (1 + g_m R_{down}) = i_x (R_{sig} + R_{down})$$

$$\frac{V_x}{i_x} = R_{gs1} = \frac{R_{sig} + R_{down}}{1 + g_m R_{down}}$$

$$\Rightarrow R_{gs1} = \frac{R_{sig} + (r_o1 || r_o2 || \frac{1}{g_m2} || R_L)}{1 + g_m (r_o1 || r_o2 || \frac{1}{g_m2} || R_L)}$$

For C_{out}

$$R_{out} = r_o1 || r_o2 || \frac{1}{g_m1} || \frac{1}{g_m2} || R_L$$

$$Z_{out} = C_{out} R_{out}$$


$$- Z_{gs1} = C_{gs1} R_{gs1}$$

Then according to open-circuit time constant methodology.

$$f_{3-\text{dB}} = \frac{1}{\sum_{i=1}^3 Z_i} = \frac{1}{(Z_{\text{out}} + Z_{\text{gsi}} + Z_{\text{gd}})2\pi}$$


$$f_{3-\text{dB}} = \frac{1}{2\pi(C_{\text{out}}R_{\text{out}} + C_{\text{gsi}}R_{\text{gsi}} + C_{\text{gd}}R_{\text{gd}})}$$

2)

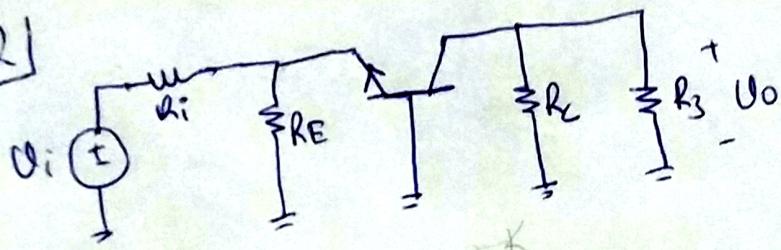


Since C_1 and C_2 are coupling capacitors, at high frequencies, they becomes short circuit.

1) $\text{O}_i = 0$

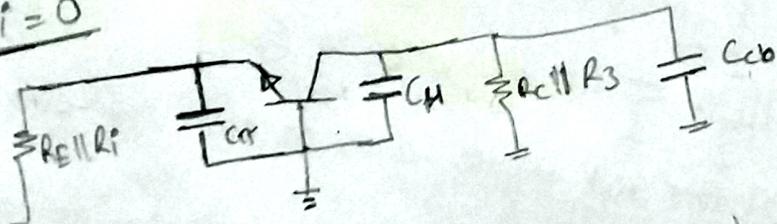

For C_π

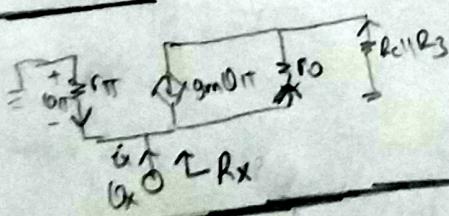

$$\text{O}_x - \left(ix + \frac{\text{O}_i}{r_\pi} + g_m \text{O}_i \right) r_o - \left(ix + \frac{\text{O}_i}{r_\pi} \right) (R_C || R_3) = 0$$

$$\text{O}_x - \left(ix - \frac{\text{O}_x}{r_\pi} - g_m \text{O}_x \right) r_o - \left(ix - \frac{\text{O}_x}{r_\pi} \right) (R_C || R_3) = 0$$


since $(\text{O}_i = -\text{O}_\pi)$ $\Rightarrow \text{O}_x - \left(ix - \frac{\text{O}_x}{r_\pi} - g_m \text{O}_x \right) r_o - \left(ix - \frac{\text{O}_x}{r_\pi} \right) (R_C || R_3) = 0$

$$R_x = \frac{r_o + (R_C || R_3)}{r_o + (R_C || R_3)} = \frac{r_{no} + r_\pi (R_C || R_3)}{r_\pi + r_o + g_m r_o + r_o + (R_C || R_3)}$$

$$R_x = \frac{1 + \frac{r_o}{r_\pi} + g_m r_o + \frac{R_C || R_3}{r_\pi}}{\frac{r_\pi}{r_\pi} (r_o + R_C || R_3)} \Rightarrow R_\pi = R_x || R_E || R_P$$

$$Z_\pi = C_\pi R_\pi = C_\pi (R_x || R_E || R_i)$$

For $C_\mu + C_{cb}$

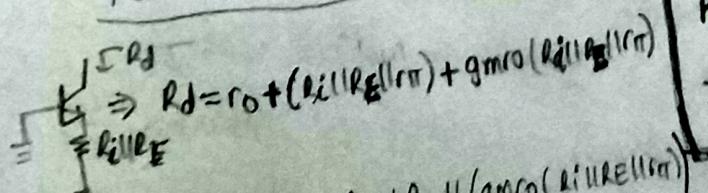


$$R_\mu = R_d + R_C || R_3 \times R_C || R_3 || (g_m r_o (R_E || R_i || r_\mu))$$


$$Z_\mu = (C_\mu + C_{cb}) [R_C || R_3 || (g_m r_o (R_E || R_i || r_\mu))]$$

$$f_{3-\text{dB}} = \frac{1}{2\pi(Z_\mu + Z_\pi)}$$

3

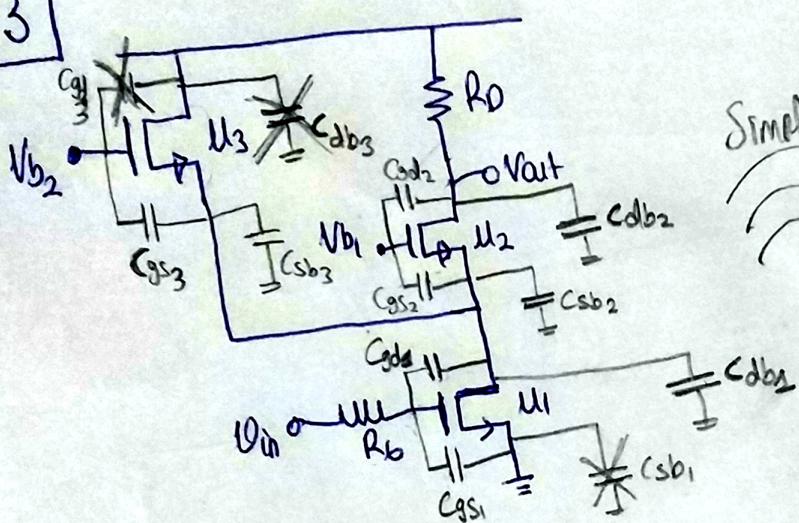

Similitr

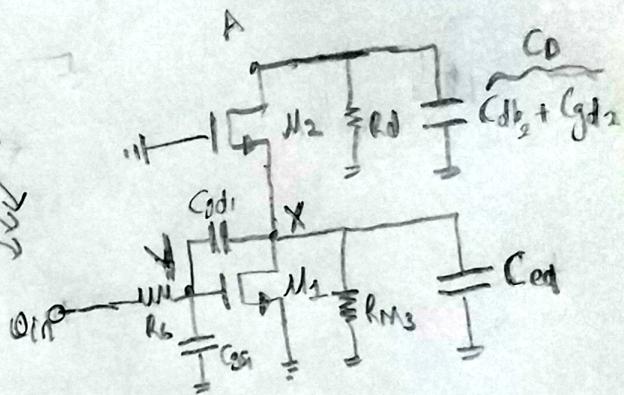



where

$$C_{eq} = C_{db1} + C_{gs2} + C_{sb2} + C_{gs3} + C_{sb3}$$

There is only one floating capacitor, C_{gd1} , and since we're asked to apply Miller's approximation, we need to calculate the DC gain between the terminals at C_{gd1} . (Between the terminals X-X')

In order to find DC gain we need to find R_{out} for which V_{out} is taken from the

drain of M_1 (Node X)

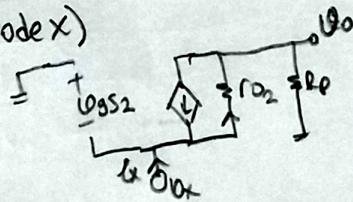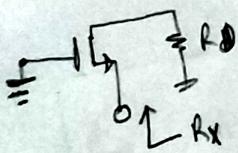


$$V_x - (i_x + g_m 2 V_{GS2}) R_{D2} - i_x R_D = 0$$

$$(V_x (1 + g_m 2 R_{D2})) = i_x (R_{D2} + R_D)$$

$$R_x = \frac{V_x}{i_x} = \frac{R_{D2} + R_D}{1 + g_m 2 R_{D2}} = \frac{(1/g_m 2)(R_{D2} + R_D)}{\frac{1}{g_m 2} + R_{D2}}$$

$$R_x \approx \frac{R_{D2} + R_D}{g_m 2 R_{D2}} \quad (\text{since } R_{D2} \gg \frac{1}{g_m 2})$$

Then,

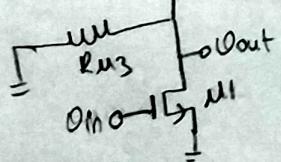

$$6m = g_m 1$$


$$R_{out} = R_x \parallel R_{M3} \parallel R_{D1}$$

$$R_{out} = \left(\frac{R_{D2} + R_D}{g_m 2 R_{D2}} \right) \parallel \left(\frac{1}{g_m 3} \parallel R_{D1} \right) \parallel R_{D1}$$

$$A_v = g_m 1 \left[\left(\frac{R_{D2} + R_D}{g_m 2 R_{D2}} \right) \parallel \left(\frac{1}{g_m 3} \parallel R_{D1} \right) \parallel R_{D1} \right]$$

Now we separate C_{gd1} into two standard capacitors by using Miller's theorem.
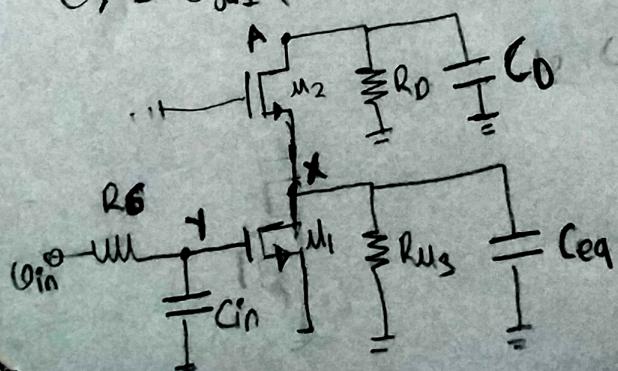
$$C_y = C_{gd1} (1 + A_v) ; C_x = C_{gd1} \left(1 + \frac{1}{A_v} \right), \text{ and draw the new model}$$




where

$$C_D = C_{db2} + C_{gd2}$$

$$C_{in} = C_y + C_{gs1}$$

$$C_{eq} = C_x + C_{db1} + C_{gs2} + C_{sb2} + C_{gs3} + C_{sb3}$$

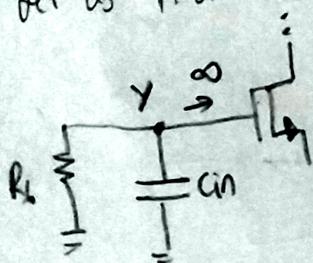Now, we obtained the model that we can apply the pole identification on
let us first examine input pole which stems from the capacitor C_{in}




$$R_y = R_6$$

$$Z_y = C_{in} R_6.$$

$$f_{in} = \frac{1}{2\pi C_{in} R_6}$$

Then, examine C_{eq}

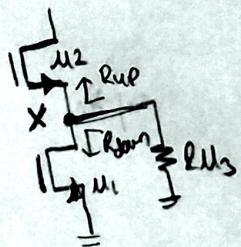we have found that $R_{up} \approx \frac{r_{O2} + R_0}{g_{m2} r_{O2}}$




and we know $R_{down} = r_{O1}$

Then $R_x = R_{M3} \parallel R_{up} \parallel R_{down}$

$$\Rightarrow R_x = \left(\frac{1}{g_{m3}} \parallel r_{O3} \right) \parallel \left(\frac{r_{O2} + R_0}{g_{m2} r_{O2}} \right) \parallel r_{O1}$$

$$\Rightarrow Z_x = C_{eq} R_x \Rightarrow f_{eq} = \frac{1}{2\pi C_{eq} R_x}$$

Lastly, examine C_{up}

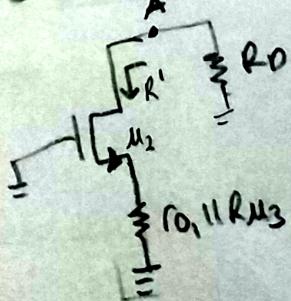

$$R' = r_{O2} + (r_{O1} \parallel R_{M3}) + g_{m2} r_{O2} (r_{O1} \parallel R_{M3})$$

$$R_A = R_0 \parallel R' = R_0 \parallel [r_{O2} + (1 + g_{m2} r_{O2})(r_{O1} \parallel R_{M3})]$$

$$Z_A = R_A C_0$$

$$f_A = \frac{1}{2\pi (R_A C_0)}$$

Node's names

X: Drain at M_1 and Source of M_2

Y: Gate of M_1

A: Drain at M_3

R_{M3} : The resistance seen looking into the source of M_3

4th question is simulated using LTSPICE

First of all, we need to models that are given to us.


In order to add these models in LTspice,

1-) Models codes are copied into a txt file named 180nm_bulk.txt


2-) We include this txt file using the command: `.inc 180nm_bulk.txt`

After the inclusion of the models, draw the asked circuit and select the asked transistors sizing.


The circuit is drawn as shown:

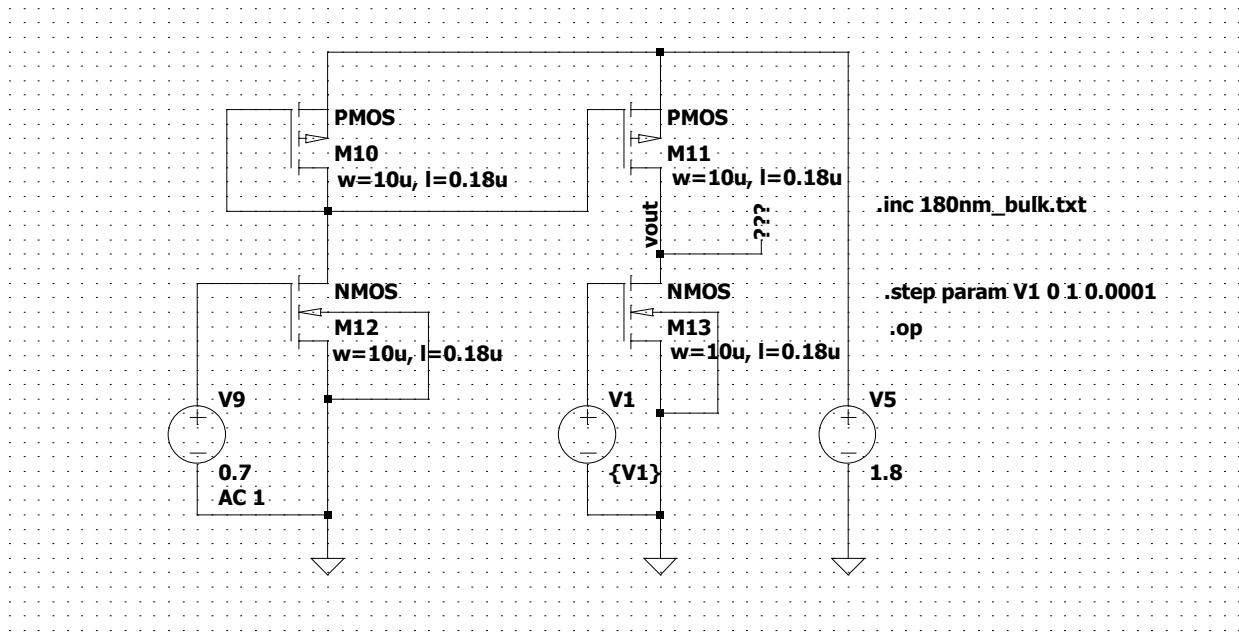

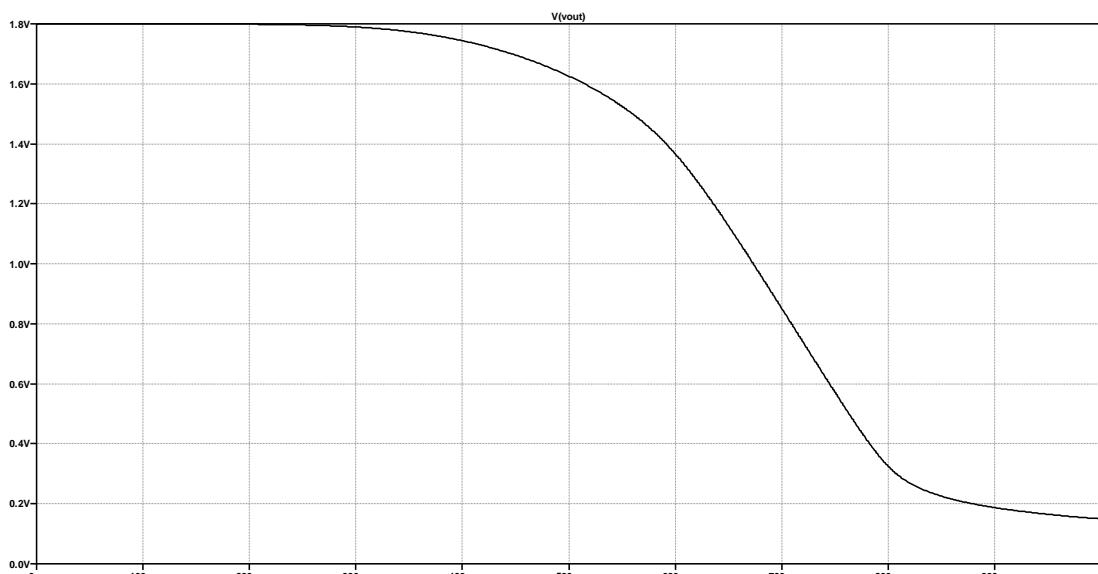Then, in order to determine the V1 voltage (input to M13) that corresponds to an output voltage of $V_{out} = 0.74V$, I increased V1 from 0V to 1V with small increments. The reason of increasing with small steps is the sensitivity of the circuit. It is very sensitive to small V1 voltages and the $V_{out} - V_1$ relationship can be seen from the figure:




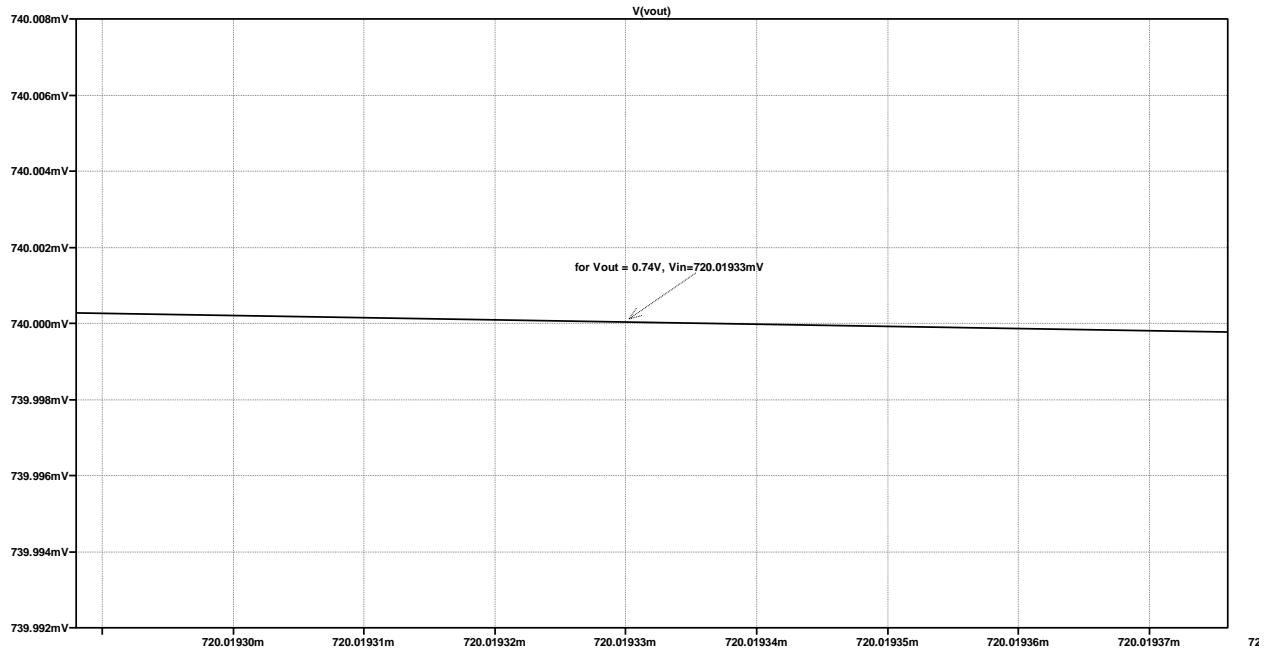Then we can determine the V₁ voltage that corresponds to 0.74V of output voltage from the figure. And to be precise let's zoom in the considered area. We can see the V₁ voltage from the figure:




As it can be clearly seen $V_1 = 720.01933\text{mV}$ corresponds to $V_{out} = 740\text{mV}$

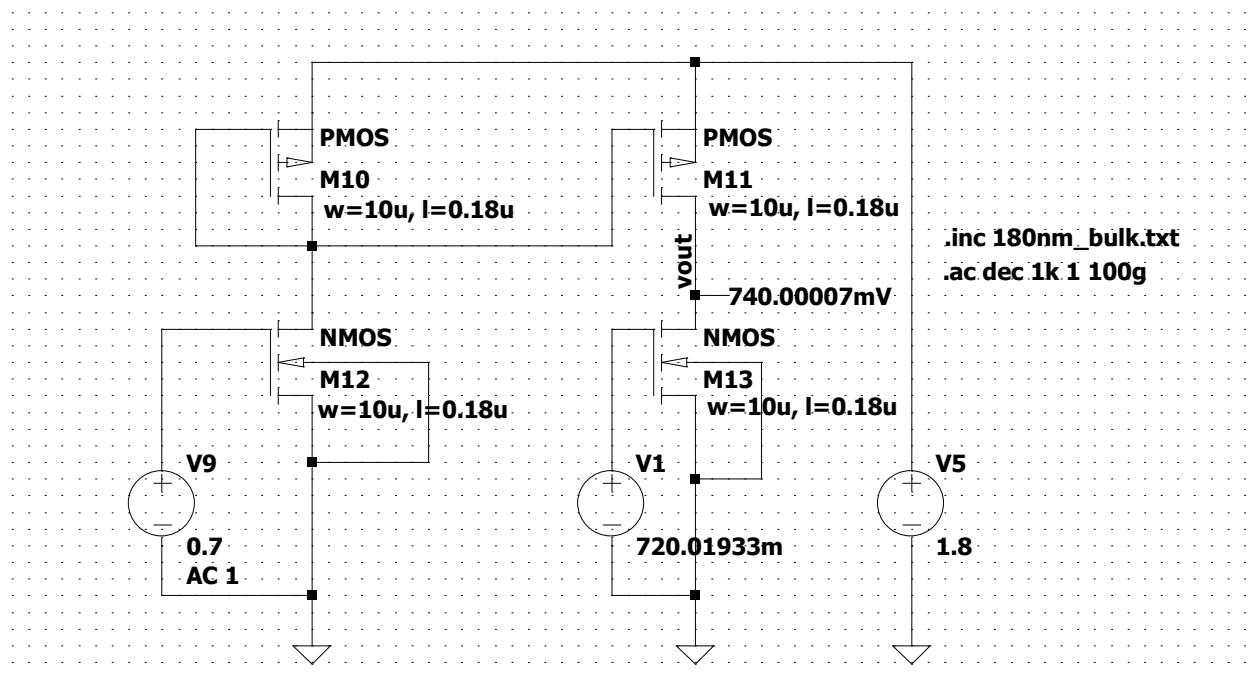Then by selecting $V1 = 720.01933$, analyze the gain of this circuit structure. We are using ac analysis for 1k points from 1 Hz to 100Ghz. The code for this is shown in the figure.




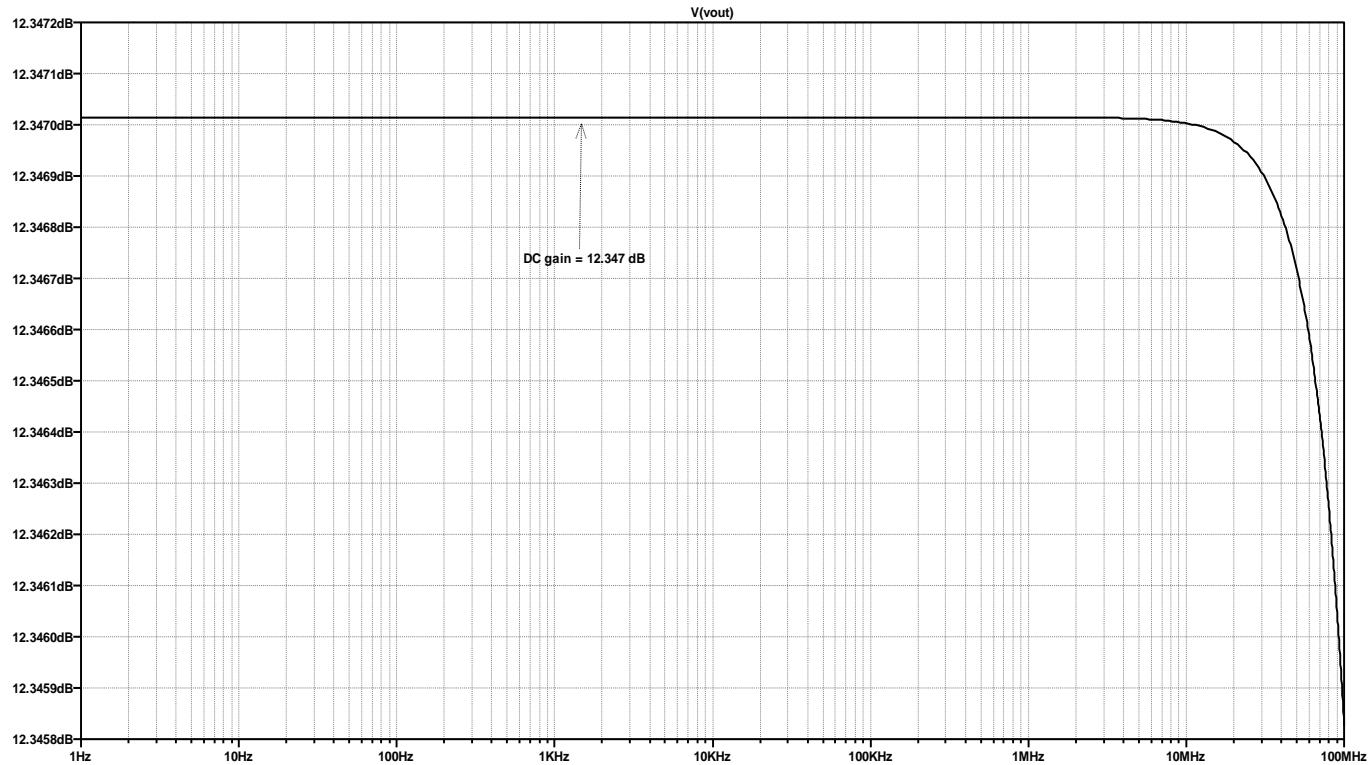If we run the circuit above, we get a frequency response as shown:



From this figure we find the DC gain of this circuit as $A_v = 12.3470 \text{ dB}$

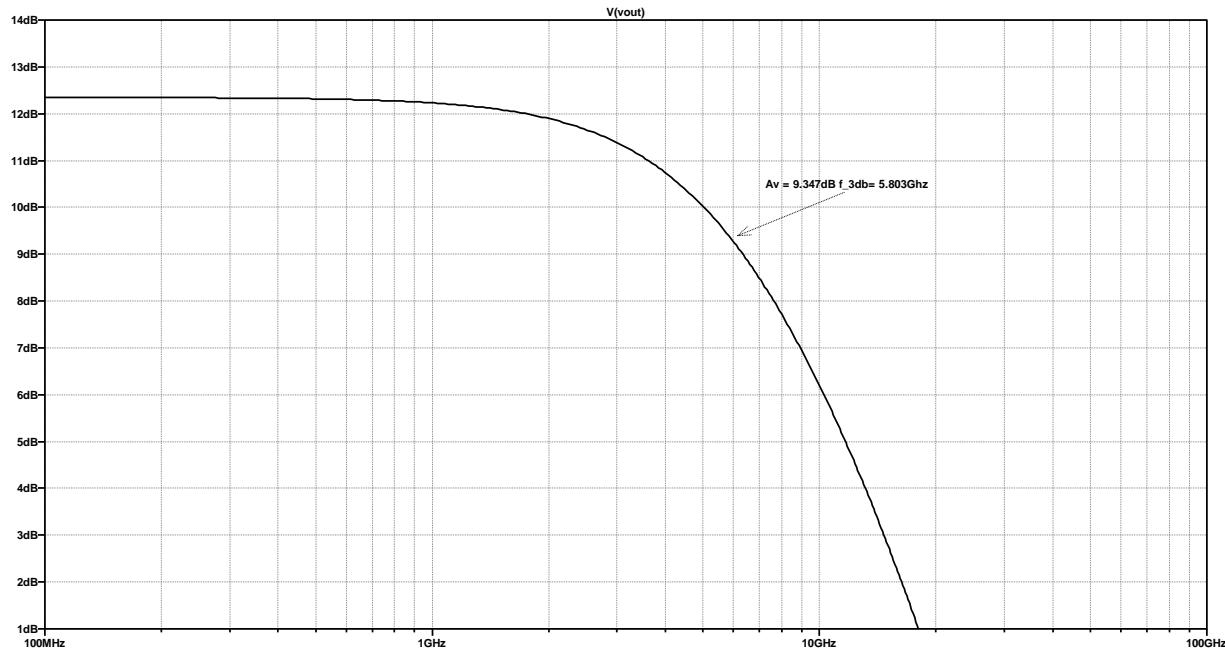Then let's zoom in to see at which frequency the circuit power halves. In other words, the gain drops by 3dB. The zoomed figure as shown:



Now from this figure we can say that $A_v = 12.3470 \text{ dB}$ and $f_{3-db} = 5.0803 \text{ Ghz}$

