


– EHB 335E – ANALOG ELECTRONICS – 11219 –



SERDEN SAIT ERANIL
040170025

EHB-335E / HMW #4

1)

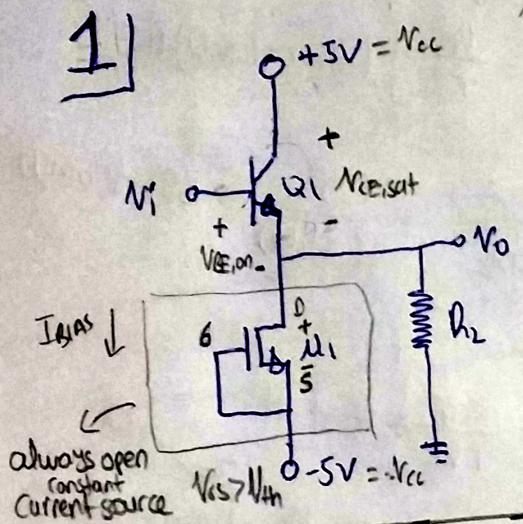

$$V_{BE,ON} = 0.7V$$

$$V_{CE,ISAT} = 0.2V$$

$$N_{TH} = -1.8V$$

$$k_n = \frac{1}{2} \mu_n C_{Ox} = \frac{12mA}{V^2}$$

$$\begin{aligned} N_A &= \infty \\ \lambda &= 0 \end{aligned} \quad \left. \begin{array}{l} \text{no transistor} \\ \text{output impedance} \end{array} \right\}$$

$$a) V_{CC} - V_{CE,ISAT} = V_{o,max} \quad (\text{At the edge of saturation})$$

$$-V_{CC} + V_{o,min_1} = V_{o,min_2} \quad (\text{At the edge of triode})$$

$$-I_{BIAS} R_L = V_{o,min_2} \quad (Q_1 \text{ off}) \quad V_{DD} = 16V$$

$$\Rightarrow V_{o,max} = 5V - 0.2V = 4.8V$$

$$I_{BIAS} = k_n (V_{BS} - N_{TH})^2 = \left(\frac{12mA}{V^2} \right) \cdot (1.8V)^2 = 12 \cdot (1.8)^2 mA = 38.88mA$$

$$\rightarrow \text{For } V_{o,min}$$

$$\bullet V_{o,min_1} = -V_{CC} + V_{oV} = -V_{CC} + (V_{BS} - N_{TH}) = -5V + 1.8V = -3.2V$$

$$\bullet V_{o,min_2} = -I_{BIAS} R_L$$

$$i) \text{ For } R_L = \infty \quad (\text{open-circuit})$$

$$V_{o,min} = -3.2V$$

$$ii) \text{ For } R_L = 600\Omega = 0.6k\Omega \Rightarrow V_{o,min_2} = -(38.88)(0.6) = -15.552V$$

$$V_{o,min} = -3.2V$$

- b) Since M_1 is a constant current source, the maximum current that can flow through the load resistance is equal to the bias current, it is achieved if Q_1 is in cut-off

Then,

$$I_{BIAS} = \frac{V_{out}}{R_L} = \frac{V_{o,min}}{R_{L,min}} \Rightarrow R_{L,min} = \frac{|V_P|}{I_{BIAS}} = \frac{2V}{38.88mA} = 51.64\Omega$$

C) What is power efficiency?

Given stage is an example of class-A output stage.

$$P_{avg,L} = \frac{1}{T} \int_0^T (V_{out}) \cdot \frac{V_{out}}{R_L} dt = \frac{V_p^2}{T R_L} \int_0^T \sin^2 \omega t dt = \frac{V_p^2}{T R_L} \int_0^T \left(\frac{1}{2} - \cos(2\omega t) \right) dt$$

$(V_{out} = V_p \sin \omega t)$

$$P_{avg,L} = \frac{V_p^2}{T R_L} \cdot \frac{T}{2} - \frac{V_p^2}{T R_L} \int_0^T \cos(2\omega t) dt = \frac{V_p^2}{2 R_L} = \frac{(2)^2}{2(51.46)} = 38.88 \text{ mW}$$

$$P_{avg,V^+} = \frac{1}{T} \int_0^T (I_{BIAS} + i_{RL}) V_{cc} dt = I_{BIAS} V_{cc} + \frac{V_{cc}}{T R_L} \int_0^T V_{out} dt$$

$$P_{avg,V^+} = I_{BIAS} V_{cc} + \frac{V_{cc}}{T R_L} \int_0^T V_p \sin \omega t dt = I_{BIAS} V_{cc} + \frac{V_{cc} \cdot V_p}{T R_L} \int_0^T \sin \omega t dt$$

$$P_{avg,V^+} = I_{BIAS} V_{cc} = (38.88) (5)$$

$$P_{avg,V^-} = I_{BIAS} V_{cc}; \quad P_{avg,V^-} = I_{BIAS} V_{cc} = (38.88) (5)$$


$$\eta = \frac{P_{avg,L}}{P_{avg,V^+} + P_{avg,V^-}} = \frac{P_{avg,L}}{2 P_{avg,V^-}} = \frac{38.88 \text{ mW}}{2(38.88)(5) \text{ mW}} = \frac{1}{10} = 10\%$$

\Rightarrow Since this is a class-A output stage, 10% power conversion efficiency is not surprising.

Class-AB (Assume all transistors are matched)

$$V_+ = -V_- = 12 \text{ V}; \quad \beta = 40; \quad V_{BE} = 0.7; \quad R_1 = R_2 = 250 \Omega$$
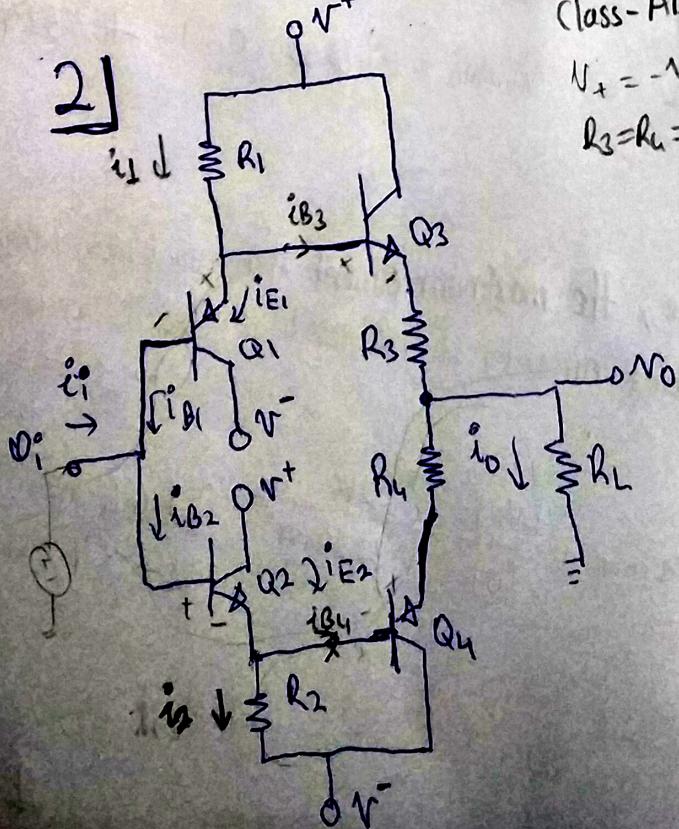
$$R_3 = R_4 = 0 \Omega; \quad R_L = 8 \Omega$$



a) for $V_i = 0 \text{ V}$

$$(i_1 + V_{EB1} - V_{BE3} - V_0) = 0$$

$$i_1 = V_0 = 0 \Rightarrow i_0 = \frac{V_0}{R_L} = 0$$

$$i_1 = \frac{V_+ - V_{BE1}}{R_1} = \frac{12 - 0.7}{250} = 45.2 \text{ mA}$$

$$i_2 = \frac{-V_{EB2} - (V^-)}{R_2} = \frac{12 - 0.7}{250} = 45.2 \text{ mA}$$

$$i_{E3} = i_0 = 0 \Rightarrow$$

$$\Rightarrow i_{E3} = i_0 = 0A \Rightarrow i_{B3} = 0 \Rightarrow i_1 = i_{B1} = 45.2mA$$

$$i_{B1} = i_{E1} / (\beta + 1) = \frac{45.2}{41} = 1.1mA$$

and since $i_{E3} = i_0 + i_{E4} \Rightarrow i_{E4} = 0 \Rightarrow i_{B4} = 0 =$

$$i_{B4} = 0 \Rightarrow i_2 = i_{E2} = 45.2mA \Rightarrow i_{B2} = \frac{45.2mA}{41} = 1.1mA$$

$$\Rightarrow \boxed{i_{E1} = 45.2mA} ; \boxed{i_{E2} = 45.2mA} ; \boxed{i_{B1} = 1.1mA} ; \boxed{i_{B2} = 1.1mA}$$

b) for $V_i = 5V$

we know that $0i + U_{eb1} - U_{eb3} - V_o = 0 \Rightarrow V_i = V_o = 5V$

Assume $i_{E3} = i_0 = \frac{V_o}{R_L} = \frac{5V}{8\Omega} = 0.625A \Rightarrow i_{B3} = \frac{i_{E3}}{\beta + 1} = \frac{0.625}{41} = 15.2mA$

$$i_1 = i_{E1} + i_{B3} \Rightarrow i_{E1} = i_1 - i_{B3} = \frac{N^+ - (V_i + U_{eb1})}{R_1} - i_{B3}$$

$$i_{E1} = \frac{12 - 5.7}{250} - 15.2mA = 9.96mA$$

$$i_{E3} = i_0 \Rightarrow i_{E4} = 0 \Rightarrow i_{B4} = 0$$

$$i_{E2} = i_2 = \frac{(V_i - U_{EB2}) - V}{R_2} = 65.2mA$$

$$i_{B2} = \frac{i_{E2}}{\beta + 1} = \frac{65.2}{41} = 1.6mA \Rightarrow i_{in} = i_{B2} - i_{B1} = 1.347mA$$

$$i_{in} = 1.347mA$$

$$i_0 = 0.625A$$

$$i_{E1} = 9.96mA$$


$$i_{E2} = 65.2mA$$

$$i_{B2} = 1.6mA$$

$$i_{B1} = 0.263mA$$

c) Current gain is calculated $A_i = \frac{i_{out}}{i_{in}} = \frac{i_0}{i_{in}} = \frac{0.625A}{1.347mA} = 463.994$

3)

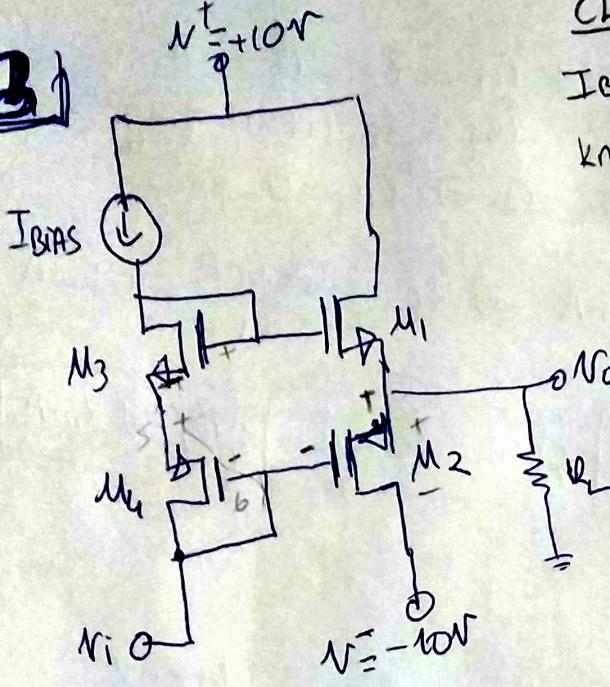

$$V_i + V_{S6,2} = V_o \Rightarrow V_{S6,2} = -V_i$$

$$V_{S6,2} = 1.5V$$

CLASS AB

$$I_{BIAS} = 0.2mA, R_L = 1k\Omega, V_{th,n} = 0.8V$$

$$k_n^l = 100\mu A/V^2$$

$$V_{th,p} = -0.8V, k_p^l = 40mA/V^2$$

$$V_{S6,3} = V_{S6,4}; V_{S6,2} = V_{S6,1}; \beta = 0$$

$$a) V_i = -1.5V; V_o = 0V \quad i_{D1} = i_{D2} = 0.5mA$$

$$V_i + V_{S6,4} + V_{S6,3} - V_{S6,1} = V_o$$

$$-1.5 + 2V_{S6,3} - V_{S6,1} = 0V$$

$$\boxed{2V_{S6,3} - V_{S6,1} = 1.5V}$$

$$2V_{S6,3} = 3V$$

$$V_{S6,3} = 1.5V$$

$$\text{For } M_1 \text{ and } M_2 \quad i_{D1} = i_{D2} = 0.5mA$$

$$5 \times 10^{-3} = (0.5) \left(10^{\frac{W}{L}} \right) \left(\frac{W}{L} \right)_1 (1.5 - 0.8)^2 \Rightarrow \left(\frac{W}{L} \right)_1 = 20.4$$

$$5 \times 10^{-3} = (0.5) \left(4 \times 10^3 \right) \left(\frac{W}{L} \right)_2 (1.5 - 0.8)^2 \Rightarrow \left(\frac{W}{L} \right)_2 = 51.02$$

$$\text{For } M_3 \text{ and } M_4 \quad I_{D3} = I_{D4} = I_{BIAS} = 0.2mA$$

$$2 \times 10^{-3} = (0.5) \left(10^{\frac{W}{L}} \right) \left(\frac{W}{L} \right)_3 (1.5 - 0.8)^2 \Rightarrow \left(\frac{W}{L} \right)_3 = 8.16$$

$$2 \times 10^{-3} = (0.5) \left(4 \times 10^5 \right) \left(\frac{W}{L} \right)_4 (1.5 - 0.8)^2 \Rightarrow \left(\frac{W}{L} \right)_4 = 20.4$$

$$b) \quad \underline{V_{o,max}}$$

$$V_{o,max,1} = V^+ - V_{ov1} = V^+ - (V_{S6,1} - V_{th,n}) = 10V - (0.7V) = 9.3V$$

$$V_{o,max,2} = V^+ - V_{IBIAS} - V_{S6,1} = 10 - (0.2 + 1.5V) = 8.3V$$

$$\text{then } V_{o,max} = 8.3V$$

V_{o,min}

$$V_{o,min,1} = V_{in} + V_{S6,2} = (-1.5V) + (1.5V) = 0$$


$$V_{o,min,2} = V^- + V_{S6,1} = V^- + (V_{S6} - |V_{th}|) = -10V + (1.5 - 0.8V) = -9.3V$$

$$\text{then } V_{o,min} = 0V$$

$$0V \leq V_o \leq 8.3V$$

4th QUESTION IS REALIZED USING LTSPICE


First of all, the circuit is drawn:

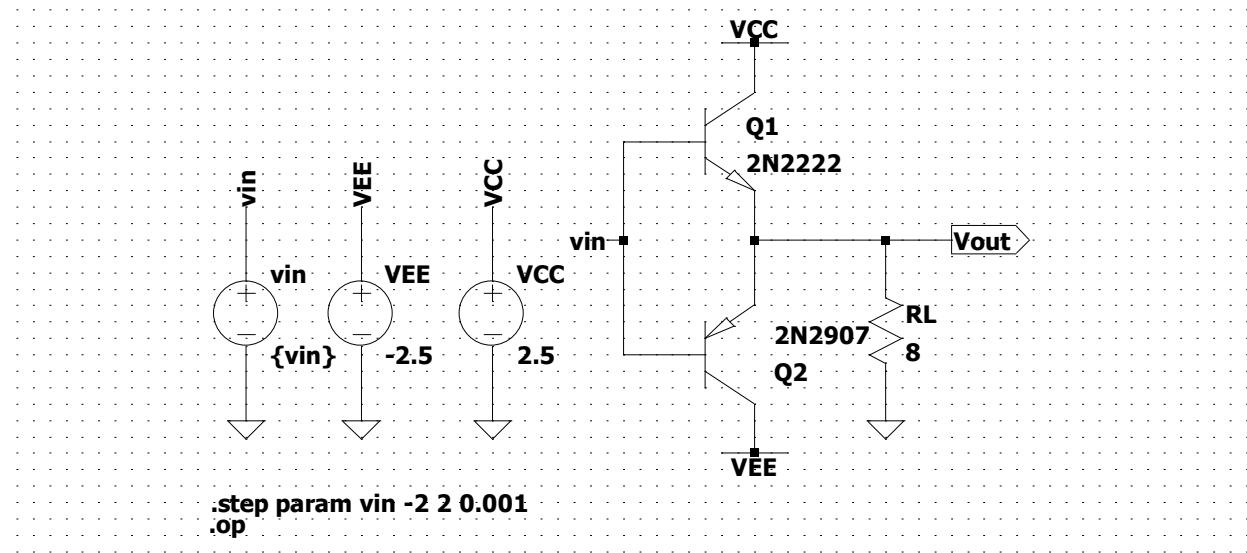

$$RL = 8 \Omega$$

In order to see how the output of the circuit responds changes in input voltage, lets sweep some input voltage from -2V to 2V by using the command .step param vin -2 2 0.001 and .op


The graph is shown as:

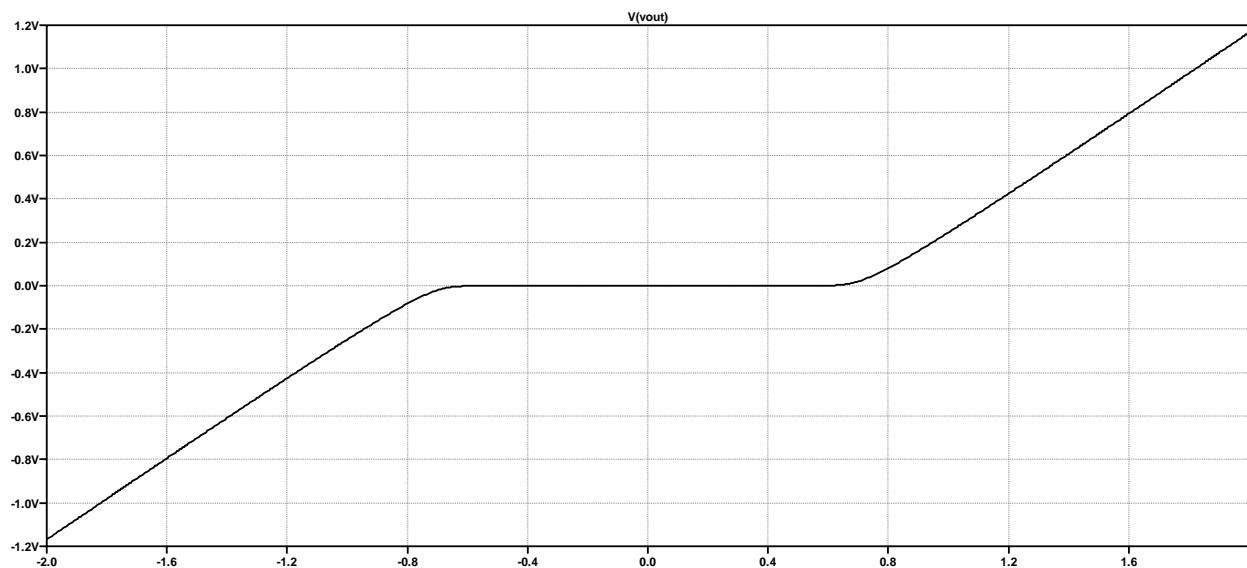

As it can be seen from this graph, for some input voltage values the output voltage becomes zero and the characteristic is not linear. Not being linear will introduce some harmonics to the amplified signal and therefore the audio or the output signal will be distorted (will be in different shape form from the input voltage).

To see the crossover distortion(harmonics) let's do transient analysis for an input sinusoid with 2V peak amplitude and 1 kHz frequency.


The plot is given as:

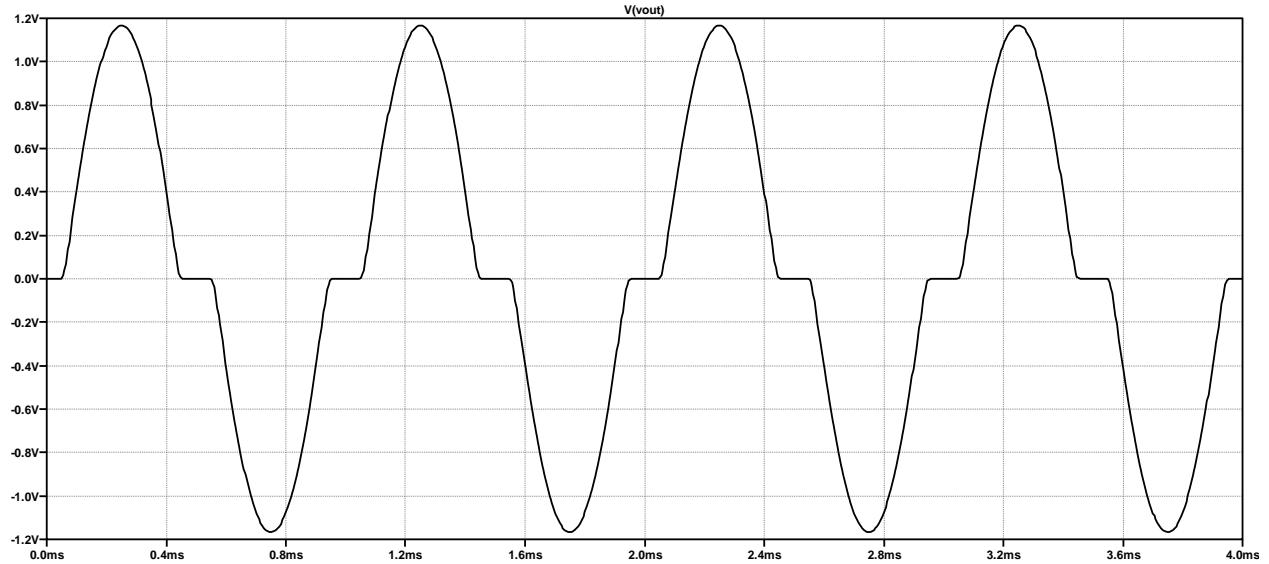

As it can be seen from this graph, the output signal is not sinusoid anymore which is not desirable and will introduce some higher frequencies into the signal.


RL = 16 Ω

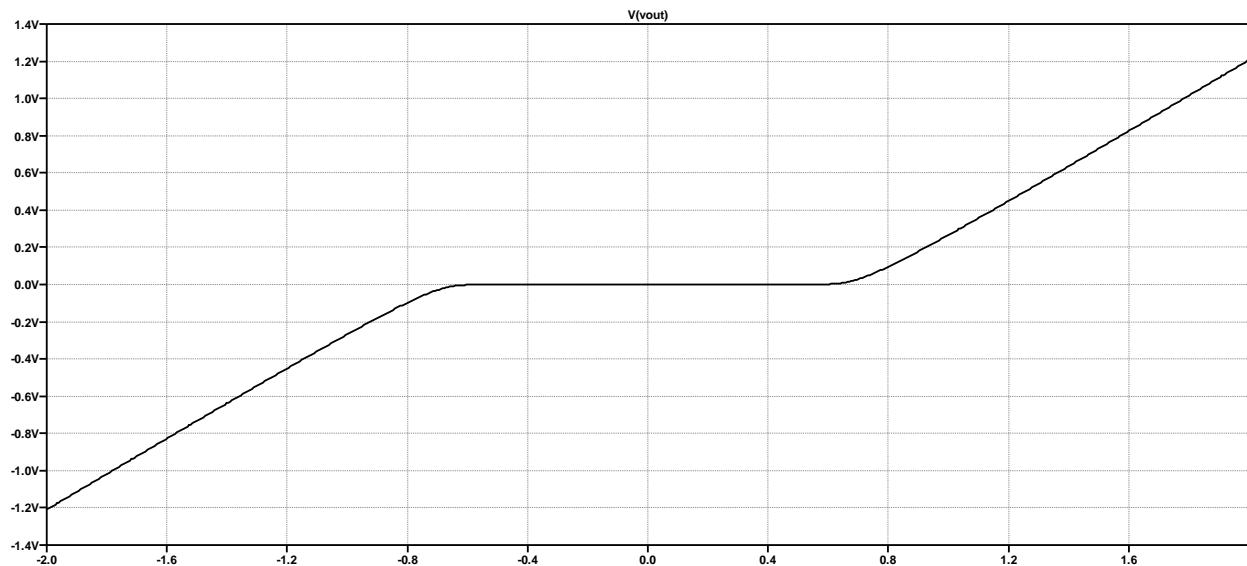Now let's increase the load resistance a bit and see what happens. Let's begin with linearity



Nothing changes much. Let us also analyze the circuit by transient analysis

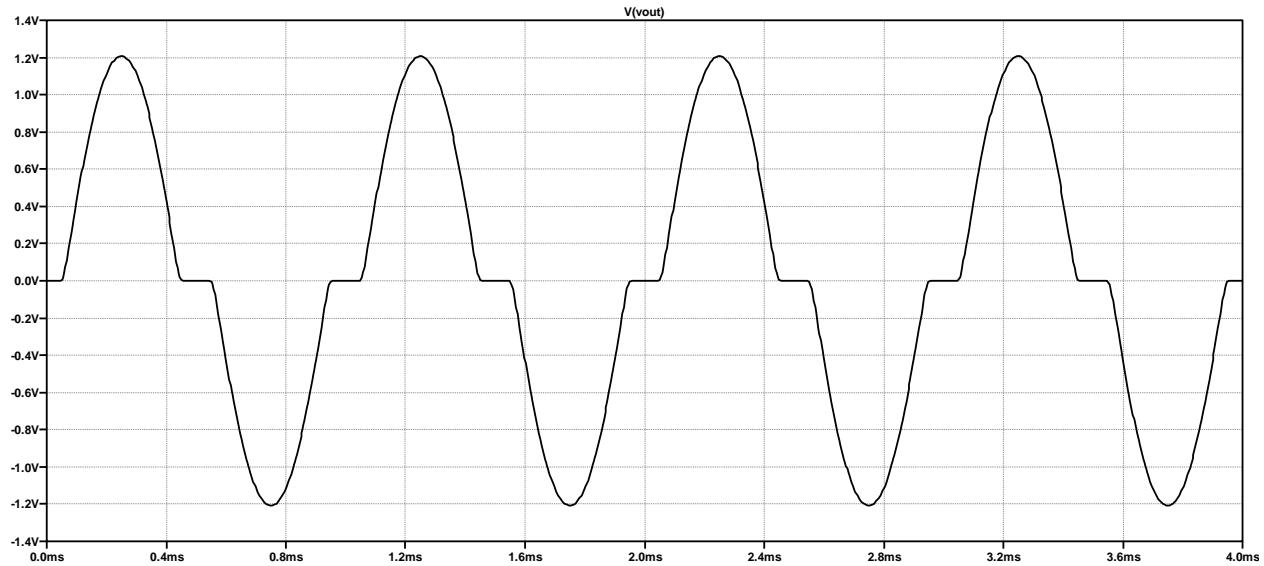The transient analysis for the same input sinusoid (2V peak amplitude and 1 kHz frequency) as given:



Very little changes occur in the amplitude but negligible. On the other hand in shape-wise if we increase the load resistance to 16Ω , No big changes occur.