

## Tutorial Problems: Bipolar Junction Transistor (Basic BJT Amplifiers)

### Part A. Common-Emitter Amplifier

1. For the circuit shown in Figure 1, the transistor parameters are  $\beta = 100$  and  $V_A = \infty$ . Design the circuit such that  $I_{CQ} = 0.25$  mA and  $V_{CEO} = 3$  V. Find the small-signal voltage gain  $A_v = v_o / v_s$ . Find the input resistance seen by the signal source  $v_s$ .

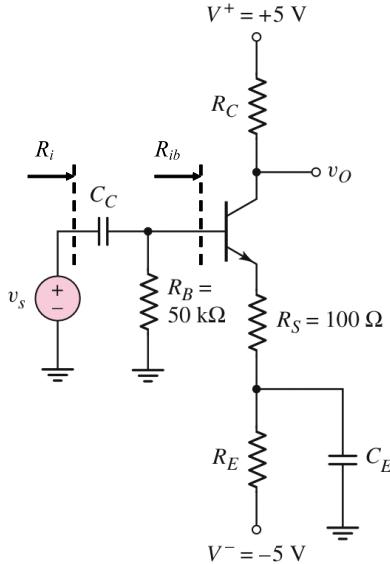


Figure 1

*Solution:*

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

For dc analysis, the capacitors  $C_C$  and  $C_E$  both act as *open circuit*.

Given the desired operating point  $I_{CQ} = 0.25$  mA and  $V_{CEO} = 3$  V, we have:

$$\begin{aligned}
 0 - V^- &= I_{BQ}R_B + V_{BE(on)} + I_{EQ}(R_S + R_E) \\
 &= \frac{I_{CQ}}{\beta}R_B + V_{BE(on)} + \left(\frac{1+\beta}{\beta}\right)I_{CQ}(R_S + R_E) \\
 0 - (-5) &= \left(\frac{0.25}{100}\right)(50) + 0.7 + \left(\frac{101}{100}\right)(0.25)(0.1 + R_E) \\
 \Rightarrow R_E &= 16.43 \text{ (k}\Omega\text{)}
 \end{aligned}$$

$$\begin{aligned}
 V^+ - V^- &= I_{CQ}R_C + V_{CEO} + I_{EQ}(R_S + R_E) \\
 5 - (-5) &= (0.25)R_C + 3 + \left(\frac{101}{100}\right)(0.25)(0.1 + 16.43) \\
 \Rightarrow R_C &= 11.30 \text{ (k}\Omega\text{)}
 \end{aligned}$$

The small-signal parameters are:

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.25} = 10.4 \text{ (k}\Omega\text{)}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.25}{0.026} = 9.6154 \text{ (mA/V)}$$

$$r_o = \frac{V_A}{I_{CQ}} = \infty$$

For small-signal ac analysis, all dc voltages and capacitors act as *short circuit*. The following expressions are obtained:

$$\begin{aligned} v_o &= -\beta i_b R_C \\ v_s &= i_b r_\pi + (1 + \beta) i_b R_S \\ A_v &= \frac{v_o}{v_s} = -\frac{\beta R_C}{r_\pi + (1 + \beta) R_S} \\ &= -\frac{(100)(11.30)}{10.4 + (101)(0.1)} \\ &= -55.12 \end{aligned}$$

The input resistance  $R_i$  seen by the signal source  $v_s$  is:

$$\begin{aligned} R_i &= R_B \parallel R_{ib} \\ &= R_B \parallel (r_\pi + (1 + \beta) R_S) \\ &= 50 \parallel 20.5 \\ &= 14.54 \text{ (k}\Omega\text{)} \end{aligned}$$

2. Consider the circuit shown in Figure 2. The transistor parameters are  $\beta = 100$  and  $V_A = 100$  V. Determine  $R_i$ ,  $A_v = v_o / v_s$  and  $A_i = i_o / i_s$ .

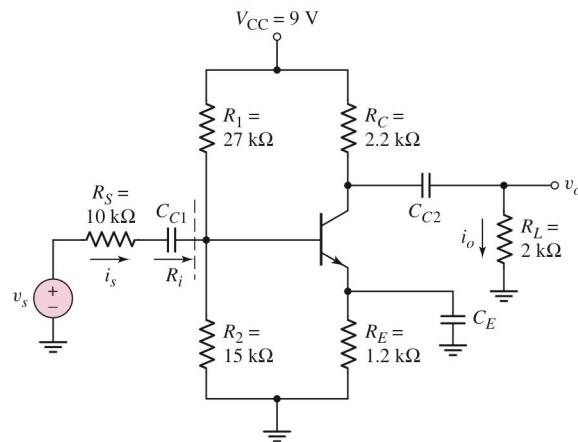


Figure 2

*Solution:*

A dc analysis is performed to determine the dc operating point by treating all capacitors as *open circuit*.

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC} = \left( \frac{15}{15+27} \right) (9) = 3.2143 \text{ (V)}$$

$$R_{TH} = R_1 \parallel R_2 = \frac{(15)(27)}{15+27} = 9.6429 \text{ (k}\Omega\text{)}$$

$$I_{BQ} = \frac{V_{TH} - V_{BE(on)}}{R_{TH} + (1+\beta)R_E} = \frac{3.2143 - 0.7}{9.6429 + (101)(1.2)} = 19.22 \text{ (\mu A)}$$

$$I_{CQ} = \beta I_{BQ} = 1.922 \text{ (mA)}$$

$$I_{EO} = (1+\beta) I_{BQ} = 1.941 \text{ (mA)}$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_C - I_{EO} R_E = 9 - (1.922)(2.2) - (1.941)(1.2) = 2.44 \text{ (V)}$$


The small-signal parameters are:

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{1.922} = 1.353 \text{ (k}\Omega\text{)}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{1.922}{0.026} = 73.923 \text{ (mA/V)}$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{100}{1.922} = 52.029 \text{ (k}\Omega\text{)}$$

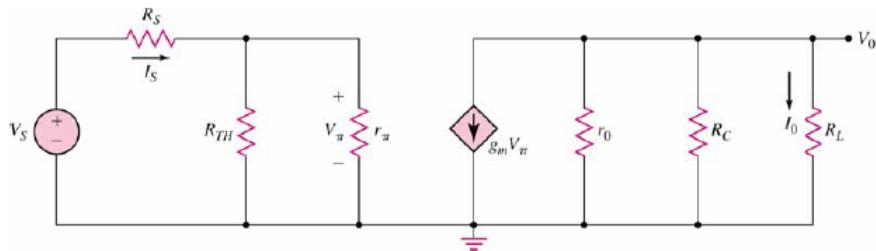For small-signal ac analysis, all dc voltages and capacitors act as *short circuit*. The following small-signal ac equivalent circuit is obtained:



Small-signal model of transistor circuit ( $*g_m V_\pi = \beta i_b$ )

$$v_o = -\beta i_b (R_L \parallel R_C \parallel r_o)$$

$$V_\pi = \frac{R_{TH} \parallel r_\pi}{R_s + R_{TH} \parallel r_\pi} v_s = i_b r_\pi$$

$$A_v = \frac{v_o}{v_s} = -\frac{\beta (R_L \parallel R_C \parallel r_o)}{r_\pi} \left[ \frac{R_{TH} \parallel r_\pi}{R_s + R_{TH} \parallel r_\pi} \right]$$

$$= -\frac{(100)(1.027)}{1.353} \left( \frac{1.187}{10 + 1.187} \right) = -8.05$$

$$\begin{aligned}
i_s &= \frac{v_s}{R_S + R_{TH} \parallel r_\pi} \\
i_o &= \frac{v_o}{R_L} \\
A_i &= \frac{i_o}{i_s} = \frac{R_S + R_{TH} \parallel r_\pi}{R_L} \cdot \frac{v_o}{v_s} \\
&= \left[ \frac{R_S + R_{TH} \parallel r_\pi}{R_L} \right] \left[ -\frac{\beta (R_L \parallel R_C \parallel r_o)}{r_\pi} \left( \frac{R_{TH} \parallel r_\pi}{R_S + R_{TH} \parallel r_\pi} \right) \right] \\
&= -\frac{\beta (R_L \parallel R_C \parallel r_o) (R_{TH} \parallel r_\pi)}{R_L r_\pi} \\
&= -\beta \left( \frac{R_C \parallel r_o}{R_L + R_C \parallel r_o} \right) \left( \frac{R_{TH}}{r_\pi + R_{TH}} \right) \\
&= -(100) \left( \frac{2.111}{2 + 2.111} \right) \left( \frac{9.6429}{1.353 + 9.6429} \right) = -45.05
\end{aligned}$$

The input resistance  $R_i$  is:

$$\begin{aligned}
R_i &= R_{TH} \parallel r_\pi \\
&= (9.6429) \parallel (1.353) = 1.187 \text{ (k}\Omega\text{)}
\end{aligned}$$

3. The parameters of the transistor in Figure 3 are  $\beta = 100$  and  $V_A = 100$  V.

- (a) Find the dc voltages at the base and emitter terminals.
- (b) Find  $R_C$  such that  $V_{CEQ} = 3.5$  V.
- (c) Assuming  $C_C$  and  $C_E$  act as short circuits, determine the small-signal voltage gain  $A_v = v_o / v_s$ .
- (d) Repeat part (c) if a  $500 \Omega$  source resistor is in series with the  $v_s$  signal source.

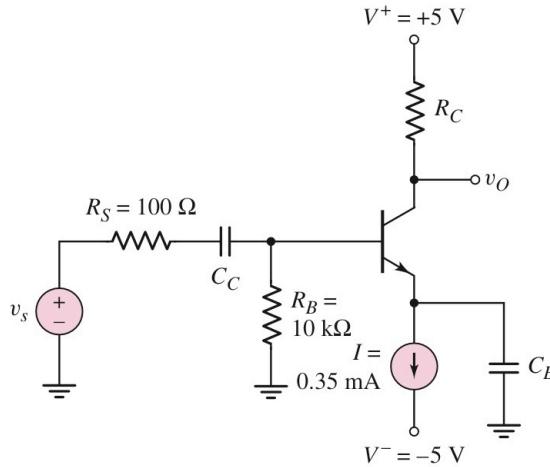


Figure 3

*Solution:*

(a)

A dc analysis is performed to determine the dc operating point by treating all capacitors as *open circuit*.

$$I_{CQ} = \frac{\beta}{1+\beta} I_{EQ} = \left( \frac{100}{1+100} \right) (0.35) = 0.347 \text{ (mA)}$$

$$I_{BQ} = \frac{I_{EQ}}{1+\beta} = \frac{0.35}{1+100} = 3.47 \text{ (\mu A)}$$

$$V_B = 0 - I_{BQ} R_B = -(3.47 \times 10^{-3})(10) = -0.0347 \text{ (V)}$$

$$V_E = V_B - V_{BE(on)} = -0.737 \text{ (V)}$$

(b)

Given  $V_{CEQ}$  is desired to be 3.5 V, hence:

$$\begin{aligned} V^+ &= V_E + V_{CEQ} + I_{CQ} R_C \\ R_C &= \frac{V^+ - V_E - V_{CEQ}}{I_{CQ}} \\ &= \frac{5 - (-0.737) - 3.5}{0.347} = 6.45 \text{ (k\Omega)} \end{aligned}$$

(c)

The small-signal parameters are:

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.347} = 7.493 \text{ (k\Omega)}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.347}{0.026} = 13.346 \text{ (mA/V)}$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{100}{0.347} = 288.184 \text{ (k\Omega)}$$

Using the small-signal ac equivalent circuit, the following expressions are obtained:

$$\begin{aligned} v_o &= -\beta i_b (R_C \parallel r_o) \\ V_\pi &= \frac{R_B \parallel r_\pi}{R_S + R_B \parallel r_\pi} v_s = i_b r_\pi \\ A_v &= \frac{v_o}{v_s} = -\frac{\beta (R_C \parallel r_o)}{r_\pi} \left( \frac{R_B \parallel r_\pi}{R_S + R_B \parallel r_\pi} \right) \\ &= -\frac{(100)(6.309)}{7.493} \left( \frac{4.283}{0.1 + 4.283} \right) = -82.28 \end{aligned}$$

(d)

If the source resistor is changed to  $500 \Omega$ , the new value of  $A_v$  is:

$$A_v = \frac{v_o}{v_s} = -\frac{\beta(R_C \parallel r_o)}{r_\pi} \left( \frac{R_B \parallel r_\pi}{R_S + R_B \parallel r_\pi} \right)$$

$$= -\frac{(100)(6.309)}{7.493} \left( \frac{4.283}{0.5 + 4.283} \right) = -75.40$$

Therefore the voltage gain  $A_v$  decreases as the source resistance  $R_S$  increases due to a larger voltage drop across the source resistor.

4. The transistor in the circuit in Figure 4 has a dc current gain of  $\beta = 100$ .

- (a) Determine the small-signal voltage gain  $A_v = v_o / v_s$ .
- (b) Find the input and output resistances  $R_i$  and  $R_o$ .

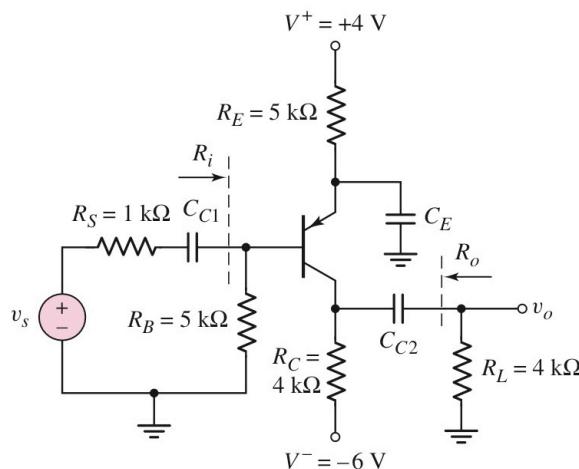


Figure 4

*Solution:*

(a)

A dc analysis is performed to determine the dc operating point by treating all capacitors as *open circuit*.

$$V^+ = I_{EQ}R_E + V_{EB(on)} + I_{BQ}R_B$$

$$I_{BQ} = \frac{V^+ - V_{EB(on)}}{R_B + (1 + \beta)R_E} = \frac{4 - 0.7}{5 + (101)(5)} = 6.47 (\mu A)$$

$$I_{CQ} = \beta I_{BQ} = (100)(6.47 \times 10^{-3}) = 0.647 (mA)$$

$$I_{EQ} = (1 + \beta)I_{BQ} = 0.654 (mA)$$

$$V_{ECQ} = V^+ - V^- - I_{EQ}R_E - I_{CQ}R_C = 4 - (-6) - (0.654)(5) - (0.647)(4) = 4.14 (V)$$


The small-signal parameters are:

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.647} = 4.019 \text{ (k}\Omega\text{)}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.647}{0.026} = 24.885 \text{ (mA/V)}$$

$$r_o = \frac{V_A}{I_{CQ}} = \infty$$

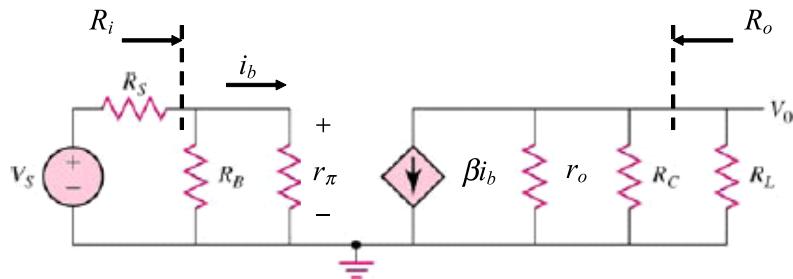Using the small-signal ac equivalent circuit, the following expressions are obtained:



$$v_o = -\beta i_b (R_L \parallel R_C \parallel r_o)$$

$$V_\pi = \frac{R_B \parallel r_\pi}{R_S + R_B \parallel r_\pi} v_s = i_b r_\pi$$

$$\begin{aligned} A_v &= \frac{v_o}{v_s} = -\frac{\beta (R_L \parallel R_C \parallel r_o)}{r_\pi} \left( \frac{R_B \parallel r_\pi}{R_S + R_B \parallel r_\pi} \right) \\ &= -\frac{(100)(2)}{4.019} \left( \frac{2.228}{1+2.228} \right) = -34.35 \end{aligned}$$

(b)

The input resistance  $R_i$  is:

$$\begin{aligned} R_i &= R_B \parallel r_\pi \\ &= (5) \parallel (4.019) = 2.228 \text{ (k}\Omega\text{)} \end{aligned}$$

To calculate the output resistance  $R_o$ , the signal source  $v_s$  is short-circuited and this gives  $i_b = 0$ . The following equation can be written by KCL at node  $v_o$ :

$$\begin{aligned} -i_o + \frac{v_o}{R_C} &= 0 \\ \frac{v_o}{i_o} &= R_o = R_C \\ &= 4 \text{ (k}\Omega\text{)} \end{aligned}$$

## Part B. Common-Collector Amplifier (Emitter Follower)

5. The transistor parameters for the circuit in Figure 5 are  $\beta = 180$  and  $V_A = \infty$ .

- Find  $I_{CQ}$  and  $V_{CEQ}$ .
- Plot the dc and ac load lines.
- Calculate the small-signal voltage gain.
- Determine the input and output resistances  $R_{ib}$  and  $R_o$ .

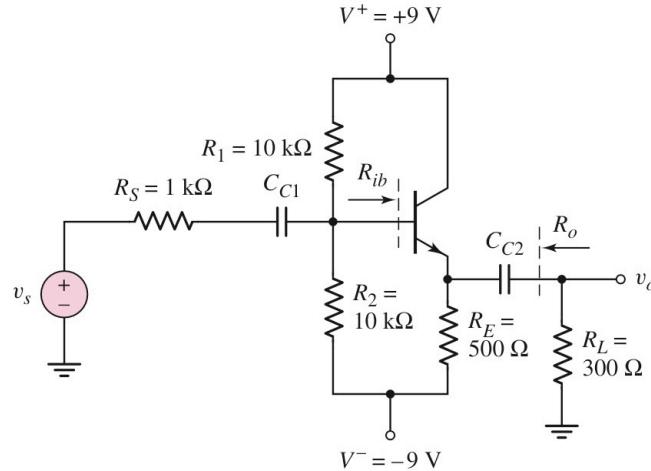


Figure 5

*Solution:*

(a)

For dc analysis, the capacitors  $C_{C1}$  and  $C_{C2}$  act as *open circuit*.

$$V_{TH} = \frac{R_2}{R_1 + R_2} (V^+ - V^-) + V^- = \left( \frac{10}{10+10} \right) (18) + (-9) = 0 \text{ (V)}$$

$$R_{TH} = R_1 \parallel R_2 = \frac{(10)(10)}{10+10} = 5.0 \text{ (k}\Omega\text{)}$$

$$I_{BQ} = \frac{V_{TH} - V_{BE(on)} - V^-}{R_{TH} + (1+\beta)R_E} = \frac{0 - 0.7 - (-9)}{5 + (181)(0.5)} = 86.91 \text{ (\mu A)}$$

$$I_{CQ} = \beta I_{BQ} = 15.644 \text{ (mA)}$$

$$I_{EQ} = (1+\beta)I_{BQ} = 15.731 \text{ (mA)}$$

$$V_{CEQ} = V^+ - V^- - I_{EQ}R_E = 9 - (-9) - (15.731)(0.5) = 10.13 \text{ (V)}$$

(b)

The dc load line is given by:


$$V^+ - V^- = V_{CE} + I_E R_E \approx V_{CE} + I_C R_E \text{ (for large } \beta\text{)}$$

$$I_C = -\frac{V_{CE}}{R_E} + \frac{(V^+ - V^-)}{R_E} = -2V_{CE} + 36$$

The ac load line is given by:

$$v_{ce} + i_e (R_E \parallel R_L) = 0$$
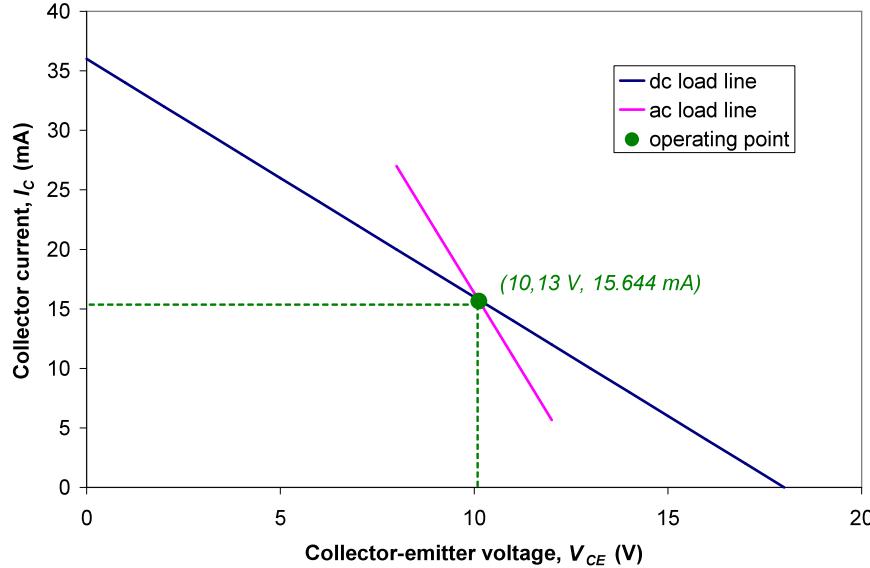
$$i_e \approx i_c = -\frac{v_{ce}}{R_E \parallel R_L} = -5.333 v_{ce}$$



(c)


The small-signal parameters are:

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(180)(0.026)}{15.644} = 0.299 \text{ (k}\Omega\text{)}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{15.644}{0.026} = 601.692 \text{ (mA/V)}$$

$$r_o = \frac{V_A}{I_{CQ}} = \infty$$

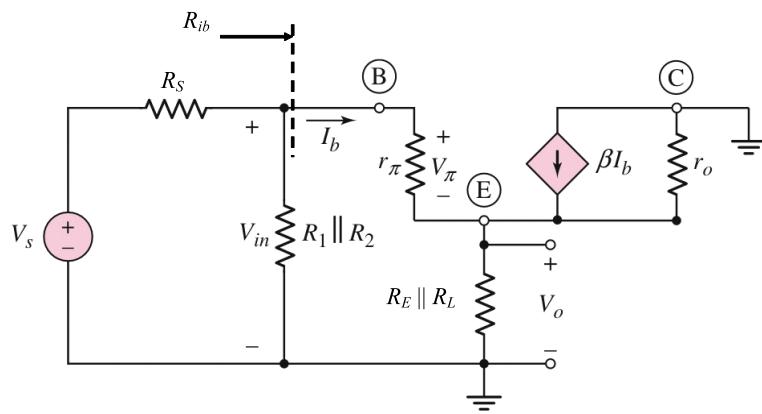The small-signal ac equivalent circuit becomes:



Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

$$\begin{aligned}
v_o &= (1+\beta)i_b(R_E \parallel R_L) \\
\Rightarrow \frac{v_o}{i_b} &= (1+\beta)(R_E \parallel R_L) = (181)(0.1875) = 33.9375 \\
v_b &= V_\pi + v_o = i_b r_\pi + (1+\beta)i_b(R_E \parallel R_L) \\
\Rightarrow \frac{v_b}{i_b} &= R_{ib} = r_\pi + (1+\beta)(R_E \parallel R_L) = 0.299 + 33.9375 = 34.2365 \\
v_b &= \frac{R_{ib} \parallel R_1 \parallel R_2}{R_S + R_{ib} \parallel R_1 \parallel R_2} v_s \\
\Rightarrow \frac{v_b}{v_s} &= \frac{R_{ib} \parallel R_1 \parallel R_2}{R_S + R_{ib} \parallel R_1 \parallel R_2} = \frac{4.3628}{1 + 4.3628} = 0.8135 \\
\frac{v_o}{v_s} &= \frac{v_o}{i_b} \times \frac{i_b}{v_b} \times \frac{v_b}{v_s} \\
&= (1+\beta)(R_E \parallel R_L) \times \frac{1}{R_{ib}} \times \frac{R_{ib} \parallel R_1 \parallel R_2}{R_S + R_{ib} \parallel R_1 \parallel R_2} \\
&= \frac{(1+\beta)(R_E \parallel R_L)}{R_{ib}} \left( \frac{R_{ib} \parallel R_1 \parallel R_2}{R_S + R_{ib} \parallel R_1 \parallel R_2} \right) \\
&= (33.9375) \left( \frac{1}{34.2365} \right) (0.8135) = 0.8064
\end{aligned}$$

(d)

The input resistance  $R_{ib}$  is:

$$\begin{aligned}
R_{ib} &= r_\pi + (1+\beta)(R_E \parallel R_L) \\
&= 0.299 + 33.9375 = 34.24 (\text{k}\Omega)
\end{aligned}$$

To calculate the output resistance  $R_o$ , the signal source  $v_s$  is short-circuited and the following equations can be written by KCL at node  $v_o$  and node  $v_b$ :

$$\begin{aligned}
v_b &= v_o + r_\pi i_b \\
\frac{v_b}{R_S \parallel R_1 \parallel R_2} + i_b &= 0 \quad (\text{KCL at node } v_b) \\
\frac{v_o + r_\pi i_b}{R_S \parallel R_1 \parallel R_2} + i_b &= 0 \Rightarrow \frac{v_o}{i_b} = -(r_\pi + R_S \parallel R_1 \parallel R_2) \\
i_o + (1+\beta)i_b &= \frac{v_o}{R_E} \quad (\text{KCL at node } v_o) \\
i_o - (1+\beta) \left( \frac{v_o}{r_\pi + R_S \parallel R_1 \parallel R_2} \right) &= \frac{v_o}{R_E} \\
\Rightarrow \frac{v_o}{i_o} &= R_o = R_E \parallel \left( \frac{r_\pi + R_S \parallel R_1 \parallel R_2}{1+\beta} \right) = 6.18 (\Omega)
\end{aligned}$$

6. For the circuit shown in Figure 6, let  $V_{CC} = 5$  V,  $R_L = 4$  k $\Omega$ ,  $R_E = 3$  k $\Omega$ ,  $R_1 = 60$  k $\Omega$ , and  $R_2 = 40$  k $\Omega$ . The transistor parameters are  $\beta = 50$  and  $V_A = 80$  V.
- Determine  $I_{CQ}$  and  $V_{ECQ}$ .
  - Plot the dc and ac load lines.
  - Determine  $A_v = v_o / v_s$  and  $A_i = i_o / i_s$ .
  - Determine  $R_{ib}$  and  $R_o$ .

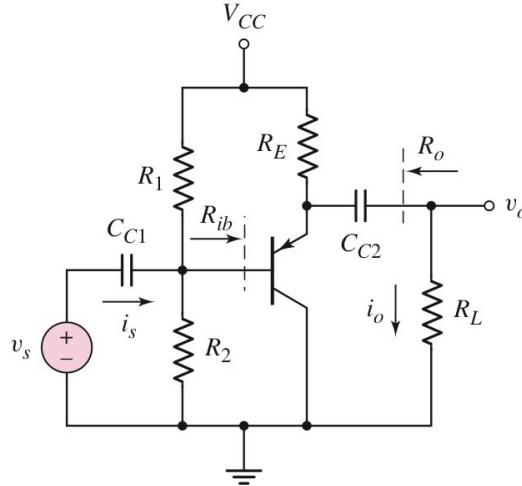


Figure 6

*Solution:*

(a)

For dc analysis, the capacitors  $C_{C1}$  and  $C_{C2}$  act as *open circuit*.

$$V_{TH} = \frac{R_2}{R_1 + R_2} V_{CC} = \left( \frac{40}{60+40} \right) (5) = 2.0 \text{ (V)}$$

$$R_{TH} = R_1 \parallel R_2 = \frac{(60)(40)}{60+40} = 24.0 \text{ (k}\Omega\text{)}$$

$$I_{BQ} = \frac{V_{CC} - V_{EB(\text{on})} - V_{TH}}{R_{TH} + (1+\beta)R_E} = \frac{5 - 0.7 - 2}{24 + (51)(3)} = 12.99 \text{ (\mu A)}$$

$$I_{CQ} = \beta I_{BQ} = 0.650 \text{ (mA)}$$

$$I_{EQ} = (1+\beta) I_{BQ} = 0.663 \text{ (mA)}$$

$$V_{ECQ} = V_{CC} - I_{EQ} R_E = 5 - (0.663)(3) = 3.01 \text{ (V)}$$

(b)

The dc load line is given by:


$$V_{CC} = I_E R_E + V_{EC} \approx \left( \frac{1+\beta}{\beta} \right) I_C R_E + V_{EC}$$

$$I_C = -\frac{V_{EC}}{\left( \frac{1+\beta}{\beta} \right) R_E} + \frac{V_{CC}}{\left( \frac{1+\beta}{\beta} \right) R_E} = -0.3268 V_{EC} + 1.6340$$

The ac load line is given by:

$$v_{ec} + i_e (R_E \parallel R_L) = 0$$
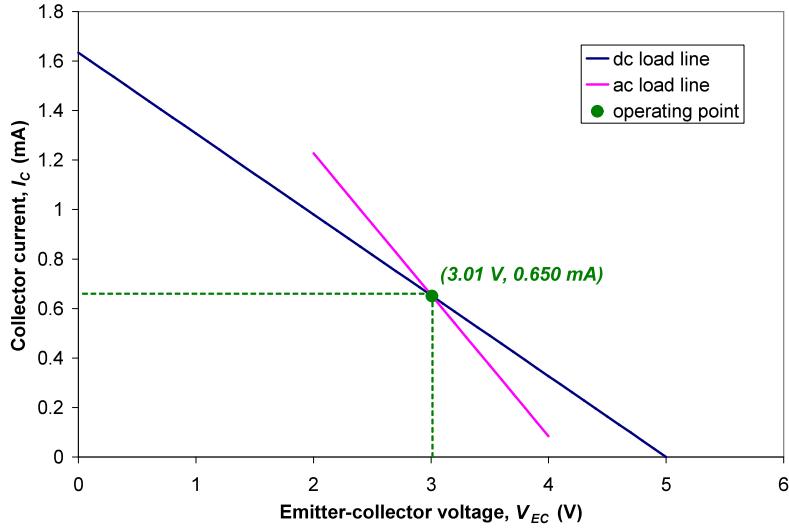
$$v_{ec} + i_c \left( \frac{1+\beta}{\beta} \right) (R_E \parallel R_L) = 0 \Rightarrow i_c = - \frac{v_{ce}}{\left( \frac{1+\beta}{\beta} \right) (R_E \parallel R_L)} = -0.5719 v_{ce}$$



(c)


The small-signal parameters are:

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(50)(0.026)}{0.650} = 2.0 \text{ (k}\Omega\text{)}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.650}{0.026} = 25.0 \text{ (mA/V)}$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{80}{0.650} = 123.077 \text{ (k}\Omega\text{)}$$

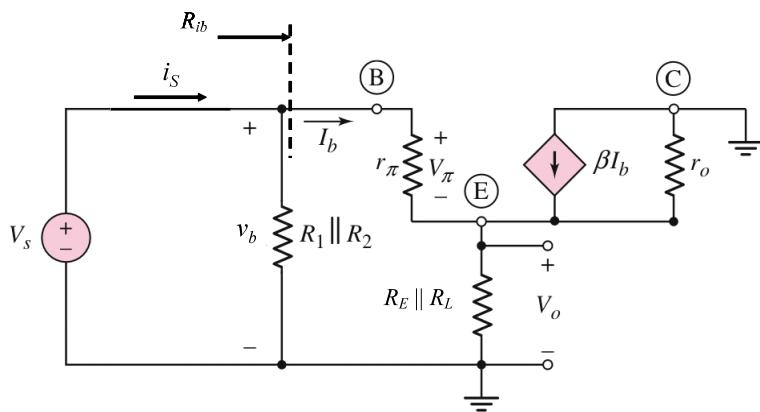The small-signal ac equivalent circuit becomes:



Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

$$\begin{aligned}
v_o &= \left[ i_b + \beta i_b + \frac{-v_o}{r_o} \right] (R_E \parallel R_L) \\
&\Rightarrow \frac{v_o}{i_b} = \frac{(1+\beta)(R_E \parallel R_L)}{1+(R_E \parallel R_L)/r_o} = \frac{(51)(1.7143)}{1+1.7143/123.077} = 86.2283 \\
v_b &= V_\pi + v_o = i_b r_\pi + \left[ \frac{(1+\beta)(R_E \parallel R_L)}{1+(R_E \parallel R_L)/r_o} \right] i_b \\
&\Rightarrow \frac{v_b}{i_b} = R_{ib} = r_\pi + \left[ \frac{(1+\beta)(R_E \parallel R_L)}{1+(R_E \parallel R_L)/r_o} \right] = 2.0 + 86.2283 = 88.2283
\end{aligned}$$

$$\begin{aligned}
v_b &= v_s \\
&\Rightarrow \frac{v_b}{v_s} = 1 \\
\frac{v_o}{v_s} &= \frac{v_o}{i_b} \times \frac{i_b}{v_b} \times \frac{v_b}{v_s} \\
&= \frac{(1+\beta)(R_E \parallel R_L)}{1+(R_E \parallel R_L)/r_o} \times \frac{1}{R_{ib}} \times 1 \\
&= \frac{1}{R_{ib}} \left[ \frac{(1+\beta)(R_E \parallel R_L)}{1+(R_E \parallel R_L)/r_o} \right] \\
&= (86.2283) \left( \frac{1}{88.2283} \right) = 0.9773
\end{aligned}$$

$$\begin{aligned}
v_o &= i_o R_L \\
&\Rightarrow \frac{v_o}{i_o} = R_L = 4 \\
v_o &= \left[ i_b + \beta i_b + \frac{-v_o}{r_o} \right] (R_E \parallel R_L) \\
&\Rightarrow \frac{v_o}{i_b} = \frac{(1+\beta)(R_E \parallel R_L)}{1+(R_E \parallel R_L)/r_o} = \frac{(51)(1.7143)}{1+1.7143/123.077} = 86.2283 \\
i_b &= \frac{R_1 \parallel R_2}{R_{ib} + R_1 \parallel R_2} i_s \\
&\Rightarrow \frac{i_b}{i_s} = \frac{R_1 \parallel R_2}{R_{ib} + R_1 \parallel R_2} = \frac{24}{88.2283 + 24} = 0.2138 \\
\frac{i_o}{i_s} &= \frac{i_o}{v_o} \times \frac{v_o}{i_b} \times \frac{i_b}{i_s} \\
&= \frac{1}{R_L} \times \frac{(1+\beta)(R_E \parallel R_L)}{1+(R_E \parallel R_L)/r_o} \times \frac{R_1 \parallel R_2}{R_{ib} + R_1 \parallel R_2} \\
&= \left( \frac{1}{4} \right) (86.2283) (0.2138) = 4.61
\end{aligned}$$

(d)

The input resistance  $R_{ib}$  is:

$$R_{ib} = r_\pi + \left[ \frac{(1+\beta)(R_E \parallel R_L)}{1+(R_E \parallel R_L)/r_o} \right] = 2.0 + 86.2283 = 88.23 \text{ (k}\Omega\text{)}$$

To calculate the output resistance  $R_o$ , the signal source  $v_s$  is short-circuited and the following equations can be written by KCL at node  $v_o$ :

$$\begin{aligned} i_b &= -\frac{v_o}{r_\pi} \\ i_o + \beta i_b + i_b &= \frac{v_o}{r_o \parallel R_E} \\ i_o + (1+\beta) \left( -\frac{v_o}{r_\pi} \right) &= \frac{v_o}{r_o \parallel R_E} \\ \frac{v_o}{i_o} = R_o &= \frac{1}{\frac{1+\beta}{r_\pi} + \frac{1}{r_o \parallel R_E}} \\ &= r_o \parallel R_E \parallel \frac{r_\pi}{1+\beta} \\ &= 38.70 \text{ (\Omega)} \end{aligned}$$

7. For the transistor in Figure 7, the parameters are  $\beta = 100$  and  $V_A = \infty$ .

- (a) Design the circuit such that  $I_{EQ} = 1 \text{ mA}$  and the  $Q$ -point is in the center of the dc load line.
- (b) If the peak-to-peak sinusoidal output voltage is 4 V, determine the peak-to-peak sinusoidal signals at the base of the transistor and the peak-to-peak value of  $v_s$ .
- (c) If the load resistor  $R_L = 1 \text{ k}\Omega$  is connected to the output through a coupling capacitor, determine the peak-to-peak value in the output voltage, assuming  $v_s$  is equal to the value determined in part (b).

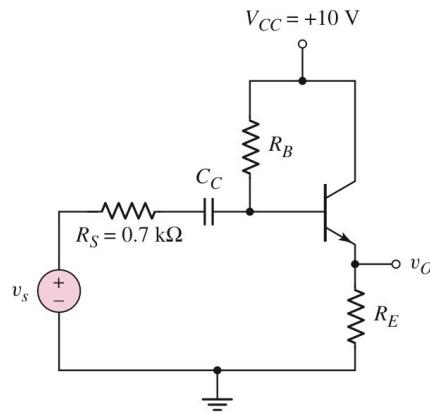


Figure 7

*Solution:*

(a)

For dc analysis, the capacitor  $C_C$  acts as *open circuit*.

$$\begin{aligned} V_{CC} &= I_{BQ}R_B + V_{BE(on)} + I_{EQ}R_E \\ &= \left( \frac{R_B}{1+\beta} + R_E \right) I_{EQ} + V_{BE(on)} \\ \frac{R_B}{101} + R_E &= \frac{V_{CC} - V_{BE(on)}}{I_{EQ}} = \frac{10 - 0.7}{1} = 9.3 \text{ (k}\Omega\text{)} \quad \dots(1) \end{aligned}$$

$$V_{CC} = V_{CEQ} + I_{EQ}R_E \quad (V_{CEQ} = \frac{V_{CC}}{2} \text{ for } Q\text{-point is in the center of the dc load line})$$

$$10 = 5 + (1)R_E$$

$$R_E = 5 \text{ (k}\Omega\text{)} \quad \dots(2)$$

$$\Rightarrow R_B = (101)(9.3 - R_E) = 434.3 \text{ (k}\Omega\text{)}$$

$$I_{CQ} = \left( \frac{\beta}{1+\beta} \right) I_{EQ} = \left( \frac{100}{101} \right) (1) = 0.990 \text{ (mA)}$$


$$r_\pi = \frac{\beta V_T}{I_{CQ}} = \frac{(100)(0.026)}{0.990} = 2.6263 \text{ (k}\Omega\text{)}$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.990}{0.026} = 38.0769 \text{ (mA/V)}$$

$$r_o = \frac{V_A}{I_{CQ}} = \infty$$

(b)

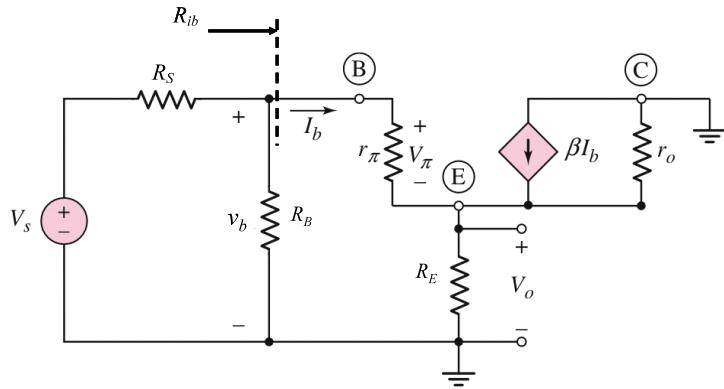The small-signal ac equivalent circuit is given by:



Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

$$r_o = \infty$$

$$\begin{aligned}
v_o &= (1 + \beta) R_E i_b \\
\Rightarrow \frac{v_o}{i_b} &= (1 + \beta) R_E = (101)(5) = 505 \\
v_b &= V_\pi + v_o = i_b r_\pi + (1 + \beta) R_E i_b \\
\Rightarrow \frac{v_b}{i_b} &= R_{ib} = r_\pi + (1 + \beta) R_E = 2.6263 + 505 = 507.6263 \\
v_b &= \frac{R_B \parallel R_{ib}}{R_S + R_B \parallel R_{ib}} v_s \\
\Rightarrow \frac{v_b}{v_s} &= \frac{R_B \parallel R_{ib}}{R_S + R_B \parallel R_{ib}} = \frac{234.0545}{0.7 + 234.0545} = 0.9970 \\
\frac{v_b}{v_o} &= \frac{v_b}{i_b} \times \frac{i_b}{v_o} \\
&= \frac{r_\pi + (1 + \beta) R_E}{(1 + \beta) R_E} \\
&= \frac{507.6263}{505} = 1.0052 \quad \dots(3) \\
\frac{v_o}{v_s} &= \frac{v_o}{i_b} \times \frac{i_b}{v_b} \times \frac{v_b}{v_s} \\
&= (1 + \beta) R_E \times \frac{1}{R_{ib}} \times \frac{R_B \parallel R_{ib}}{R_S + R_B \parallel R_{ib}} \\
&= 505 \times \frac{1}{507.6263} \times 0.9970 = 0.9918 \quad \dots(4)
\end{aligned}$$

If the peak-to-peak output voltage  $v_{o(peak-peak)}$  is 4 V,

$$\begin{aligned}
\text{Eq.(3)} \Rightarrow v_{b(peak-peak)} &= 1.0052 v_{s(peak-peak)} = 4.021 \text{ (V)} \\
\text{Eq.(4)} \Rightarrow v_{s(peak-peak)} &= \frac{v_{o(peak-peak)}}{0.9918} = 4.033 \text{ (V)}
\end{aligned}$$

(c)

If the load resistor  $R_L = 1 \text{ k}\Omega$  is added in parallel to  $R_E$ , Eq. (4) must be modified accordingly:

$$\begin{aligned}
\frac{v_o}{v_s} &= \frac{(1 + \beta)(R_E \parallel R_L)}{r_\pi + (1 + \beta)(R_E \parallel R_L)} \left( \frac{R_B \parallel R_{ib}}{R_S + R_B \parallel R_{ib}} \right) \\
&= \frac{(101)(0.8333)}{2.6263 + (101)(0.8333)} (0.9970) = 0.9668 \\
\Rightarrow v_{o(peak-peak)} &= 0.9668 v_{s(peak-peak)} = (0.9668)(4.033) = 3.90 \text{ (V)}
\end{aligned}$$

Therefore  $v_{o(peak-peak)}$  becomes smaller due to the loading effect by  $R_L$ .

8. An emitter-follower amplifier, with the configuration shown in Figure 8, is to be designed such that an audio signal given by  $v_s = 5 \sin(3000t)$  V but with a source resistance of  $R_S = 10 \Omega$  can drive a small speaker. Assume the supply voltages are  $V^+ = +12$  V and  $V^- = -12$  V and  $\beta = 50$ . The load, representing the speaker, is  $R_L = 12 \Omega$ . The amplifier should be capable of delivering approximately 1 W of average power to the load. What is the signal power gain of your amplifier?

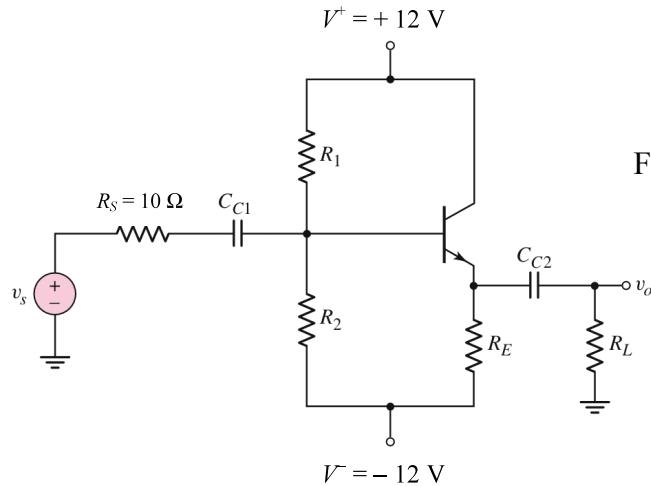


Figure 8

*Solution:*

To deliver 1 W of average power to the load, the peak-to-peak output voltage should be:

$$\begin{aligned}\frac{v_{o(rms)}^2}{R_L} &= \frac{v_{o(peak)}^2}{2R_L} = 1 \\ \Rightarrow v_{o(peak)} &= 4.899 \text{ (V)} \\ \Rightarrow i_{o(peak)} &= \frac{4.899}{12} = 0.408 \text{ (A)} \\ \Rightarrow v_{o(peak-peak)} &= 9.798 \text{ (V)}\end{aligned}$$

The required voltage gain  $A_v$  is:

$$A_v = \frac{v_{o(peak)}}{v_{s(peak)}} = \frac{4.899}{5.0} = 0.9798$$


Choose  $I_{EQ} = 0.8$  A and  $V_{CEQ} = 12$  V,

$$R_E = \frac{V^+ - V^- - V_{CEQ}}{I_{EQ}} = \frac{12 - (-12) - 12}{0.8} = 15 \text{ } \Omega$$

$$R_{TH} = \frac{1}{10}(1 + \beta)R_E = \left(\frac{51}{10}\right)(15) = 76.5 \text{ } \Omega \text{ (for bias-stable circuit)}$$

$$\begin{aligned}
V_{TH} &= V^- + I_{EQ}R_E + V_{BE(on)} + I_{BQ}R_{TH} \\
&= -12 + (0.8)(15) + 0.7 + \left(\frac{0.8}{51}\right)(76.5) = 1.9 \text{ (V)} \\
&= \frac{R_1}{R_1 + R_2} (V^+ - V^-) + V^- = \frac{1}{R_1} (R_1 \parallel R_2) (V^+ - V^-) + V^- \\
\Rightarrow R_1 &= 132 \text{ } (\Omega) \quad R_2 = 182 \text{ } (\Omega)
\end{aligned}$$

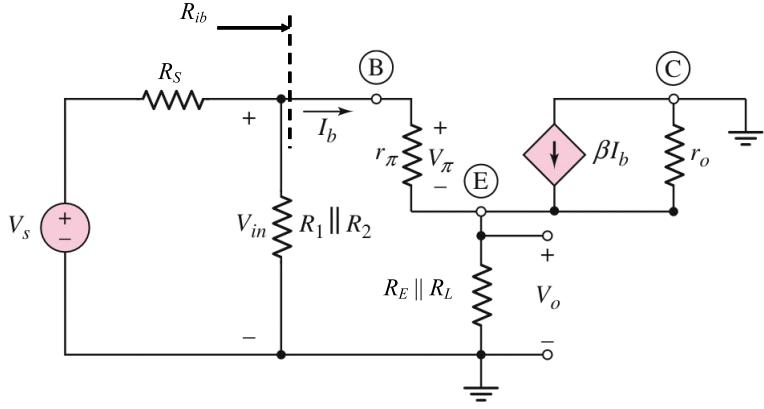The small-signal ac equivalent circuit is given by:



Choosing  $I_{EQ} = 0.5 \text{ A}$  gives:

$$\begin{aligned}
I_{CQ} &= \frac{\beta}{1+\beta} I_{EQ} = \left(\frac{50}{51}\right)(0.8) = 0.784 \text{ (A)} \\
r_\pi &= \frac{\beta V_T}{I_{CQ}} = \frac{(50)(0.026)}{0.784} = 1.658 \text{ } (\Omega)
\end{aligned}$$

The small-signal voltage gain is taken from Q.7 with some modifications:

$$\begin{aligned}
\frac{v_o}{v_s} &= \frac{(1+\beta)(R_E \parallel R_L)}{r_\pi + (1+\beta)(R_E \parallel R_L)} \left( \frac{R_1 \parallel R_2 \parallel R_{ib}}{R_S + R_1 \parallel R_2 \parallel R_{ib}} \right) \\
&= \frac{(51)(6.667)}{1.658 + (51)(6.667)} \left( \frac{62.5116}{10 + 62.5116} \right) \\
&= 0.8579
\end{aligned}$$

Due to the presence of the source resistance  $R_S$  (loading effect) the required voltage gain of  $A_v = 0.9798$  cannot be achieved. Note that  $A_v = 0.9951$  if  $R_S = 0$ .

Therefore the maximum achievable peak output voltage is:

$$\frac{v_{o(peak)}}{v_{s(peak)}} = 0.8579 \Rightarrow v_{o(peak)} = 4.290 \text{ (V)}$$

Hence the output power delivered to the load  $R_L$  is:

$$P_L = \frac{v_{o(peak)}^2}{2R_L} = 0.767 \text{ (W)}$$

The input power delivered by the signal source  $v_s$  is:

$$\begin{aligned} P_S &= v_{s(rms)} i_{s(rms)} \\ i_{s(rms)} &= \frac{v_{s(rms)}}{R_i} = \frac{v_{s(rms)}}{R_S + R_1 \parallel R_2 \parallel R_{ib}} = \frac{5/\sqrt{2}}{10 + 62.5116} = 48.758 \text{ (mA)} \\ \Rightarrow P_S &= v_{s(rms)} i_{s(rms)} = \left( \frac{5}{\sqrt{2}} \right) (48.758) = 172.386 \text{ (mW)} \end{aligned}$$

Hence the signal power gain of the amplifier is:

$$G_{power} = \frac{P_L}{P_S} = \frac{0.767}{172.386 \times 10^{-3}} = 4.45$$

### Part C. AC Load Line Analysis / Maximum Symmetrical Swing

9. For the circuit in Figure 9, the transistor parameters are  $\beta = 100$  and  $V_A = 100$  V. The values of  $R_C$ ,  $R_E$  and  $R_L$  are as shown in the figure. Design a bias-stable circuit to achieve the maximum undistorted swing in the output voltage if the total instantaneous C-E voltage is to remain in the range  $1 \leq v_{CE} \leq 8$  V and the minimum collector current is to be  $i_C(\min) = 0.1$  mA.

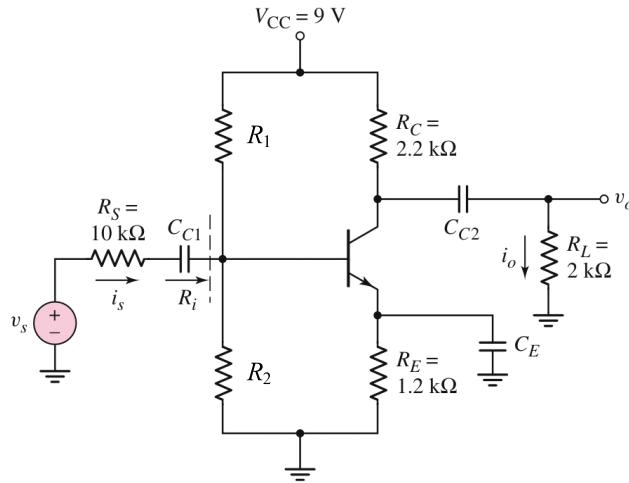


Figure 9

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

*Solution:*

To obtain a bias-stable circuit, let:

$$\begin{aligned} R_{TH} &= R_1 \parallel R_2 \\ &= \frac{1}{10} (1 + \beta) R_E = \left( \frac{101}{10} \right) (1.2) = 12.12 (\text{k}\Omega) \end{aligned}$$

The dc load line of the circuit is given by:

$$\begin{aligned} V_{CC} &= I_C R_C + V_{CE} + I_E R_E \\ &= I_C R_C + V_{CE} + \left( \frac{1 + \beta}{\beta} \right) I_C R_E \\ I_C &= -\frac{V_{CE}}{R_C + \left( \frac{1 + \beta}{\beta} \right) R_E} + \frac{V_{CC}}{R_C + \left( \frac{1 + \beta}{\beta} \right) R_E} = -0.2931 V_{CE} + 2.6377 \quad \dots(1) \end{aligned}$$

The ac load line of the circuit is given by:

$$\begin{aligned} v_{ce} + i_c (R_C \parallel R_L) &= 0 \\ i_c &= -\frac{v_{ce}}{R_C \parallel R_L} = -0.9545 v_{ce} \quad \dots(2) \end{aligned}$$

Given  $v_{CE(\min)} = 1 \text{ V}$  and  $i_{C(\min)} = 0.1 \text{ mA}$ , the maximum swing of  $v_{CE}$  and  $i_C$  from the  $Q$ -point ( $I_{CQ}$ ,  $V_{CEQ}$ ) would be:

$$\begin{aligned} |\Delta v_{CE(\max)}| &= V_{CEQ} - v_{CE(\min)} = V_{CEQ} - 1 \\ |\Delta i_{C(\max)}| &= I_{CQ} - i_{C(\min)} = I_{CQ} - 0.1 \end{aligned}$$

Since  $|\Delta v_{CE(\max)}|$  and  $|\Delta i_{C(\max)}|$  are related by the ac load line,


$$\begin{aligned} |\Delta i_C| &= 0.9545 |\Delta v_{CE}| \\ I_{CQ} - 0.1 &= 0.9545 (V_{CEQ} - 1) \\ I_{CQ} &= 0.9545 V_{CEQ} - 0.8545 \quad \dots(3) \end{aligned}$$

Solving (1) and (3) at the  $Q$ -point ( $I_{CQ}$ ,  $V_{CEQ}$ ):

$$\begin{aligned} 0.9545 V_{CEQ} - 0.8545 &= -0.2931 V_{CEQ} + 2.6377 \\ 1.2476 V_{CEQ} &= 3.4922 \\ V_{CEQ} &= 2.80 \text{ (V)} \\ I_{CQ} &= 1.817 \text{ (mA)} \end{aligned}$$

To decide the value for  $V_{TH}$ :
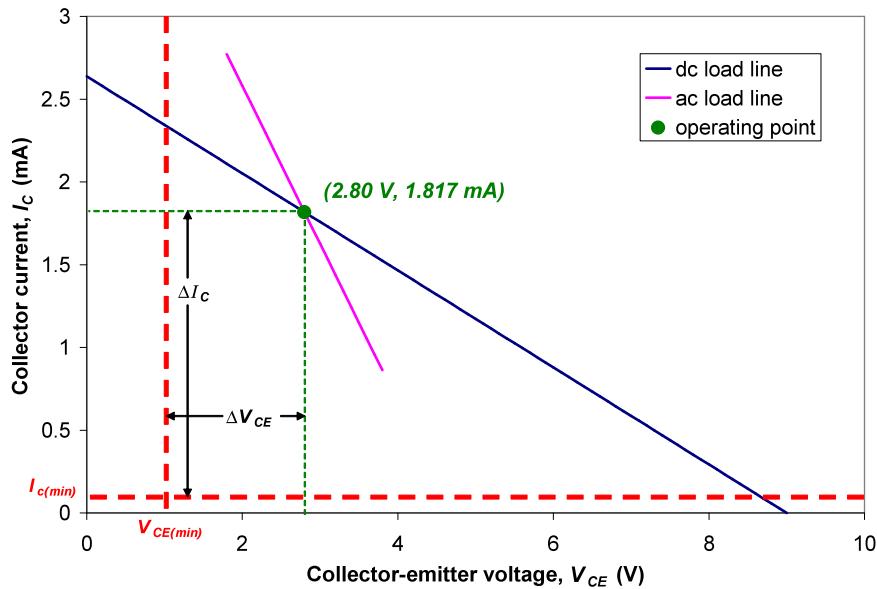
$$\begin{aligned}
 V_{TH} &= I_{BQ}R_{TH} + V_{BE(on)} + I_{EQ}R_E \\
 &= \left(\frac{1.817}{100}\right)(12.12) + 0.7 + \left(\frac{101}{100}\right)(1.817)(1.2) \\
 &= 3.122 \text{ (V)} \\
 &= \frac{R_2}{R_1 + R_2}V_{CC} = \frac{1}{R_1}(R_1 \parallel R_2)V_{CC} \\
 \Rightarrow R_1 &= 34.93 \text{ (k}\Omega\text{)} \quad R_2 = 18.56 \text{ (k}\Omega\text{)}
 \end{aligned}$$



10. In the circuit in Figure 10 with transistor parameters  $\beta = 180$  and  $V_A = \infty$ , design the bias resistors  $R_1$  and  $R_2$  to achieve maximum symmetrical swing in the output voltage and to maintain a bias-stable circuit. The total instantaneous C-E voltage is to remain in the range  $0.5 \leq v_{CE} \leq 4.5$  V and the total instantaneous collector current is to be  $i_C \geq 0.25$  mA.

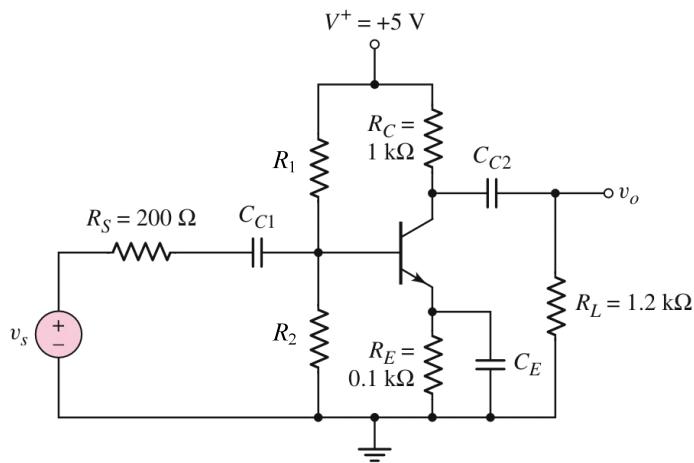


Figure 10

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

*Solution:*

To obtain a bias-stable circuit, let:

$$\begin{aligned} R_{TH} &= R_1 \parallel R_2 \\ &= \frac{1}{10}(1 + \beta)R_E = \left(\frac{181}{10}\right)(0.1) = 1.81 \text{ (k}\Omega\text{)} \end{aligned}$$

The dc load line of the circuit is given by:

$$\begin{aligned} V_{CC} &= I_C R_C + V_{CE} + I_E R_E \\ &= I_C R_C + V_{CE} + \left(\frac{1+\beta}{\beta}\right) I_C R_E \\ I_C &= -\frac{V_{CE}}{R_C + \left(\frac{1+\beta}{\beta}\right) R_E} + \frac{V_{CC}}{R_C + \left(\frac{1+\beta}{\beta}\right) R_E} = -0.9086 V_{CE} + 4.5432 \quad \dots(1) \end{aligned}$$

The ac load line of the circuit is given by:

$$\begin{aligned} v_{ce} + i_c (R_C \parallel R_L) &= 0 \\ i_c &= -\frac{v_{ce}}{R_C \parallel R_L} = -1.8333 v_{ce} \quad \dots(2) \end{aligned}$$

Given  $v_{CE(\min)} = 0.5$  V and  $i_{C(\min)} = 0.25$  mA, the maximum swing of  $v_{CE}$  and  $i_C$  from the  $Q$ -point ( $I_{CQ}$ ,  $V_{CEQ}$ ) would be:

$$\begin{aligned} |\Delta v_{CE(\max)}| &= V_{CEQ} - v_{CE(\min)} = V_{CEQ} - 0.5 \\ |\Delta i_{C(\max)}| &= I_{CQ} - i_{C(\min)} = I_{CQ} - 0.25 \end{aligned}$$

Since  $|\Delta v_{CE(\max)}|$  and  $|\Delta i_{C(\max)}|$  are related by the ac load line,

$$\begin{aligned} |\Delta i_C| &= 1.8333 |\Delta v_{CE}| \\ I_{CQ} - 0.25 &= 1.8333 (V_{CEQ} - 0.5) \\ I_{CQ} &= 1.8333 V_{CEQ} - 0.6667 \quad \dots(3) \end{aligned}$$

Solving (1) and (3) at the  $Q$ -point ( $I_{CQ}$ ,  $V_{CEQ}$ ):

$$\begin{aligned} 1.8333 V_{CEQ} - 0.6667 &= -0.9086 V_{CEQ} + 4.5432 \\ 2.7419 V_{CEQ} &= 5.2099 \\ V_{CEQ} &= 1.90 \text{ (V)} \\ I_{CQ} &= 2.817 \text{ (mA)} \end{aligned}$$

To decide the value for  $V_{TH}$ :

$$\begin{aligned}
 V_{TH} &= I_{BQ}R_{TH} + V_{BE(on)} + I_{EQ}R_E \\
 &= \left( \frac{2.817}{180} \right)(1.81) + 0.7 + \left( \frac{181}{180} \right)(2.817)(0.1) \\
 &= 1.012 \text{ (V)} \\
 &= \frac{R_2}{R_1 + R_2}V_{CC} = \frac{1}{R_1}(R_1 \parallel R_2)V_{CC} \\
 \Rightarrow R_1 &= 8.95 \text{ (k}\Omega\text{)} \quad R_2 = 2.27 \text{ (k}\Omega\text{)}
 \end{aligned}$$

