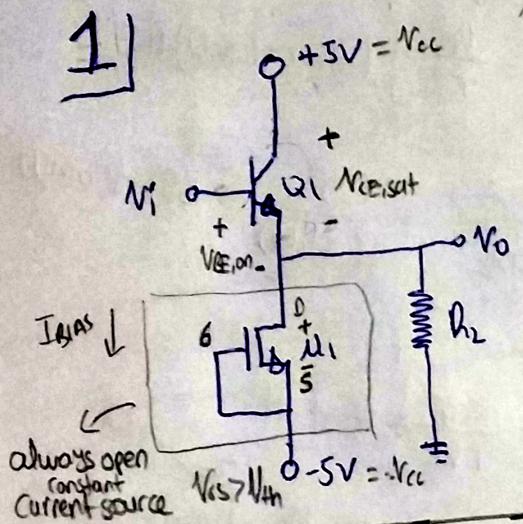


# EHB-335E / HMW #4

1)



$$V_{BE, on} = 0.7V$$

$$V_{CE,sat} = 0.2V$$

$$N_{th} = -1.8V$$

$$k_n = \frac{1}{2} m_n C_{ox} = \frac{12 \text{ mA}}{\text{V}^2}$$

$$\begin{aligned} N_A &= \infty \\ \lambda &= 0 \end{aligned} \quad \left. \begin{array}{l} \text{no transistor} \\ \text{output impedance} \end{array} \right\}$$

$$\begin{aligned} \text{a) } V_{cc} - V_{CE,sat} &= V_o, \max \quad (\text{At the edge of saturation}) \\ -V_{cc} + V_{ov,1} &= V_o, \min_1 \quad (\text{At the edge of triode}) \\ -I_{BIAS} R_L &= V_o, \min_2 \quad (\text{Q}_1 \text{ off}) \quad V_{DD} = 16V \end{aligned}$$

$$\Rightarrow V_o, \max = 5V - 0.2V = 4.8V$$

$$I_{BIAS} = k_n (V_{BS} - V_{th})^2 = \left( \frac{12 \text{ mA}}{\text{V}^2} \right) \cdot (1.8V)^2 = 12 \cdot (1.8)^2 \text{ mA} = 38.88 \text{ mA}$$

$$\rightarrow \text{For } V_{min}$$

$$\bullet V_{min,1} = -V_{cc} + V_{ov} = -V_{cc} + (V_{BS} - V_{th}) = -5V + 1.8V = -3.2V$$

$$\bullet V_{min,2} = -I_{BIAS} R_L$$

$$\text{i) For } R_L = \infty \quad (\text{open-circuit})$$

$$V_{min} = -3.2V$$

$$\text{ii) For } R_L = 600\Omega = 0.6k\Omega \Rightarrow V_{min,2} = -(38.88)(0.6) = -15.552V$$

$$V_{min} = -3.2V$$

- b) Since  $M_1$  is a constant current source, the maximum current that can flow through the load resistance is equal to the bias current, it is achieved if  $Q_1$  is in cut-off

Then,

$$I_{BIAS} = \frac{V_{out}}{R_L} = \frac{V_{BS} - V_{th}}{R_{L,\min}} \Rightarrow R_{L,\min} = \frac{|V_P|}{I_{BIAS}} = \frac{2V}{38.88 \text{ mA}} = 51.64 \Omega$$

C) What is power efficiency?

Given stage is an example of class-A output stage.

$$P_{avg,L} = \frac{1}{T} \int_0^T (V_{out}) \cdot \frac{V_{out}}{R_L} dt = \frac{V_p^2}{T R_L} \int_0^T \sin^2 \omega t dt = \frac{V_p^2}{T R_L} \int_0^T \left( \frac{1}{2} - \cos(2\omega t) \right) dt$$

$(V_{out} = V_p \sin \omega t)$

$$P_{avg,L} = \frac{V_p^2}{T R_L} \cdot \frac{T}{2} - \frac{V_p^2}{T R_L} \int_0^T \cos(2\omega t) dt = \frac{V_p^2}{2 R_L} = \frac{(2)^2}{2(51.46)} = 38.88 \text{ mW}$$

$$P_{avg,V^+} = \frac{1}{T} \int_0^T (I_{BIAS} + i_{RL}) V_{cc} dt = I_{BIAS} V_{cc} + \frac{V_{cc}}{T R_L} \int_0^T V_{out} dt$$

$$P_{avg,V^+} = I_{BIAS} V_{cc} + \frac{V_{cc}}{T R_L} \int_0^T V_p \sin \omega t dt = I_{BIAS} V_{cc} + \frac{V_{cc} \cdot V_p}{T R_L} \int_0^T \sin \omega t dt$$

$$P_{avg,V^+} = I_{BIAS} V_{cc} = (38.88) (5)$$

$$P_{avg,V^-} = I_{BIAS} V_{cc}; \quad P_{avg,V^-} = I_{BIAS} V_{cc} = (38.88) (5)$$


$$\eta = \frac{P_{avg,L}}{P_{avg,V^+} + P_{avg,V^-}} = \frac{P_{avg,L}}{2 P_{avg,V^-}} = \frac{38.88 \text{ mW}}{2(38.88)(5) \text{ mW}} = \frac{1}{10} = 10\%$$

$\Rightarrow$  Since this is a class-A output stage, 10% power conversion efficiency is not surprising.

Class-AB (Assume all transistors are matched)

$$V_+ = -V_- = 12 \text{ V}; \quad \beta = 40; \quad V_{BE} = 0.7; \quad R_1 = R_2 = 250 \Omega$$
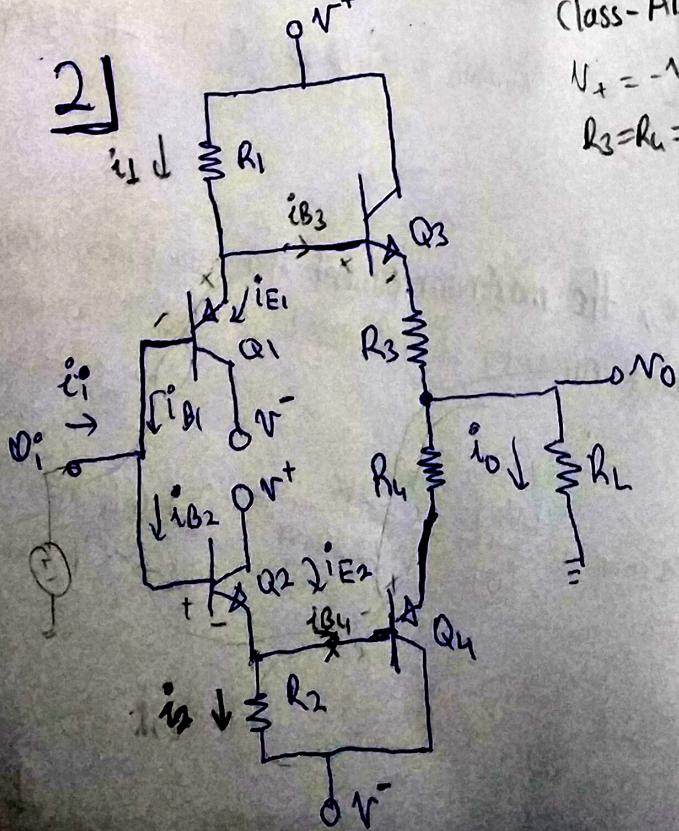
$$R_3 = R_4 = 0 \Omega; \quad R_L = 8 \Omega$$



a) for  $V_i = 0 \text{ V}$

$$(i_1 + V_{EB1} - V_{BE3} - V_0) = 0$$

$$i_1 = V_0 = 0 \Rightarrow i_0 = \frac{V_0}{R_L} = 0$$

$$i_1 = \frac{V_+ - V_{BE1}}{R_1} = \frac{12 - 0.7}{250} = 45.2 \text{ mA}$$

$$i_2 = \frac{-V_{EB2} - (V^-)}{R_2} = \frac{12 - 0.7}{250} = 45.2 \text{ mA}$$

$$i_{E3} = i_0 = 0 \Rightarrow$$

$$\Rightarrow i_{E3} = i_0 = 0A \Rightarrow i_{B3} = 0 \Rightarrow i_1 = i_{B1} = 45.2mA$$

$$i_{B1} = i_{E1} / (\beta + 1) = 45.2 / 41 = 1.1mA$$

and since  $i_{E3} = i_0 + i_{E4} \Rightarrow i_{E4} = 0 \Rightarrow i_{B4} = 0 =$

$$i_{B4} = 0 \Rightarrow i_2 = i_{E2} = 45.2mA \Rightarrow i_{B2} = \frac{45.2mA}{41} = 1.1mA$$

$$\Rightarrow \boxed{i_{E1} = 45.2mA} ; \boxed{i_{E2} = 45.2mA} ; \boxed{i_{B1} = 1.1mA} ; \boxed{i_{B2} = 1.1mA}$$

b) for  $V_i = 5V$

we know that  $0i + U_{eb1} - U_{eb3} - V_o = 0 \Rightarrow V_i = V_o = 5V$

Assume  $i_{E3} = i_0 = \frac{V_o}{R_L} = \frac{5V}{8\Omega} = 0.625A \Rightarrow i_{B3} = \frac{i_{E3}}{\beta + 1} = \frac{0.625}{41} = 15.2mA$

$$i_1 = i_{E1} + i_{B3} \Rightarrow i_{E1} = i_1 - i_{B3} = \frac{N^+ - (V_i + U_{eb1})}{R_1} - i_{B3}$$

$$i_{E1} = \frac{12 - 5.7}{250} - 15.2mA = 9.96mA$$

$$i_{E3} = i_0 \Rightarrow i_{E4} = 0 \Rightarrow i_{B4} = 0$$

$$i_{E2} = i_2 = \frac{(V_i - U_{EB2}) - V}{R_2} = 65.2mA$$

$$i_{B2} = \frac{i_{E2}}{\beta + 1} = \frac{65.2}{41} = 1.6mA$$

$$i_{B1} = \frac{9.96}{41} = 0.243mA$$

$$i_{in} = 1.347mA$$

$$i_0 = 0.625A$$

$$i_{E1} = 9.96mA$$


$$i_{E2} = 65.2mA$$

$$i_{B2} = 1.6mA$$

$$i_{B1} = 0.243mA$$

c) Current gain is calculated  $A_i = \frac{i_{out}}{i_{in}} = \frac{i_0}{i_{in}} = \frac{0.625A}{1.347mA} = 463.994$

3)

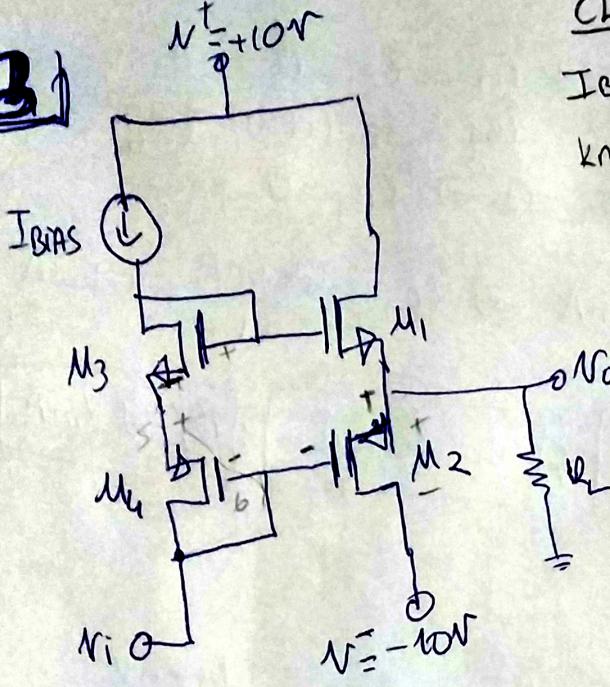CLASS AB

$$I_{BIAS} = 0.2 \text{ mA}, R_L = 1 \text{ k}\Omega, V_{th,n} = 0.8 \text{ V}$$

$$k_n^l = 100 \mu\text{A/V}^2, V_{th,p} = -0.8 \text{ V}, k_p^l = 40 \text{ mA/V}^2$$

$$V_{GS,3} = V_{GS,4}; V_{GS,2} = V_{GS,1}; \beta = 0$$

$$a) V_i = -1.5 \text{ V}; V_o = 0 \text{ V} \quad i_{D1} = i_{D2} = 0.5 \text{ mA}$$

$$V_i + V_{GS,4} + V_{GS,3} - V_{GS,1} = V_o$$

$$-1.5 + 2V_{GS,3} - V_{GS,1} = 0 \text{ V}$$

$$2V_{GS,3} - V_{GS,1} = 1.5 \text{ V}$$

$$2V_{GS,3} = 3 \text{ V}$$

$$V_{GS,3} = 1.5 \text{ V}$$

$$V_i + V_{GS,2} = V_o \Rightarrow V_{GS,2} = -V_i$$

$$V_{GS,2} = 1.5 \text{ V}$$

$$\text{For } M_1 \text{ and } M_2 \quad i_{D1} = i_{D2} = 0.5 \text{ mA}$$

$$5 \times 10^{-3} = (0.5) (10^4 \frac{\text{A}}{\text{V}}) (\frac{w}{L})_1 (1.5 - 0.8)^2 \Rightarrow (\frac{w}{L})_1 = 20.4$$

$$5 \times 10^{-3} = (0.5) (4 \times 10^3 \frac{\text{A}}{\text{V}}) (\frac{w}{L})_2 (1.5 - 0.8)^2 \Rightarrow (\frac{w}{L})_2 = 51.02$$

$$\text{For } M_3 \text{ and } M_4 \quad I_{D3} = I_{D4} = I_{BIAS} = 0.2 \text{ mA}$$

$$2 \times 10^{-3} = (0.5) (10^4 \frac{\text{A}}{\text{V}}) (\frac{w}{L})_3 (1.5 - 0.8)^2 \Rightarrow (\frac{w}{L})_3 = 8.16$$

$$2 \times 10^{-3} = (0.5) (4 \times 10^5 \frac{\text{A}}{\text{V}}) (\frac{w}{L})_4 (1.5 - 0.8)^2 \Rightarrow (\frac{w}{L})_4 = 20.4$$

$$b) \frac{V_{o,max}}{V_{o,min}}$$

$$V_{o,max} = V^+ - V_{ov1} = V^+ - (V_{GS1} - V_{th,n}) = 10 \text{ V} - (0.7 \text{ V}) = 9.3 \text{ V}$$

$$V_{o,max} = V^+ - V_{IBIAS} - V_{GS,1} = 10 - (0.2 + 1.5 \text{ V}) = 8.3 \text{ V}$$

$$\text{then } V_{o,max} = 8.3 \text{ V}$$

$$\frac{V_{o,min}}{V_{o,max}}$$

$$V_{o,min} = V_{in} + V_{GS2} = (-1.5 \text{ V}) + (1.5 \text{ V}) = 0$$

$$V_{o,min} = V^- + V_{GS1} = V^- + (V_{GS} - |V_{th}|) = -10 \text{ V} + (1.5 - 0.8 \text{ V}) = -9.3 \text{ V}$$

$$\text{then } V_{o,min} = 0 \text{ V}$$

$$0 \text{ V} \leq V_o \leq 8.3 \text{ V}$$