

# Homework - 1



## Solutions

1-a) The circuit  
 is an active loaded  
 cascode amplifier besides  $R_P$ ,  
 $R_P$  is parallel to  $r_{o2}$ .

$$r_{o2}' = R_P \parallel r_{o2} = \frac{R_P r_{o2}}{R_P + r_{o2}}$$


$$\begin{aligned} \text{Gain} &= -g_{m1} R_{out} \\ R_{out} &\approx (r_{o4} \cdot g_{m3} r_{o3}) \parallel (r_{o1} g_{m2} r_{o2}') \\ &= \frac{g_{m3} r_{o3} r_{o4} \cdot g_{m2} r_{o1} \frac{R_P r_{o2}}{R_P + r_{o2}}}{g_{m3} r_{o3} r_{o4} + g_{m2} r_{o1} \frac{R_P r_{o2}}{R_P + r_{o2}}} \end{aligned}$$

1-a (cnt)

$$= \frac{g_{m_2} g_{m_3} r_{o_1} r_{o_2} r_{o_3} r_{o_4} R_p}{g_{m_3} r_{o_3} r_{o_4} (R_p + r_{o_2}) + g_{m_2} r_{o_1} r_{o_2} R_p}$$

$$G_{ol:n} = -g_{m_1} \frac{g_{m_2} g_{m_3} r_{o_1} r_{o_2} r_{o_3} r_{o_4} R_p}{g_{m_2} r_{o_3} r_{o_4} (R_p + r_{o_2}) + g_{m_2} r_{o_1} r_{o_2} R_p}$$

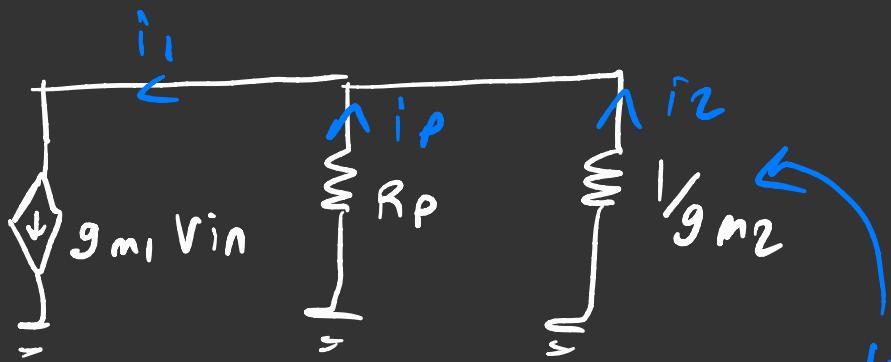- For this circuit  $G_m = g_{m_1}$
  - Do not forget  $180^\circ$  phase!
- 1-b) In the circuit small signal current is created by  $M_1$ . However this current is shared by  $M_2$  and  $R_p$ . Please see equivalent circuit.



resistance seen by source of  $M_2$

$M_2$  is common gate amplifier,  
behaves as current buffer  
and buffers  $i_2$  to  $i_{out}$ .

$$i_2 = \frac{V_{in} g_{m1} R_P}{\frac{1}{g_{m2}} + R_P}$$

$$= \frac{v_{in} g_{m1} g_{m2} R_P}{g_{m2} R_P + 1}$$

$$i_{out} = i_2 \quad (\text{current buffering})$$

$$G_m = \frac{i_{out}}{V_{IN}}$$

$$G_m = \frac{g_m (g_m R_p)}{g_m R_p + 1}$$

$$\text{Gain} = - G_m R_{out}$$


$$R_{out} = r_{o4} g_m r_{o3}$$

& we neglect the contribution of lower side of the circuit on output resistance as  $\lambda_1 = \lambda_2 = 0$

$$G_{m1} = -\frac{g_{m1} g_{m2} g_{ms} R_{os} R_{oy} R_P}{g_{m2} R_P + L}$$

The difference between  
 1-a and 1-b that  $G_{ms}$   
 of the overall circuit  
 are different. In 1-b  
 $R_P$  changes  $G_m$ !

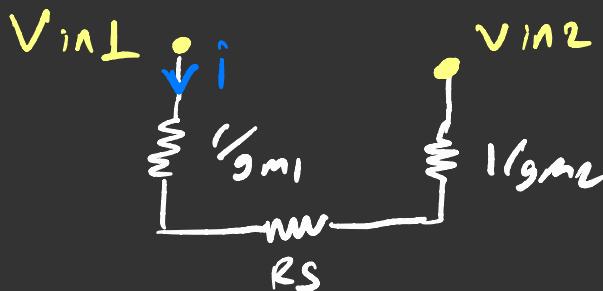2) Due to  $R_s$ , we need to calculate  $gm$  of the circuit.



$$\text{Assume } \frac{1}{g_{m1}} = \frac{1}{g_{m2}}$$

$$i = \frac{V_{in1} - V_{in2}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}} + R_s}$$

This current also flows through  $\text{Q}_3 - \text{Q}_4$  as they are current buffers. (Common-base config.)

$V_{in} - V_{in2} = V_{id}$  a differential input signal

$$i = \frac{V_{id} g_{m1,2}}{g_{m1,2} R_s + 2}$$

How about the output?



Let's assume that circuit is fully symmetrical so  $R_{out1} = R_{out2}$

$$V_{out1} = -i \cdot R_{out1,2}$$

$$V_{out2} = i \cdot R_{out1,2}$$

$$V_{out} = V_{out2} - V_{out1} = 2i \cdot R_{out1,2}$$


$$V_{out} = \frac{2Vi + g_{m1,2}}{g_{m1,2} R_S + 2} \cdot R_{out1,2}$$

$$\frac{V_{out}}{Vi} = \text{Gain} = \frac{2g_{m1,2}}{g_{m1,2} R_S + 2} \cdot \underbrace{\frac{R_{out1,2}}{g_m}}$$

$\underbrace{\hspace{1cm}}_{R_{out}}$

So what about  $R_{out1,2}$ ?

We can use half-equivalent circuit

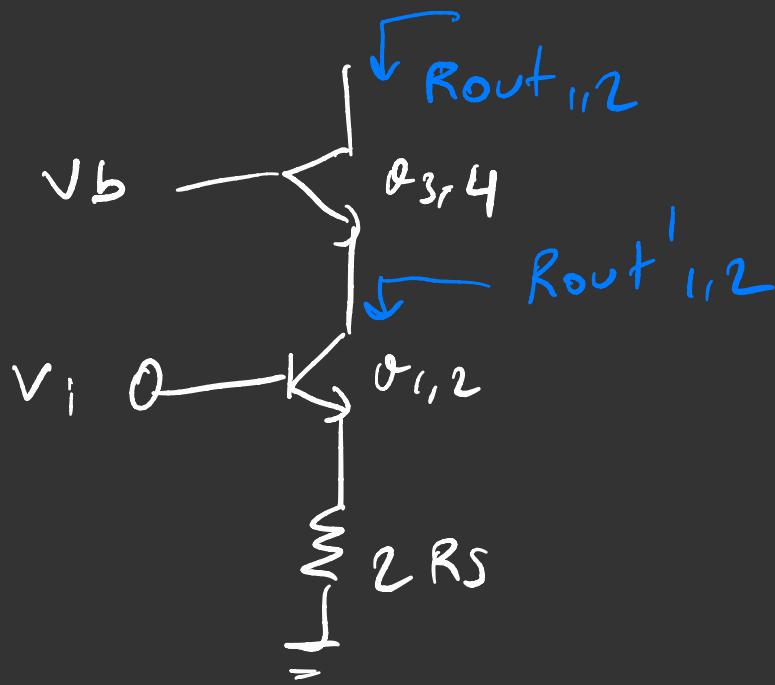

$$R_{out,1,2} = g_{m1} r_{o1} \left( 2 R_S \parallel r_{\pi1} \right)$$


$$R_{out,1,2} = \left( R_{out,1,2} \parallel r_{\pi3} \right) g_{m3} r_{o3}$$

$$R_{out,1,2} = \left[ \left( g_{m1} r_{o1} \left( 2 R_S \parallel r_{\pi1} \right) \right) \parallel r_{\pi3} \right] g_{m3} r_{o3}$$

$R_{out}$

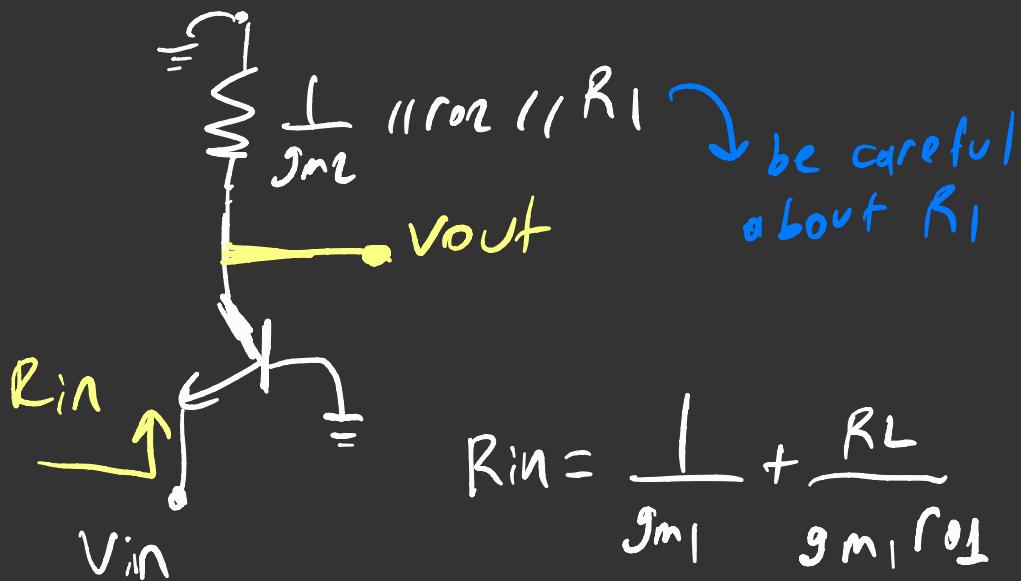3)  $C_B$  pulls base  
of  $\text{Q}_1$  to ground and  
shorts  $R_2$ . (in AC)

Let's simplify the  
circuit for small signal.



$$R_{in} = \frac{1}{g_m 1} + \frac{R_L}{g_m 1 r_{o1}}$$

where

$$R_L = \frac{1}{g_m 2} \parallel r_{o2} \parallel R_1$$

$$R_{in} = \frac{1}{g_{m1}} + \frac{\frac{1}{g_{m2}} // R_2 // R_1}{g_{m1} R_{o1}}$$

$$G_{ain} = g_m R_{out}$$

$$R_{out} = R_L // R_{o1}$$

$$G_m = g_{m1}$$

$$G_{ain} = g_{m1} \left( \frac{1}{g_{m2}} // R_{o1} // R_2 // R_1 \right)$$

\* No phase inversion in  
common base amplifier !

#### 4) Key points for the design.

- Choose a proper common mode DC voltage otherwise the circuit won't amplify the signal.
- Since the circuit has perfect symmetry  $R_1 = R_2$  and it is the only design parameter as  $V_{CC}$ ,  $I_{EC}$  predefined. You cannot change the parameters of BJT

\* How to maximize gain?


Since  $G_m$  of the circuit  
 $g_{m1,2}$ , you should maximize  
Rout. It's a SPICE question,

so you can use SPICE or  
an optimizer too!. For ex.  
you can use single frequency  
with sweeping  $R_{1,2}$  and  
you can choose the value.

Please see other page  
regarding this!



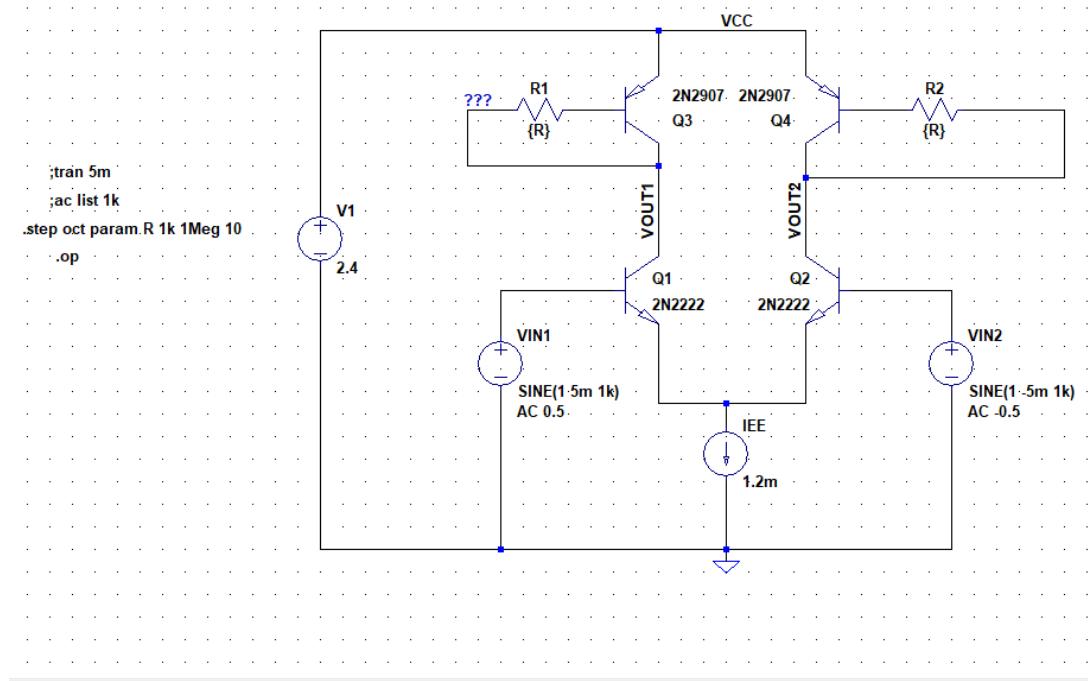
The schematic is given in below. I chose 1V common mode DC voltage. You can choose another reasonable value for common mode voltage.



Please analyze schematic,


- We have sinusoidal sources with 1V offset (DC Common Mode), 10 mV differential signal @ 1kHz (for transient analysis) and 1V differential AC signal (for AC analysis)
- We defined a parameter {R} in order to sweep it to obtain maximum gain.
- We have “ac list 1k” command to choose single frequency. We are going to observe gain vs R1,2 @ 1kHz.
- “.step oct param R 1k 1Meg 10” command sweeps the design variable R, 1k to 1M.

The sweep result is given below.

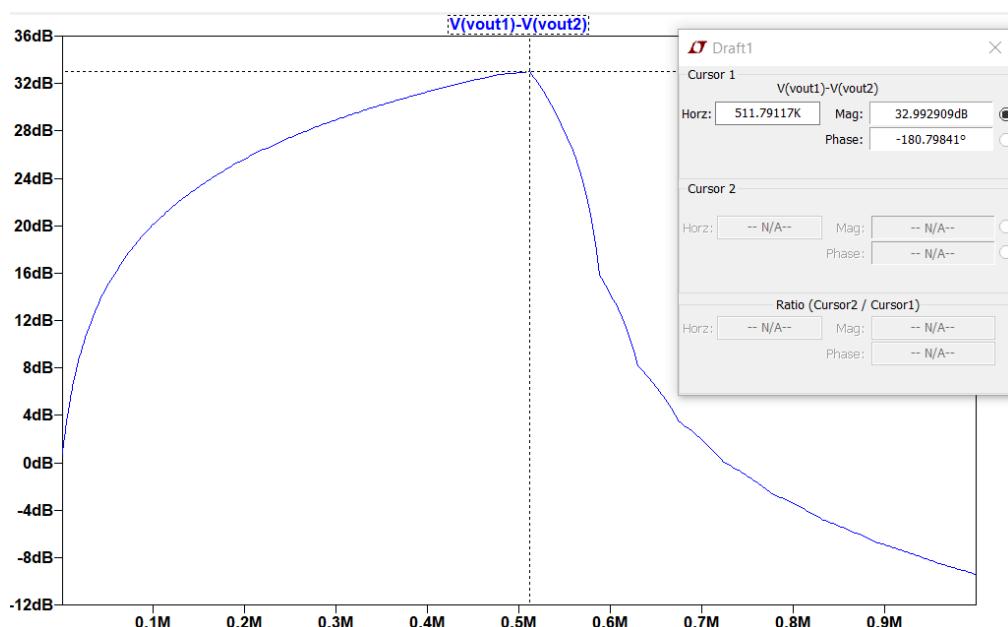

The result shows us the optimal value of  $R$  is equal to  $511 \text{ k}\Omega$ . After this point we can continue with this value.

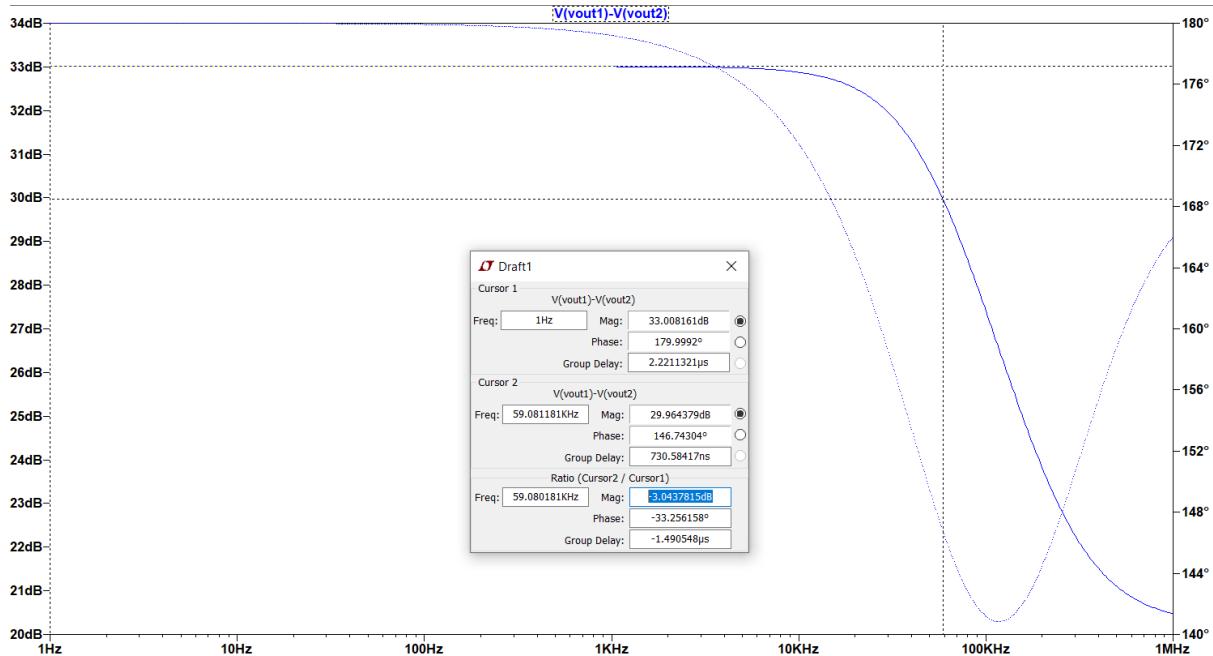The traditional AC simulation between 1 Hz and 1 MHz is given below. This is essentially a Bode plot. The gain is 33 dB and 3 dB frequency is around 60 kHz. Discuss why the circuit does not have any low frequency pole?



The transient analysis results are given below. Observe the DC common mode input-output voltages from these waveforms. Observe differential signals. For 10 mV differential input signal we have 360 mV differential output voltage. The gain is equal to 31V/V. It is not exactly the same as AC simulation results! (Why?)

