

Homework - 5 Solutions




1) Labelling the drain of M_2
or gate of M_3 as "X",
let's assume,
 $V_{in} \uparrow, X \uparrow, V_{out} \uparrow$
As a result of this, the difference
between the input terminals of
differential amplifier will decrease
and the feed back will stabilize
node X and V_{out} . The system
has the "negative feedback".

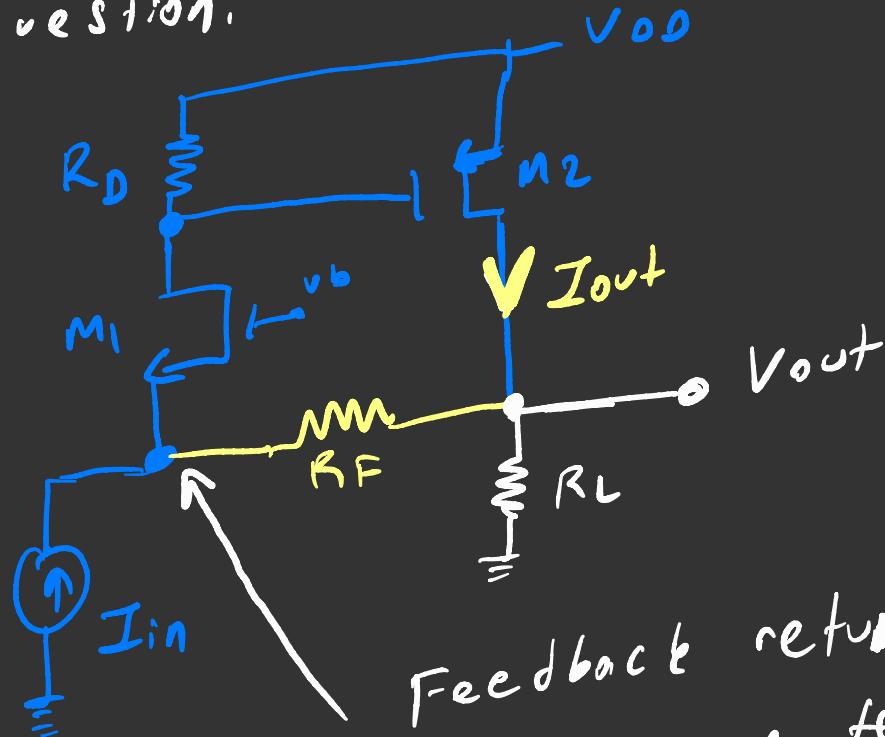2) Discussion about the feedback

→ It is relatively easy to find out which kind of feedback is employed at the input. If the feedback path returns to the same terminal with the input it is "parallel (shunt) input feedback". If the feedback returns to a different terminal it is "series input feedback". However, for the output the kind of feedback depends on which signal we are processing.

Thus, output feedback depends on the application. Let's discuss our circuit in the question.




Feedback returns to the same terminal (source of M_1).

The conclusion we have
shunt feedback
at the input.


Input current signal also is applied at the same place.

→ For the output we have two options. I_{out} or V_{out} . In the question, it is specifically expressed that collector current I_C or v_{out} will be processed. However, do not forget that we also could have selected V_{out} .
→ The output is current thus it is "series output feedback".

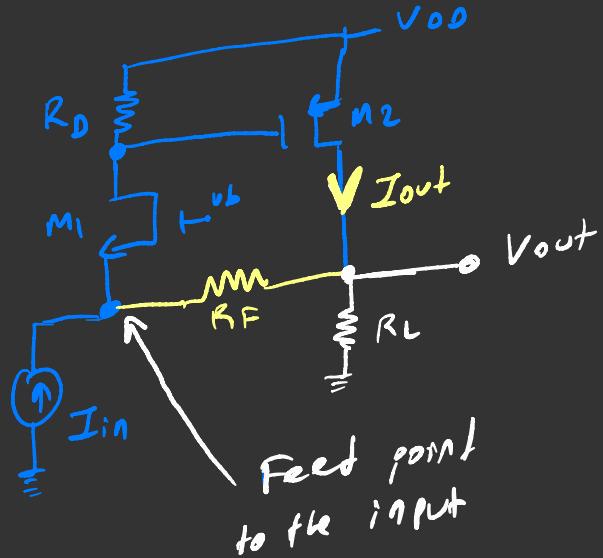A overall, we have shunt-series (current-current) feedback




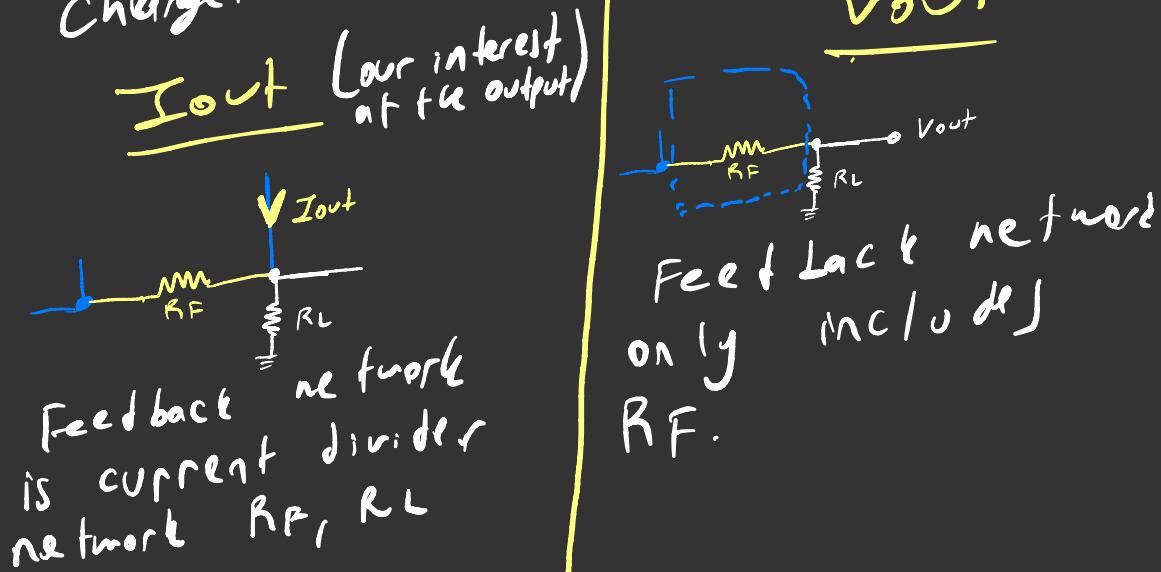So, what does it change according to the output feedback. The feedback network will change.




Let's go back to question.
My suggestion for feedback question.

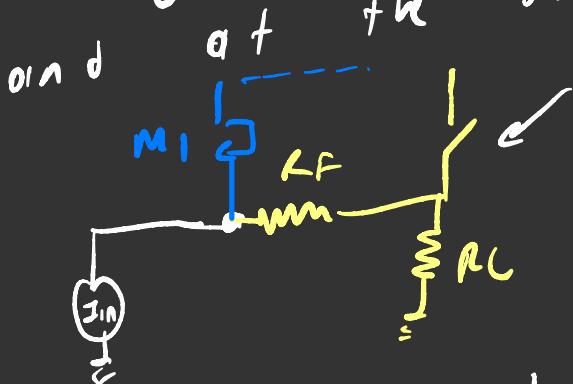- Always determine the feedback (we have current-current or shunt-series feedback)
- Solve the system for loop. we need to open find $\frac{I_{out}(OL)}{Z_{in}}$. Include loading effects at the output.




(Input loading)

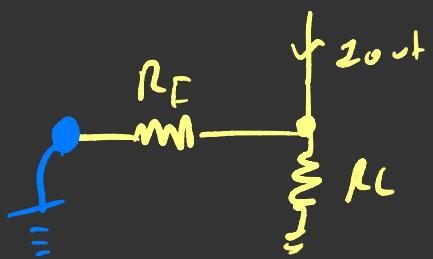Since we have series feedback at the output, we need to set open circuit.



Since we have shunt feedback at the input we need to set short circuit.

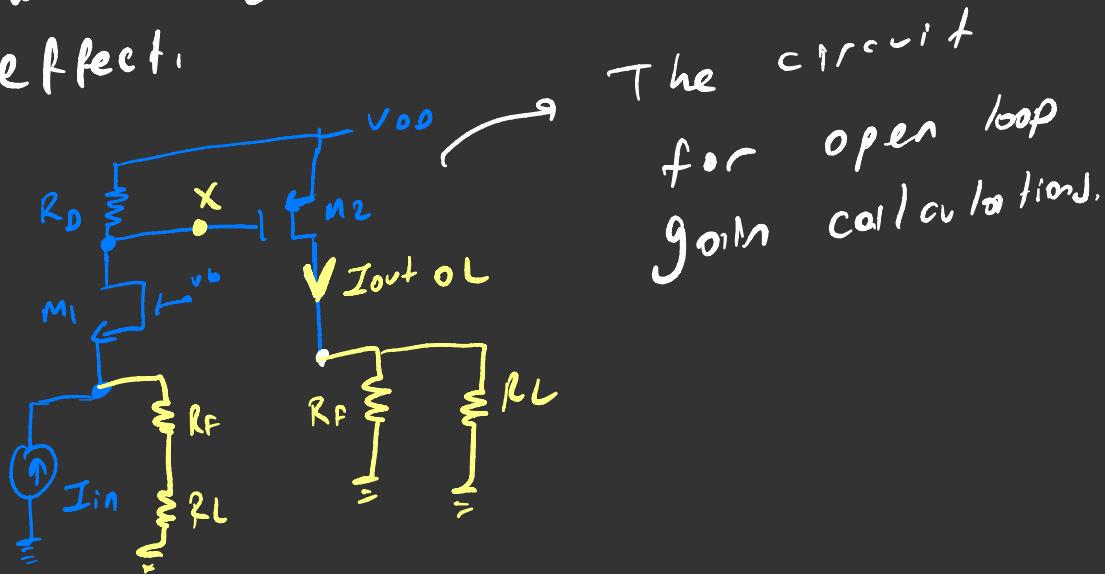As a rule apply short circuit for shunt feedback, apply open feedback for series feedback when you are dealing with loading effect.



$$I_{in} \cdot \frac{R_F + R_L}{1 + R_F + R_L} \cdot R_D \cdot g_m 2 = I_{out_{OL}}$$

Current divider at input
 $\frac{g_m 1}{1 + R_F + R_L}$
 Converts I_{in} to V_x at X
 Converts V_x to $I_{out_{OL}}$

$$\frac{I_{out_{OL}}}{I_{in}} = A_{OL} = \frac{R_F + R_L}{1 + R_F + R_L} \cdot R_D \cdot g_m 2$$


Find open loop input -
 output resistances
 $R_{in} = \frac{1}{g_m 1} \parallel (R_F + R_L)$

$$R_{in} = \frac{1}{g_m 1} \parallel (R_F + R_L)$$

$$R_{out} = \infty$$

because $V_A = \infty$
 for both transistors

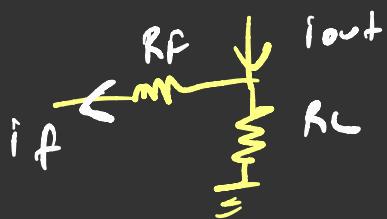..... Find β factor from feedback network



$$\frac{i_F}{I_{out}} = \frac{R_L}{R_F + R_L}$$

current divider

..... Find loop gain $A\beta$

$$\frac{R_F + R_L}{\frac{1}{g_m_1} + R_F + R_L} \cdot R_O \cdot g_{m_2} \cdot \frac{R_L}{R_F + R_L} = A\beta$$

$$= \frac{g_{m_2} R_O R_L}{\frac{1}{g_{m_1}} + R_F + R_L} \rightarrow \text{loop gain}$$

Find closed

.....

loop parameters.

$$A_{CL} = \frac{I_{out}}{I_{in}} =$$

$$\frac{\frac{R_F + R_L}{L + R_F + R_L} \cdot R_D \cdot g_m 2}{g_m 1}$$

$$1 + \frac{g_m 2 \ R_D \ R_L}{\frac{1}{g_m 1} + R_F + R_L}$$

Comment


$$\uparrow I_T \text{ goes to } \frac{R_F + R_L}{R_L} \text{ if } A_F \gg 1$$

$$R_{in} = \frac{1}{g_m 1} \parallel (R_F + R_L)$$

$$1 + \frac{g_m 2 \ R_D \ R_L}{\frac{1}{g_m 1} + R_F + R_L}$$

$$R_{out} = R_D$$


3) we will apply the steps
Question - 2.

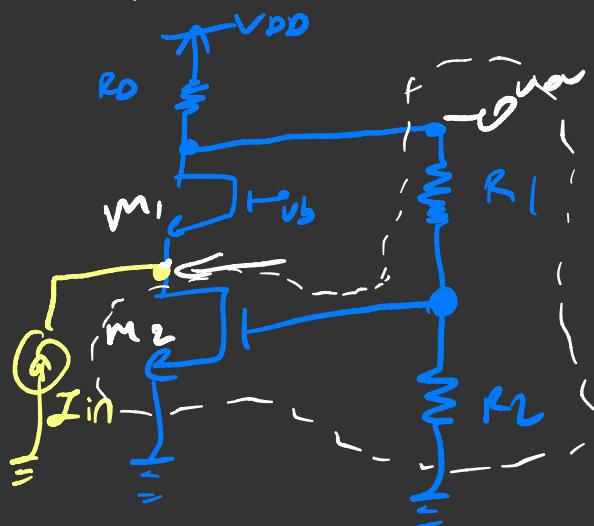

- Input feedback is parallel (shunt)
- Output is also parallel as we are processing V_{out} .

V_{out} is shunt + shunt.

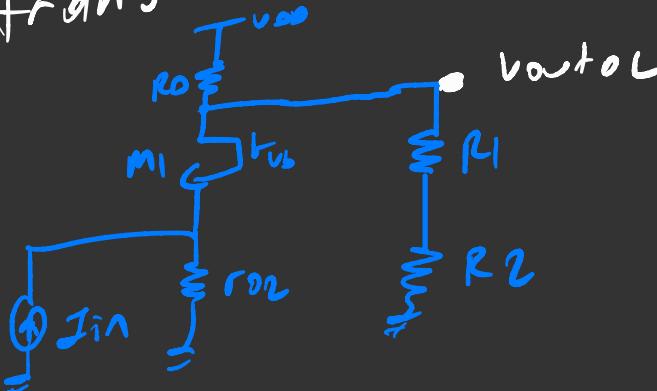- The feedback is calculation of open loop gain $\frac{V_{out}}{I_{in}}$.
- Transistor resistance gain



In open-loop signal cannot travel through drain of M₂ to gate of M₂. This is why R₁ and R₂ do not load the input.

current divider at input

$$I_{in} \cdot \frac{R_{O2}}{R_{O2} + \frac{R_x + R_O}{g_m, R_O}}$$

current divider output (A_o)

$$\frac{R_{O2} g_m R_O}{R_x + R_O g_m R_O}$$

convert I_{outOL} to V_{outOL}

$$R_x = R_O + R_1 // R_2$$

$$R_{inOL} = R_{O2} // \frac{R_x + R_O}{g_m, R_O}$$

↳ open loop input + red.

$$R_{out,OL} = R_x \parallel r_{o2} g_m, r_{o1}$$

↳ open loop output res.

$$\text{Let's call } g_m, r_{o1}, r_{o2} = R_y$$


Summarize

$$A_{OL} = \frac{V_{out,OL}}{I_{in}} = \frac{r_{o2}}{r_{o2} + \frac{R_x + r_{o1}}{g_m r_{o1}}} \cdot \frac{R_y - R_x}{R_y + R_x}$$

$$R_{in,OL} = r_{o2} \parallel \frac{R_x + r_{o1}}{g_m r_{o1}}$$

$$R_{out,OL} = R_x \parallel g_m, r_{o1}, r_{o2}$$

Let's zoom in to the feedback network.

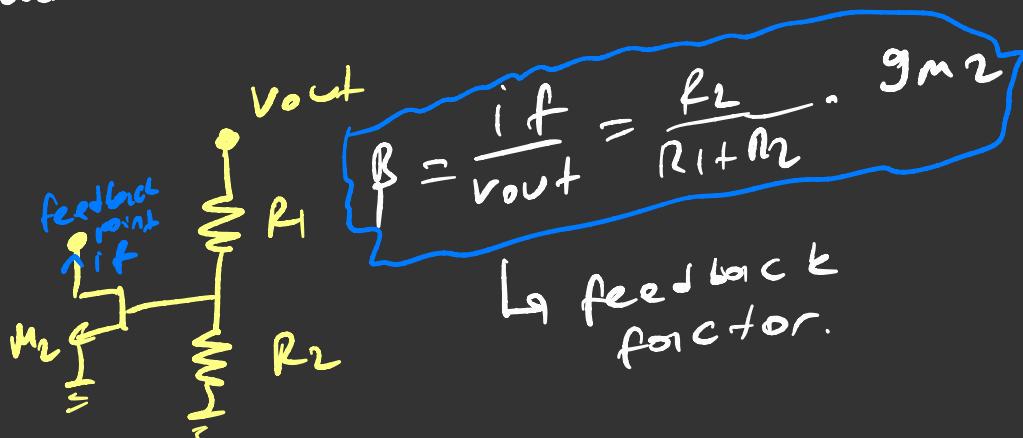

→ Loop gain

$$A\beta = \frac{r_{o2}}{r_{o2} + \frac{R_x + r_{o1}}{g_m r_{o1}}} \cdot \frac{R_y}{R_y + R_x} - R_x \cdot \frac{R_2}{R_1 + R_2} \cdot g_m 2$$

→ Closed loop gain.

$\frac{A}{1 + A\beta}$ = just put the expression
I won't write to here :D

$$R_{in} = \frac{R_{inoc}}{1 + A\beta}, \quad R_{out} = \frac{R_{outc}}{1 + A\beta}$$


3) when you apply shunt-shunt feedback both input and output resistances will decrease by $1 + A\beta$

4) It is a series-shunt circuit.
feed back
Please see next - page
for simulations.




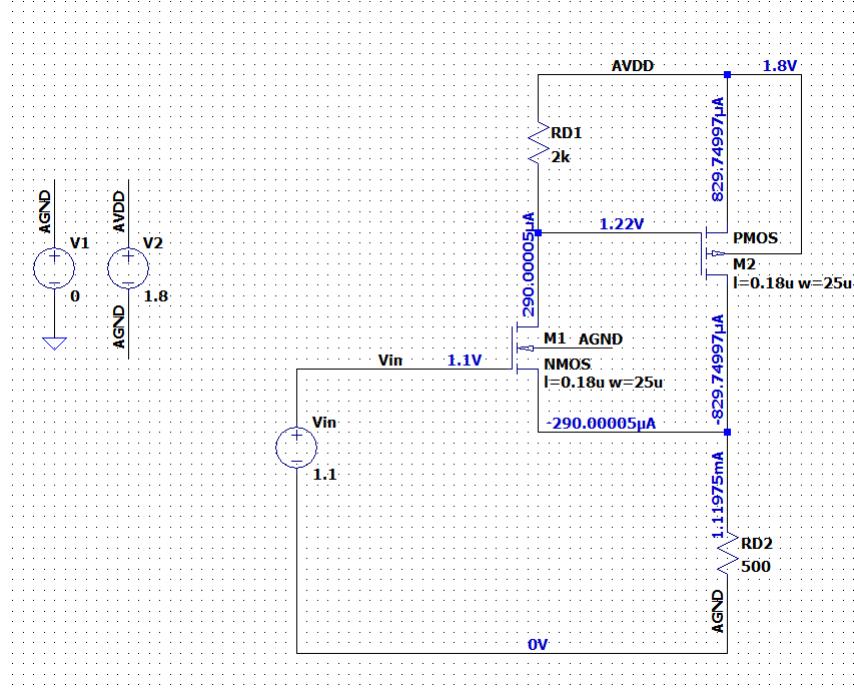QUESTION-4 (LTSPICE SOLUTIONS)


The circuit schematic and DC operating points can be seen below. (5 pts)



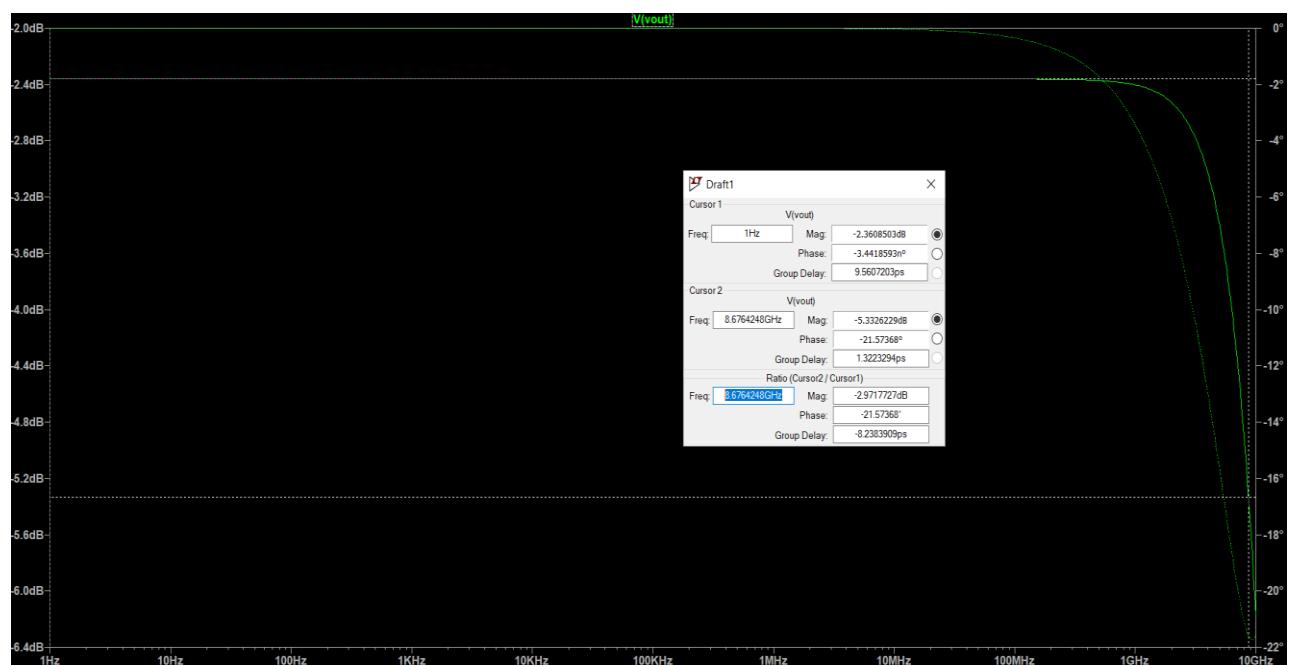The feedback is unity. We expect a 0 dB closed loop gain, however the channel length is minimum and it will cause r_o transistors to be very small. It will decrease open loop voltage gain. So we may expect a smaller closed loop gain. You can see the AC response below. Please zoom to the cursor in the graph. The closed loop gain is -2.36 dB, and the bandwidth is around 8.7 GHz. (5 pts)



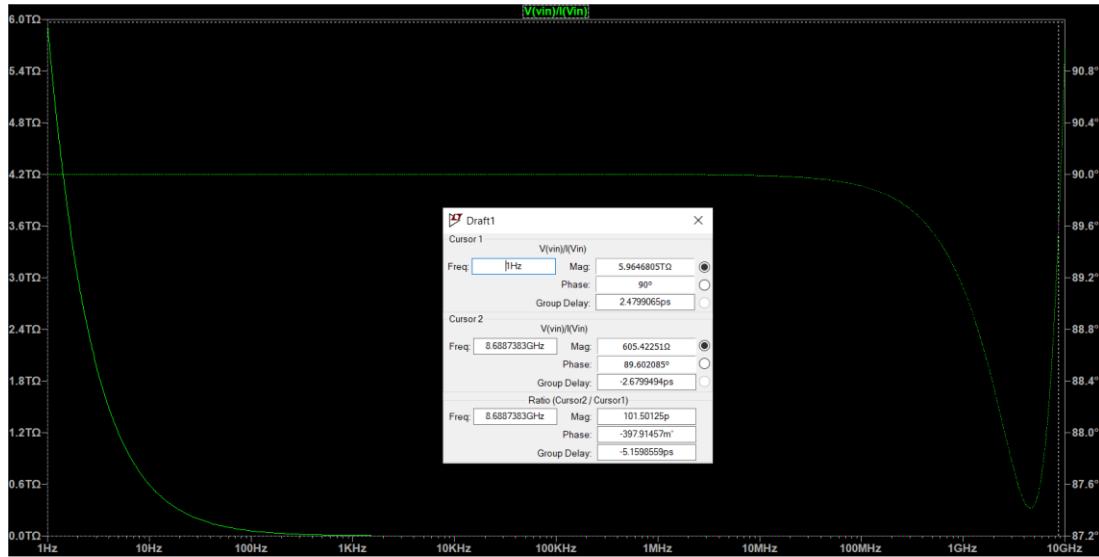For input impedance you can directly plot for V_{in}/I_{in} . As we expected the input resistance is so high (close to infinity) for low frequencies. However around 3 dB frequency it decreases to 600 ohm as parasitic capacitance (C_{gs}) comes into the play. (5 pts)



For output impedance you should not put any AC in to the input voltage source. However you should not erase the 1.1V DC at the input as we must preserve the DC conditions. Then you can either apply test voltage or test current from the output. For the test voltage you can use a very high coupling capacitor to prevent short circuit to the test voltage. Thus, applying a test current much more easier as you do not need any external component. As you can see at low frequencies, it is around 30 ohm, for high frequencies around the 3 Db frequency, it is around 107 ohm, as the feedback effect decreases and output resistance increases, which is a bad thing for a voltage output amplifier. (10 pts)

